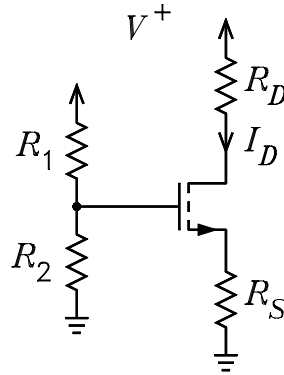



ECE3040 Assignment 4

1. (a) Calculate the drain current in an NMOS transistor if $K = 125 \mu\text{A}/\text{V}^2$, $V_{TO} = -2 \text{ V}$, $\lambda = 0$, $V_{GS} = 0 \text{ V}$, and $V_{DS} = 6 \text{ V}$. [0.5 mA] (b) Repeat assuming $\lambda = 0.025 \text{ V}^{-1}$. [0.575 mA]
2. An n -channel MOSFET has $K = 125 \mu\text{A}/\text{V}^2$, $V_{TO} = 1 \text{ V}$, and $\lambda = 0.02 \text{ V}^{-1}$. At what drain current will the MOSFET no longer be able to provide any voltage gain when connected as a common-source amplifier? Note, the maximum gain is denoted by μ_F and it is given by $\mu_F = g_m r_o$. The object here is to determine the maximum I_D such that $\mu_F \leq 1$. This will require you to select V_{DS} that minimizes μ_F before solving for I_D . [1.25 A]
3. An n -channel MOSFET has a resistor $R_D = 60 \text{ k}\Omega$ connected between its drain and a power supply voltage $V^+ = 18 \text{ V}$. At what Q-point will $r_o \parallel R_D = 50 \text{ k}\Omega$ if the transistor has $\lambda = 0.02 \text{ V}^{-1}$? Use the relations $r_o = (\lambda^{-1} + V_{DS})/I_D$, and $V_{DS} = 18 - I_D R_D$. [0.189 mA, 6.67 V]
4. The drain current in an n -channel JFET can be written $i_D = I_{DSS}(1 - v_{GS}/V_P)^2$, where $I_{DSS} = I_{DSS0}(1 + \lambda v_{DS})$. Show that the expression for the JFET can be represented in exactly the same form as that of the MOSFET using the substitution $V_{TO} = V_P$ and $K = I_{DSS}/V_P^2$.
5. For $K = 1.78 \text{ mA}/\text{V}^2$, $V_{TO} = 1.5 \text{ V}$, $V^+ = 18 \text{ V}$, $R_1 = 110 \text{ k}\Omega$, $R_2 = 68 \text{ k}\Omega$, $R_D = 0$, and $R_S = 1 \text{ k}\Omega$, solve for I_D and verify that the MOSFET is biased in the saturation region, i.e. its active mode. [$I_D = 3.897 \text{ mA}$, $V_{DS} = 14.10 \text{ V}$, $V_{GS} - V_{TO} = 1.480 \text{ V}$]



6. Add a resistor $R_3 = 20 \text{ k}\Omega$ from gate to source for the circuit in problem 5. Solve for I_D and verify that the MOSFET is biased in the saturation region. [$I_D = 0.492 \text{ mA}$, $V_{DS} = 17.41 \text{ V}$, $V_{GS} - V_{TO} = 0.526 \text{ V}$]
7. Problem 4.26 in Jaeger. Assume $K' = 25 \times 10^{-6} \text{ A}/\text{V}^2$.
8. Problem 4.34 in Jaeger. Note, $K = K_n/2 = 250 \times 10^{-6} \text{ A}/\text{V}^2$.
9. Problem 4.35 in Jaeger. Assume $K' = 25 \times 10^{-6} \text{ A}/\text{V}^2$. [(a) $I_D = 103 \mu\text{A}$, (b) $I_D = 104 \mu\text{A}$, (c) $I_D = 107 \mu\text{A}$]

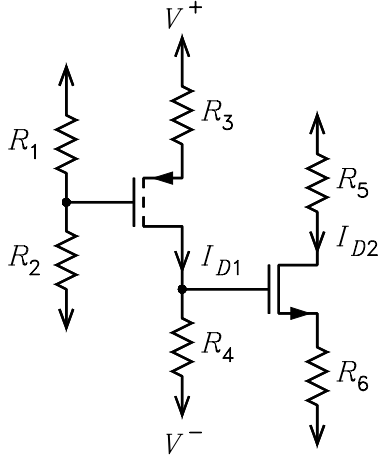10. Problem 4.41 parts (a) and (b) in Jaeger. Assume $K' = 25 \times 10^{-6} \text{ A/V}^2$. Hint: Show first that the device is operated in the triode region.
11. It is given that $K = 0.001 \text{ A/V}^2$, $V_{TH1} = 1.25 \text{ V}$, $V_{TH2} = -1.25 \text{ V}$, $V^+ = +24 \text{ V}$, $V^- = -24 \text{ V}$, $R_1 = 100 \text{ k}\Omega$, $R_3 = 1 \text{ k}\Omega$, and $R_6 = 200 \Omega$. We desire $I_{D1} = 1.5 \text{ mA}$, $I_{D2} = 5 \text{ mA}$, and $V_{DS2} = 12 \text{ V}$. Show that $R_2 = 1.108 \text{ M}\Omega$, $R_4 = 1.324 \text{ k}\Omega$, $R_5 = 7 \text{ k}\Omega$, and $V_{SD1} = 44.514 \text{ V}$. Verify that both MOSFETs are in the saturation region.



12. Assume that you are given the values for V^+ , V^- , and all the resistor values in the circuit for problem 11. Solve for I_{D1} , I_{D2} , and verify that both MOSFETs are in the saturation region.
13. Problem 13.76 in Jaeger. [$I_D = 1.25 \text{ mA}$, $W/L = 250$]
14. Problem 13.81 in Jaeger. Assume that a resistor R_D connects from the MOSFET drain to V^+ , the MOSFET source is grounded, and $V_{DS} = V^+/2$. Solve for I_D such that $R_{out} = r_0 \parallel R_D = 50 \text{ k}\Omega$.