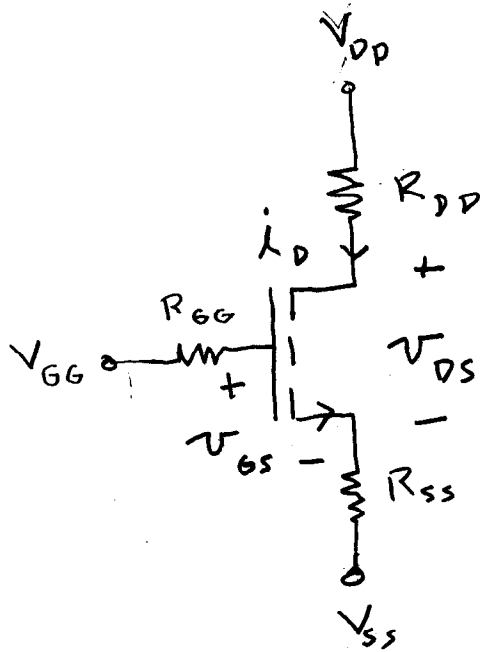


6/7/4 ①

The MOSFET DC Bias Equation

Consider the circuit



We neglect the body effect to simplify the analysis

$$V_{DD} - V_{SS} = \bar{i}_D R_{DD} + V_{DS} + \bar{i}_D R_{SS}$$


$$\Rightarrow \bar{i}_D = \frac{V_{DD} - V_{SS}}{R_{DD} + R_{SS}} - \frac{V_{DS}}{R_{DD} + R_{SS}}$$

$$V_{GG} - V_{SS} = V_{GS} + \bar{i}_D R_{SS}$$


$$\Rightarrow \bar{i}_D = \frac{V_{GG} - V_{SS}}{R_{SS}} - \frac{V_{GS}}{R_{SS}}$$

6/7/4 (2)

Graphical Solution

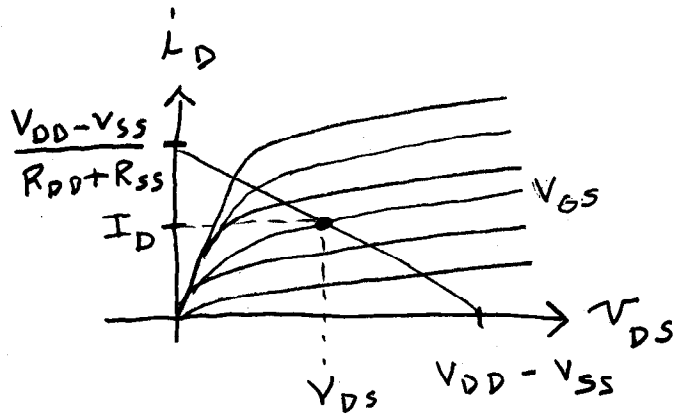

output characteristics

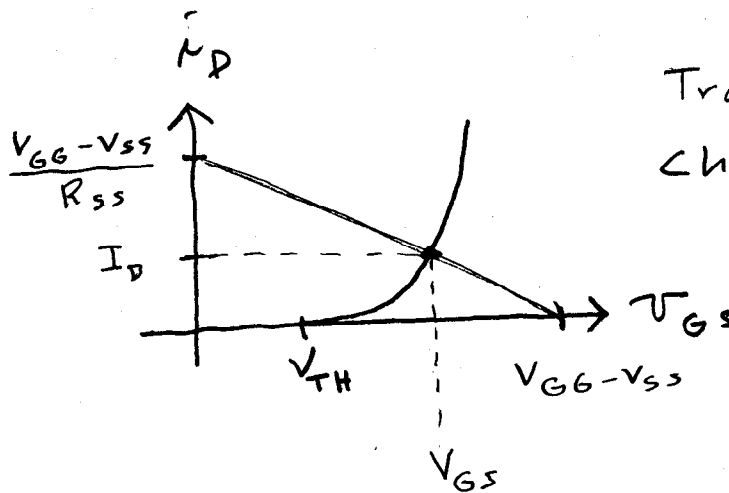

Transfer characteristic

You must plot both load lines to solve for I_D , V_{DS} , and V_{GS} .

6/7/4 (3)

Analytical Solution

$$\hat{i}_D = K (v_{GS} - v_{T0})^2$$

$$v_{GG} - v_{SS} = v_{GS} + \hat{i}_D R_{SS}$$

$$\Rightarrow v_{GS} = v_{GG} - v_{SS} - \hat{i}_D R_{SS}$$

$$\Rightarrow \hat{i}_D = K (v_{GG} - v_{SS} - \hat{i}_D R_{SS} - v_{T0})^2$$

$$\text{Let } v_1 = v_{GG} - v_{SS} - v_{T0}$$

$$\Rightarrow \hat{i}_D = K (v_1 - \hat{i}_D R_{SS})^2$$

$$\Rightarrow \frac{1}{\sqrt{K}} \sqrt{\hat{i}_D} = v_1 - \hat{i}_D R_{SS}$$

$$\text{Let } \hat{i}_D = x^2$$

$$\Rightarrow \frac{1}{\sqrt{K}} x = v_1 - x^2 R_{SS}$$

$$\Rightarrow R_{SS} x^2 + \frac{1}{\sqrt{K}} x - v_1 = 0$$

6/7/4 (4)

$$\Rightarrow x = \frac{\frac{-1}{\sqrt{k}} \pm \sqrt{\frac{1}{k} + 4R_{SS}V_1}}{2R_{SS}}$$

Must use the + sign for a positive x

$$\begin{aligned} \Rightarrow x &= \sqrt{\frac{1}{4kR_{SS}^2} + \frac{V_1}{R_{SS}}} - \frac{1}{2\sqrt{k}R_{SS}} \\ &= \frac{1}{2\sqrt{k}R_{SS}} \left[\sqrt{1 + 4kV_1R_{SS}} - 1 \right] \end{aligned}$$

$$\begin{aligned} \Rightarrow I_D &= x^2 \\ &= \frac{1}{4kR_{SS}^2} \left[\sqrt{1 + 4kV_1R_{SS}} - 1 \right]^2 \end{aligned}$$

$$V_{DD} - V_{SS} = I_D R_{DD} + V_{DS} + I_D R_{SS}$$


$$\Rightarrow V_{DS} = V_{DD} - V_{SS} - I_D (R_{DD} + R_{SS})$$

$$V_{GG} - V_{SS} = V_{GS} + I_D R_{SS}$$

$$\Rightarrow V_{GS} = V_{GG} - V_{SS} - I_D R_{SS}$$

6/7/4 (5)

Example

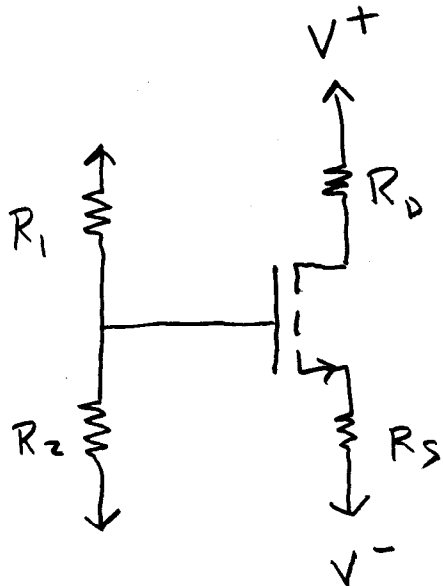

$$R_D = 5 \text{ k}\Omega$$

$$V^+ = +24 \text{ V}$$

$$V^- = -24 \text{ V}$$

$$R_1 = 5 \text{ M}\Omega$$

$$R_2 = 2 \text{ M}\Omega$$

$$R_S = 3 \text{ k}\Omega$$

$$K = 0.001 \text{ A/V}^2$$

$$V_{TH} = 1.75 \text{ V}$$

$$V_{GG} = V^+ \frac{R_2}{R_1 + R_2} + V^- \frac{R_1}{R_1 + R_2}$$

$$= -10.29 \text{ V}$$

$$R_{GG} = R_1 \parallel R_2 = 1.43 \text{ M}\Omega$$

$$V_{SS} = V^- = -24 \text{ V}, \quad R_{SS} = R_S = 3 \text{ k}\Omega$$

$$V_{DD} = V^+ = +24 \text{ V}, \quad R_{DD} = R_D = 5 \text{ k}\Omega$$

$$V_1 = V_{GG} - V_{SS} - V_{TH} = 11.96 \text{ V}$$

6/7/4 (6)

$$I_D = \frac{1}{4kR_S^2} \left[\sqrt{1 + 4kV_T R_S} - 1 \right]^2$$

$$= 3.38 \text{ mA}$$

Test for saturation or active mode

$$V_{DS} > V_{GS} - V_{TH} \text{ must hold}$$

$$V_{DS} = V_D - V_S = (V_{DD} - I_D R_D) - (V_{SS} + I_D R_{SS})$$

$$= 21.04$$

$$V_{GS} = V_{GG} - (V_S + I_D R_S)$$

$$= 3.59 \text{ V.}$$

$$V_{GS} - V_{TH} = 1.84 \text{ V, } \underline{\underline{\text{or}}} \sqrt{\frac{I_D}{k}} = 1.84 \text{ V.}$$


$$\therefore V_{DS} > V_{GS} - V_{TH}$$

\Rightarrow saturation mode

6/8/4

①

Example 2:

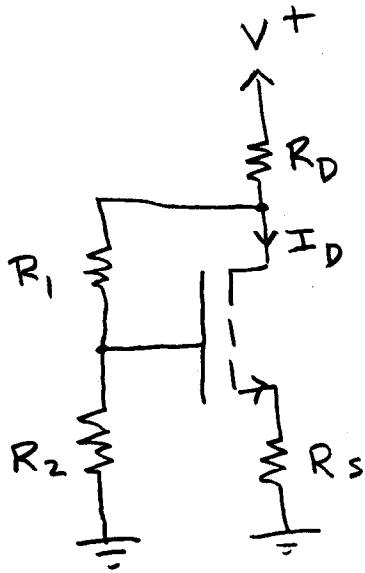

$$V^+ = 24 \text{ V}$$

$$R_D = 2.5 \text{ k}\Omega$$

$$R_S = 1 \text{ k}\Omega$$

$$R_1 = 1 \text{ M}\Omega$$

$$R_2 = 1 \text{ M}\Omega$$

$$K = 0.001 \text{ A/V}^2$$

$$V_{TH} = 1.5 \text{ V}$$

By superposition of V^+ and I_D , we have

$$V_{GG} = V^+ \frac{R_2}{R_D + R_1 + R_2} - I_D \frac{R_D}{R_D + R_1 + R_2} R_2$$

$$= 7.491 - 1199 I_D$$

$$R_{GG} = R_2 \parallel (R_1 + R_D) = 500.6 \text{ k}\Omega$$


$$V_{SS} = 0 \quad R_{SS} = R_S = 1 \text{ k}\Omega$$

$$V_{DD} = V^+ \frac{R_1 + R_2}{R_D + R_1 + R_2} = 23.97 \text{ V}$$

$$R_{DD} = R_D \parallel (R_1 + R_2) = 2.50 \text{ k}\Omega$$

6/8/4 (2)

The equivalent circuit becomes

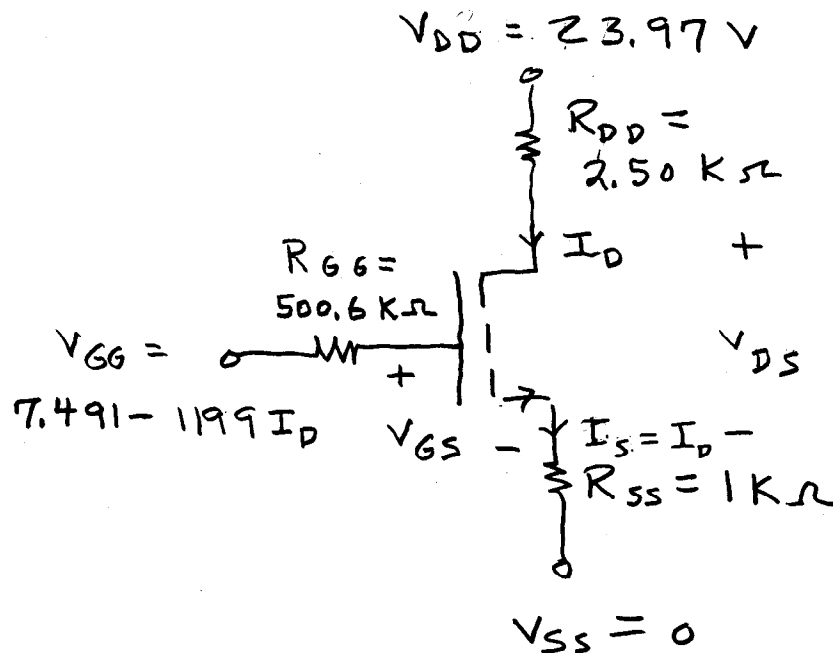

$$V_{GG} - V_{SS} = V_{GS} + I_D R_{SS}$$

$$\Rightarrow V_{GS} = V_{GG} - V_{SS} - I_D R_{SS}$$

$$I_D = K (V_{GS} - V_{TH})^2$$

$$= K (V_{GG} - V_{SS} - I_D R_{SS} - V_{TH})^2$$

$$= 0.001 (7.491 - 1199 I_D - 0 - 1000 I_D - 1.5)^2$$

$$= 0.001 (5.991 - 2199 I_D)^2$$

6/8/4 (3)

$$\text{Let } I_D = x^2$$

$$\Rightarrow x^2 = 0.001 (5.991 - 2199 x^2)^2$$

$$\Rightarrow \frac{x}{\sqrt{0.001}} = 5.991 - 2199 x^2$$

$$\Rightarrow 2199 x^2 + \frac{x}{\sqrt{0.001}} - 5.991 = 0$$

$$\Rightarrow x = \frac{\frac{-1}{\sqrt{0.001}} \pm \sqrt{\frac{1}{0.001} + 4 \times 2199 \times 5.991}}{2 \times 2199}$$

Must use the + solution for a positive answer

$$\Rightarrow x = 454.99 \times 10^{-4}$$

$$\Rightarrow I_D = x^2 = 2.07 \text{ mA}$$

Now check for the saturation or active mode

$$V_D = V_{DD} - I_D R_{DD} = 10.02 \text{ V}$$

6/8/4 (4)

$$V_S = I_D R_{SS} + V_{SS} = 2.07 \text{ V.}$$

$$V_{DS} = V_D - V_S = 7.95 \text{ V.}$$

$$V_{GS} - V_{TH} = \sqrt{\frac{I_D}{K}} = 1.53 \text{ V.}$$


$\therefore V_{DS} > V_{GS} - V_{TH} \Rightarrow$ saturation mode

The Depletion Mode MOSFET


For the enhancement mode MOSFET, $V_{TH} > 0$ because the n channel does not form until V_{GS} is made positive. A built-in n channel can be formed by a process called ion implantation. Because the n channel exists for $V_{GS} = 0$, the threshold voltage is negative, i.e. $V_{TH} < 0$.

6/8/4 (5)

The device is fabricated as follows:

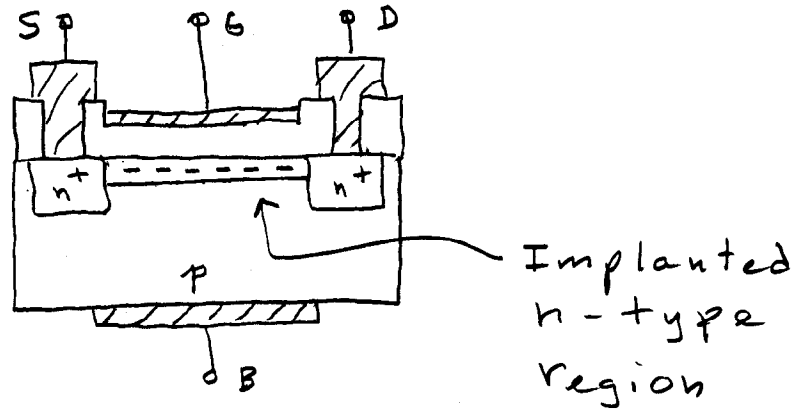

The circuit symbols are

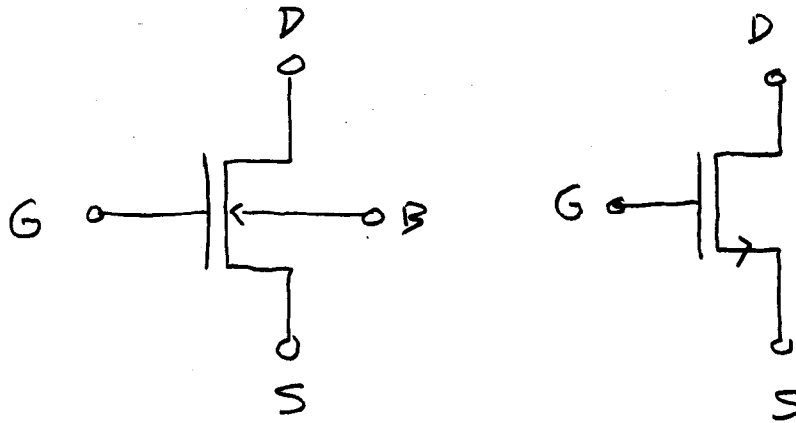


The solid line indicates a conducting channel with $V_{GS} = 0$.

The drain current is given by the same equations as for the enhancement mode

6/8/4 (6)

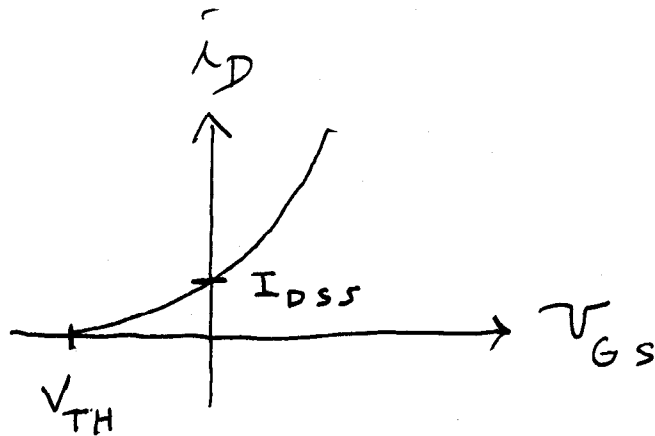device except that V_{TH} is negative. Thus the i_D versus V_{GS} curve is of the form





The value of i_D for $V_{GS} = 0$ is called I_{DSS} , the drain to source saturation current.

The P-Channel Devices



Flip over the symbols and change the directions of the arrows to obtain the following:

6/8/4 (7)

Enhancement Mode

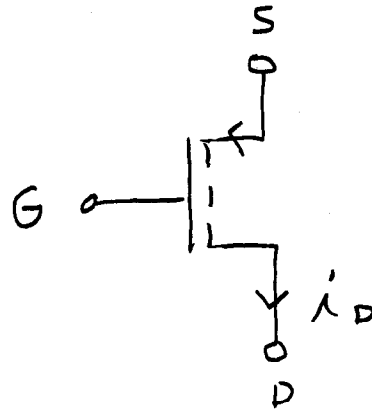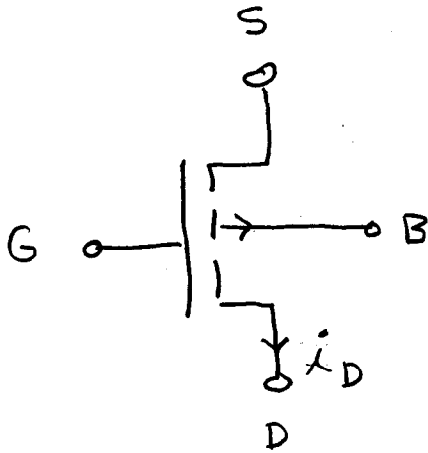

Depletion Mode

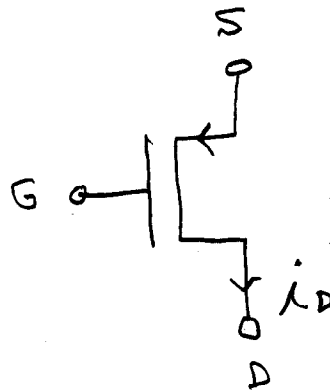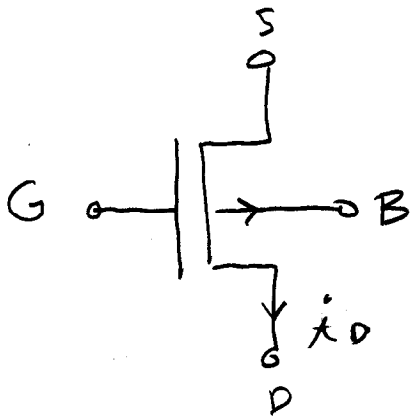

In the current equations, interchange the subscripts for all voltages.

6/8/4 (8)

Linear or Triode Region

$$I_D = 2K \left(V_{SG} - V_{TH} - \frac{V_{SD}}{2} \right) V_{SD}$$


Saturation Region

$$I_D = K (V_{SG} - V_{TH})^2$$

$$K = \frac{K'}{2} \frac{W}{L} (1 + \lambda V_{SD})$$

$$K' = \mu C_{ox}$$

Bias Example

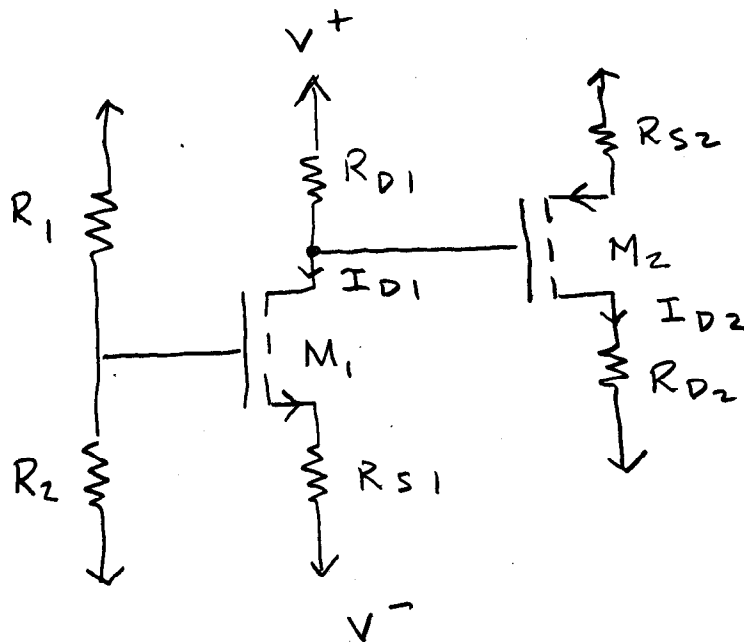

6/8/4 (9)

$$V^+ = +24 \text{ V.} \quad V^- = -24 \text{ V.}$$

$$R_1 = 5 \text{ M}\Omega \quad R_2 = 1 \text{ M}\Omega$$

$$R_{D1} = 10 \text{ K}\Omega \quad R_{S1} = 3 \text{ K}\Omega$$

$$R_{D2} = 10 \text{ K}\Omega \quad R_{S2} = 10 \text{ K}\Omega$$

$$K = 0.001 \text{ V.}$$

$$V_{TH1} = V_{TH2} = 1.75 \text{ V}$$

From a previous example, we have

$$I_{D1} = 1.655 \text{ mA}$$

For M_2 , we have

$$V_{GG2} = V^+ - I_{D1} R_{D1}$$

$$= 19.04 \text{ V.}$$

$$R_{GG2} = R_{D1} = 3 \text{ K}\Omega$$

$$V_{DD2} = V^- = -24 \text{ V.}$$


$$R_{DD2} = R_{D2} =$$

6/8/4 (10)

$$V_{SS2} = V^+ = +24 \text{ V,}$$

$$R_{SS2} = R_{S2} = 10 \text{ k}\Omega$$

The equivalent circuit for M_2 is

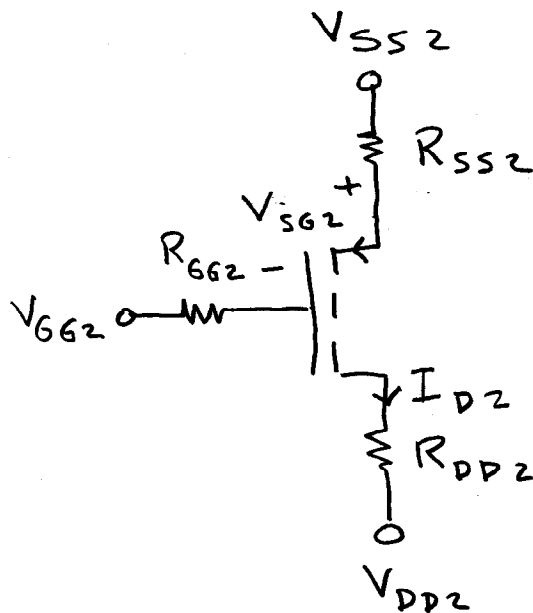

The bias equation is (omit the subscript 2)

$$V_{SS} - V_{GG} = I_D R_{SS} + V_{SG}$$

$$\Rightarrow V_{SG} = V_{SS} - V_{GG} - I_D R_{SS}$$

6/8/4

(11)

Also

$$I_D = K (V_{SG} - V_{T0})^2$$

$$\begin{aligned} \Rightarrow I_D &= K (V_{SS} - V_{GG} - I_D R_{SS} - V_{T0})^2 \\ &= K (V_{SS} - V_{GG} - V_{T0} - I_D R_{SS})^2 \end{aligned}$$

$$\text{Let } I_D = x^2$$

$$V_{SS} - V_{GG} - V_{T0} = V_1$$

$$\Rightarrow x^2 = K (V_1 - x^2 R_{SS})^2$$

$$\Rightarrow x^2 R_{SS} + \frac{x}{\sqrt{K}} - V_1 = 0$$

$$x = \frac{\frac{-1}{\sqrt{K}} \pm \sqrt{\frac{1}{K} + 4R_{SS}V_1}}{2R_{SS}} \quad \text{choose +}$$

$$= \frac{\sqrt{1 + 4KR_{SS}V_1} - 1}{2\sqrt{K} R_{SS}}$$

6/9/4

①

$$I_{D2} = x^2 = \frac{1}{4KR_{SS}^2} \left[\sqrt{1+4KR_{SS}V_1} - 1 \right]^2$$

$$\begin{aligned} V_1 &= V_{SS} - V_{GG} - V_{TH} \\ &= 24 - 19.01 - 1.75 \\ &= 3.24 \text{ V} \end{aligned}$$

$$\Rightarrow I_{D2} = 1.69 \text{ mA}$$

$$V_{SG2} - V_{TH2} = \sqrt{\frac{I_{D2}}{K}} = 1.30 \text{ V.}$$

$$V_{SD2} = V_{S2} - V_{D2}$$

$$= (V_{SS2} - I_{D2}R_{SS2}) - (V_{DD2} + I_{D2}R_{D2})$$

$$= V_{SS2} - V_{DD2} - I_{D2}(R_{SS2} + R_{D2})$$

$$= 29.41 \text{ V.}$$


$$\Rightarrow V_{SD2} > V_{SG2} - V_{TH2} \Rightarrow \text{saturation}$$

6/9/4 (2)


The Junction Field Effect Transistor

The JFET differs from the MOSFET in that the gate is separated from the channel by a pn junction rather than an insulating layer or dielectric. The devices are depletion mode devices.

Circuit Symbols

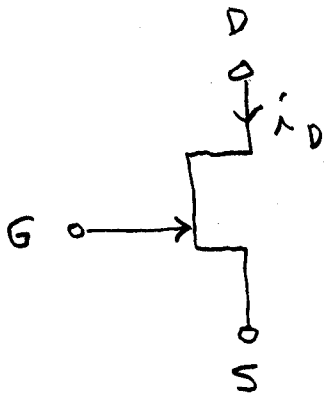

N-channel

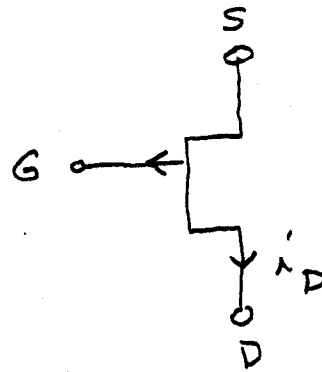

P-channel

6/9/4 (3)

For no gate current to flow,
we must have

$$V_{GS} \leq 0 \quad \text{for the n-channel}$$

$$V_{SG} \leq 0 \quad \text{for the p-channel}$$

This reverse biases the gate
to channel pn junction.

For the n-channel device

$$i_D = \beta (V_{GS} - V_{T0})^2$$

$$\beta = \beta_0 (1 + \lambda V_{DS})$$

β = transconductance parameter

V_{T0} = threshold voltage

For the p-channel device

$$i_D = \beta (V_{SG} - V_{T0})^2$$


6/9/4

④

$$\beta = \beta_0 (1 + \lambda v_{SD})$$

For both devices V_{T0} is negative.

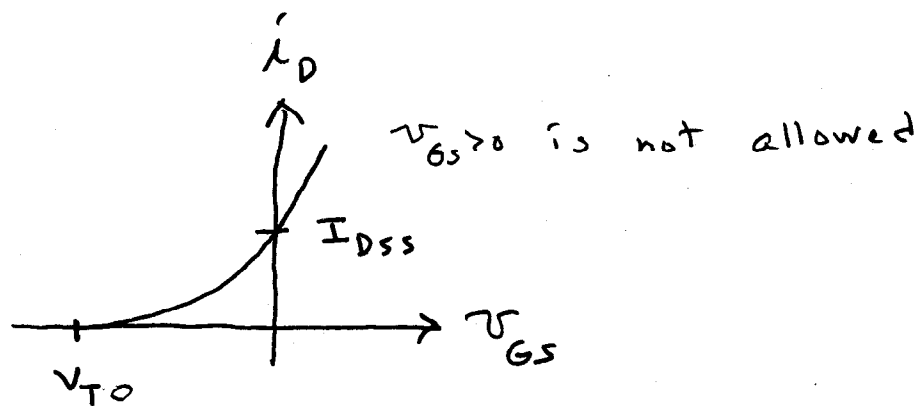Transfer Characteristics
n-channel device




$$I_{DSS} = \beta (0 - V_{T0})^2 = \beta V_{T0}^2$$

I_{DSS} is called the drain-to-source saturation current.

For the p-channel device, replace v_{GS} with v_{SG} .

6/9/4 (5)

Output characteristics n-channel Device

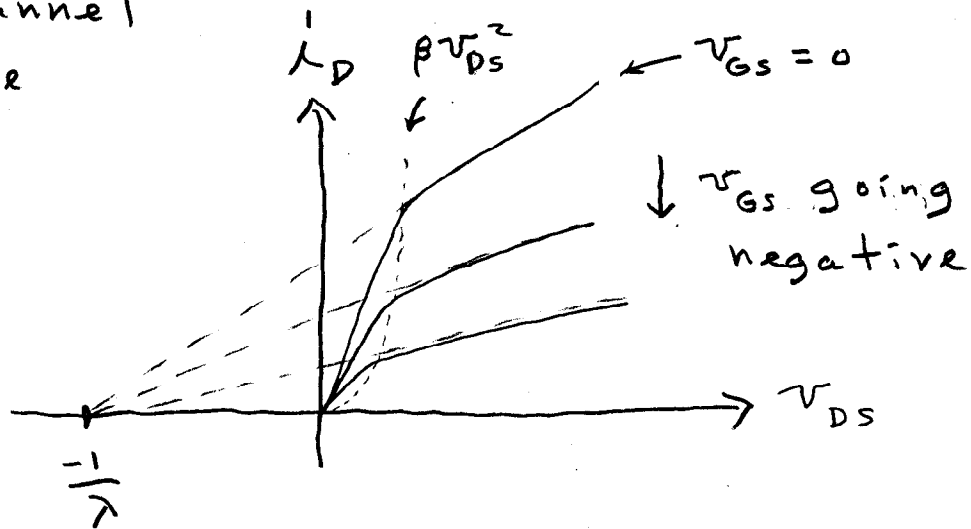

For the device to be in the saturation region, it must be operated to the right of the βV_{DS}^2 parabola. In this region


$$V_{DS} > V_{GS} - V_{TO}$$

For the p-channel device, replace V_{GS} with V_{SG} and V_{DS} with V_{SD} .

6/16/4 ①

To obtain a JFET equation from a MOSFET equation, simply replace K with β in the equation. It must be remembered that the gate-to-channel junction must be reverse biased.

The Small-Signal π Model of the MOSFET

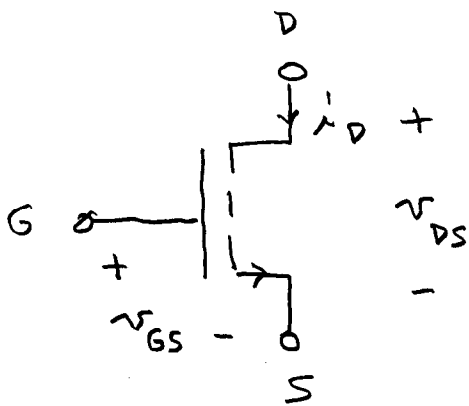

We assume that the body is connected to the source for this derivation.


$$i_D = K (v_{GS} - V_{TH})^2$$

$$K = \frac{K'}{2} \frac{W}{L} (1 + \lambda v_{DS})$$

$$K' = \mu C_{ox}$$

6/10/4 (2)

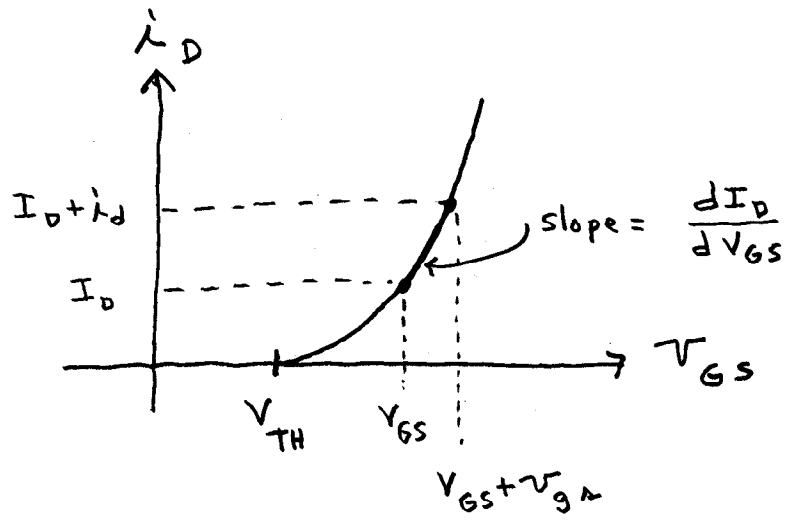First, we look at the transfer characteristics for $v_{DS} = \text{const.}$



The Q point is (v_{GS}, I_D) . We wish to relate the small-signal change in i_D to the small-signal change in v_{GS} . The slope of the curve at the Q point is used to do this.

$$I_D = K (v_{GS} - v_{TH})^2$$

$$\frac{dI_D}{dv_{GS}} = 2K (v_{GS} - v_{TH})$$

6/10/4 (3)

$$\text{But } (V_{GS} - V_{TH}) = \sqrt{\frac{I_D}{K}}$$

$$\Rightarrow \frac{dI_D}{dV_{GS}} = 2K \sqrt{\frac{I_D}{K}} = 2\sqrt{KI_D}$$

We define the transconductance g_m by

$$g_m = \frac{dI_D}{dV_{GS}} = 2\sqrt{KI_D}$$

This must be equal to

$$g_m = \frac{\Delta I_D}{\Delta V_{GS}} = \frac{I_D}{V_{GS}}$$

$$\Rightarrow I_D = g_m V_{GS}$$


This only holds for $V_{DS} = \text{constant}$.

Now, suppose we hold V_{GS} constant and vary V_{DS} .

6/10/4 (4)

$$i_D = \frac{K'}{2} \frac{W}{L} (1 + \lambda v_{DS}) (v_{GS} - V_{TH})^2$$

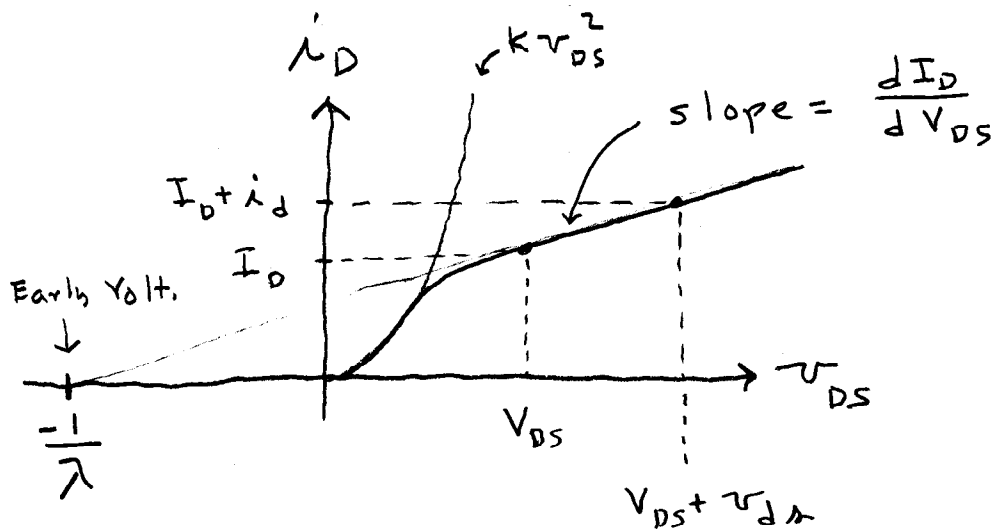We plot the output characteristics for $v_{GS} = \text{const}$ as follows:



$$I_D = \frac{K'}{2} \frac{W}{L} (1 + \lambda V_{DS}) (V_{GS} - V_{TH})^2$$

$$\frac{dI_D}{dV_{DS}} = \frac{K'}{2} \frac{W}{L} \lambda (V_{GS} - V_{TH})^2$$

$$\text{But } \frac{K'}{2} \frac{W}{L} (V_{GS} - V_{TH})^2 = \frac{I_D}{1 + \lambda V_{DS}}$$

$$\Rightarrow \frac{dI_D}{dV_{DS}} = \frac{\lambda I_D}{1 + \lambda V_{DS}} = \frac{I_D}{\frac{1}{\lambda} + V_{DS}}$$

\uparrow Early Volt.

6/10/4 (5)

Let us define the resistance r_o by

$$\frac{1}{r_o} = \frac{dI_D}{dV_{DS}} = \frac{I_D}{\frac{1}{\lambda} + V_{DS}}$$

We can relate a small-signal change in \hat{i}_D to a small-signal change in v_{DS} as follows

$$\frac{1}{r_o} = \frac{\Delta \hat{i}_D}{\Delta v_{DS}} = \frac{\hat{i}_D}{v_{DS}}$$

$$\Rightarrow \hat{i}_D = \frac{v_{DS}}{r_o}$$

This only holds for $v_{GS} = \text{constant}$.

Suppose both v_{GS} and v_{DS} vary.

Let $v_{gs} = \Delta v_{GS}$, $v_{ds} = \Delta v_{DS}$, and

$\hat{i}_D = \Delta \hat{i}_D$. It follows that

$$\hat{i}_D = g_m v_{gs} + \frac{v_{ds}}{r_o}$$

6/10/4

⑥

Because no gate current flows,
we have $\Delta \hat{i}_G = \hat{i}_g = 0$

Thus we have the two
equations

$$\hat{i}_g = 0$$

$$\hat{i}_D = g_m v_{gs} + \frac{v_{ds}}{r_o}$$

where $g_m = 2\sqrt{K I_D}$


$$r_o = \frac{\frac{1}{\lambda} + V_{DS}}{I_D}$$

Note that $\Delta \hat{i}_S = \hat{i}_A = \hat{i}_D + \hat{i}_g$
must hold. Thus we have

$$\hat{i}_A = \hat{i}_D$$

6/10/4 (7)

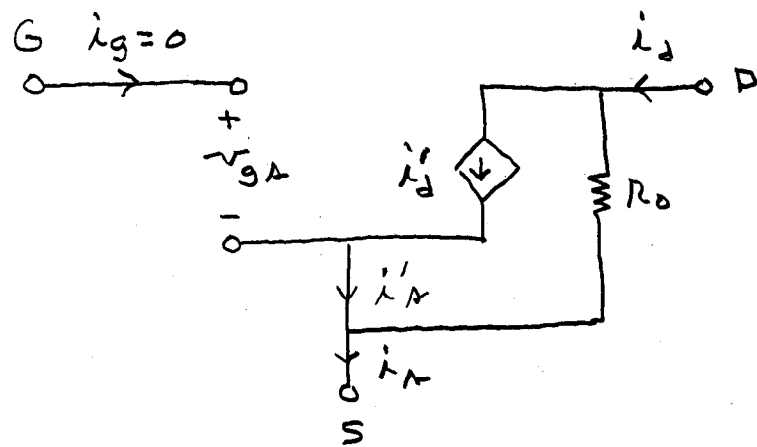Thus we can draw the following small signal circuit model



where $i'_d = g_m v_{gs}$

This is called the π model. It cannot be used to predict Q point values.

Because $i'_s = i'_d = g_m v_{gs}$, we have

$$v_{gs} = \frac{1}{g_m} i'_s$$

Let us define $R_s = \frac{1}{g_m}$

6/10/4 (8)


Thus we have the alternate set of equations

$$i_g = 0$$

$$i_d = i'_d + \frac{v_{dA}}{R_0}$$

$$i'_d = \frac{v_{gA}}{R_A}$$

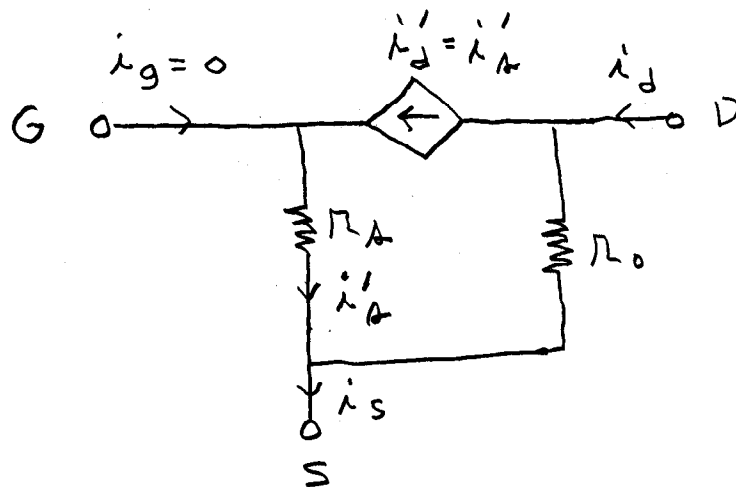The circuit which models these equations is



This is called the T model. Either model can be used to calculate the currents.