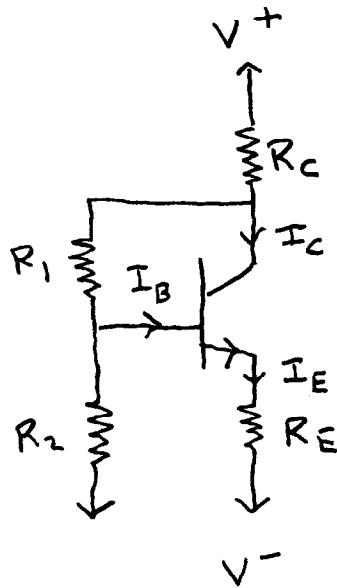


6/23/4 (10)

## Example 3



$$V^+ = +24 \text{ V.}$$

$$\beta = 99$$

$$V^- = -24 \text{ V.}$$

$$\alpha = 0.99$$

$$R_C = 7.5 \text{ k}\Omega$$

$$V_{BE} = 0.65 \text{ V.}$$

$$R_1 = 2 \text{ M}\Omega$$

$$R_2 = 1.2 \text{ M}\Omega$$

$$R_E = 6.2 \text{ k}\Omega$$

$$V_{BB} = V^+ \frac{R_2}{R_C + R_1 + R_2} + V^- \frac{R_1 + R_C}{R_C + R_1 + R_2}$$

$$- I_C \frac{R_C}{R_C + R_1 + R_C} R_2$$

$$= -6.042 - 2806 I_C$$

$$R_{BB} = (R_1 + R_C) \parallel R_2 = 751.1 \text{ k}\Omega$$

$$V_{BB} - V_{EE} = -6.042 - 2806 I_C - (-24)$$

$$= 17.958 - 2806 I_C$$

6/23/4

⑪

$$\begin{aligned}
 \text{But } V_{BB} - V_{EE} &= I_B R_{BB} + V_{BE} + I_E R_E \\
 &= \frac{I_C}{\beta} R_{BB} + V_{BE} + \frac{I_C}{\alpha} R_E \\
 &= 13.85 \times 10^3 I_C + 0.65
 \end{aligned}$$

$$\Rightarrow 17.958 - 2806 I_C = 13.85 \times 10^3 I_C + 0.65$$

$$\Rightarrow I_C = \frac{17.958 - 0.65}{2806 + 13.85 \times 10^3} = 1.039 \text{ mA}$$

Next we test for the active mode.

$$V_{CB} = (V_{CC} - I_C R_{CC}) - (V_{BE} + I_E R_E + V^-)$$

$$\begin{aligned}
 \text{But } V_{CC} &= V^+ \frac{R_1 + R_2}{R_C + R_1 + R_2} + V^- \frac{R_C}{R_C + R_1 + R_2} \\
 &\quad - I_B \frac{R_2}{R_C + R_1 + R_2}
 \end{aligned}$$


$$= 23.858 \text{ V.}$$

$$R_{CC} = R_C \parallel (R_1 + R_2) = 7482 \Omega$$

$$\begin{aligned}
 V_{CB} &= (V_{CC} - I_C R_{CC}) - (V_{BE} + \frac{I_C}{\alpha} R_E + V^-) \\
 &= 32.92 \text{ V} \Rightarrow \text{active mode}
 \end{aligned}$$

6/28/4 ①
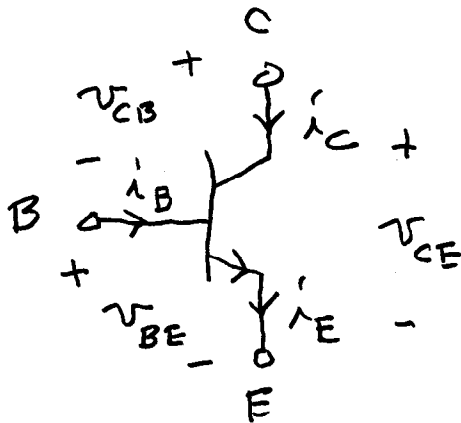
# The Small-Signal $\pi$ Model of the BJT



We assume the active mode and neglect the leakage current terms

$$i_C = I_S e^{v_{BE}/V_T}$$


$$i_B = \frac{1}{\beta} i_C$$

$$I_S = I_{S0} \left( 1 + \frac{v_{CE}}{V_A} \right)$$

$$\beta = \beta_0 \left( 1 + \frac{v_{CE}}{V_A} \right)$$

First, we look at the transfer characteristics for  $v_{CE} = \text{const.}$   
 $\Rightarrow I_S = \text{const.} \Rightarrow i_C$  is a function of  $v_{BE}$  only.

6/28/4 (2)

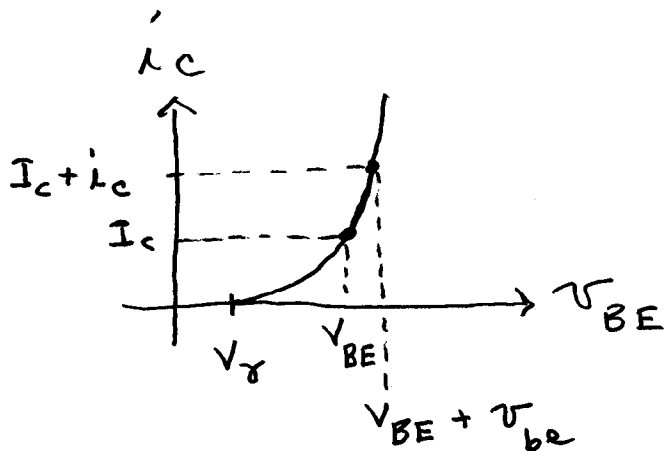

The Q point is  $(V_{BE}, I_c)$ . We wish to relate the small-signal change in  $i_c$  to the small-signal change in  $v_{BE}$ . The slope of the curve at the Q point is used to do this.

$$I_c = I_s e^{V_{BE}/V_T}$$

$$\frac{dI_c}{dV_{BE}} = \frac{1}{V_T} I_c e^{V_{BE}/V_T} = \frac{I_c}{V_T}$$

We define the transconductance  $g_m$  by

$$g_m = \frac{dI_c}{dV_{BE}} = \frac{I_c}{V_T}$$

6/28) 4 (3)

This must be equal to

$$g_m = \frac{\Delta \hat{i}_c}{\Delta v_{BE}} = \frac{\hat{i}_c}{v_{be}}$$


$$\Rightarrow \hat{i}_c = g_m v_{be}$$

This only holds for  $v_{CE} = \text{const.}$

Now suppose we hold  $v_{be}$  const. and vary  $v_{CE}$ . We have already seen that if  $v_{BE} = \text{const.}$ , then  $\hat{i}_B = \text{const.}$

$$\Rightarrow \hat{i}_c = \beta \hat{i}_B = \beta_0 \left( 1 + \frac{v_{CE}}{V_A} \right) \hat{i}_B$$

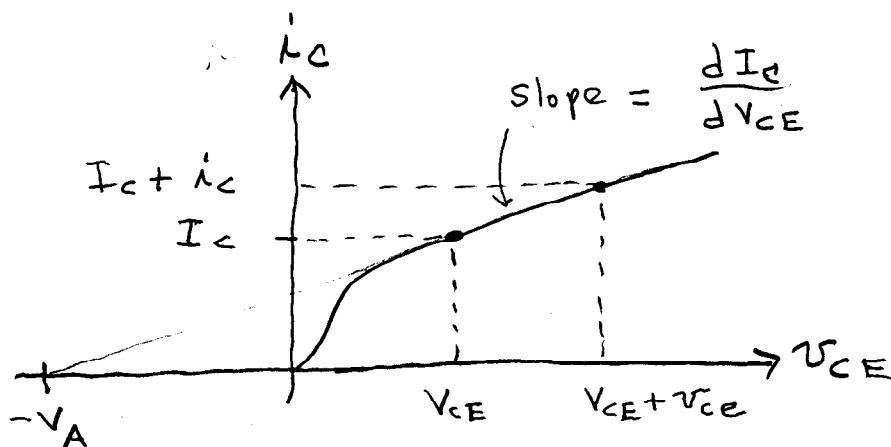We plot the output characteristics with  $\hat{i}_B = \text{const.}$  as follows:



6/28/4 (4)

$$I_c = \beta_0 \left( 1 + \frac{V_{CE}}{V_A} \right) I_B$$

$$\frac{dI_c}{dV_{CE}} = \beta_0 \frac{1}{V_A} I_B$$

$$\text{But } \beta_0 I_B = \frac{I_c}{1 + \frac{V_{CE}}{V_A}}$$

$$\Rightarrow \frac{dI_c}{dV_{CE}} = \frac{1}{V_A} \frac{I_c}{1 + \frac{V_{CE}}{V_A}} = \frac{I_c}{V_A + V_{CE}}$$

Let us define the resistance  $r_o$  by

$$\frac{1}{r_o} = \frac{dI_c}{dV_{CE}} = \frac{I_c}{V_A + V_{CE}}$$

$$\Rightarrow r_o = \frac{V_A + V_{CE}}{I_c}$$

We can relate a small-signal change in  $i_c$  to a small-signal change in  $v_{ce}$  as follows

$$\frac{1}{r_o} = \frac{\Delta i_c}{\Delta v_{ce}} = \frac{i_c}{v_{ce}}$$

$$\Rightarrow i_c = \frac{v_{ce}}{r_o}$$

6/28/4 (5)


This only holds for  $v_{BE} = \text{const.}$   
 (or  $\bar{i}_B = \text{const.}$ ). Suppose both  
 $v_{BE}$  and  $v_{CE}$  vary. Let  $v_{be} = \Delta v_{BE}$ ,  
 $v_{ce} = \Delta v_{CE}$ , and  $i_c = \Delta \bar{i}_c$ . It  
 follows that

$$\bar{i}_c = g_m v_{be} + \frac{v_{ce}}{r_o}$$

Now, let us plot  $\bar{i}_B$  versus  $v_{BE}$   
 for  $v_{CE} = \text{const.}$

$$\bar{i}_B = \frac{1}{\beta} \bar{i}_c = \frac{I_S}{\beta} e^{v_{BE}/V_T} = \frac{I_{S0}}{\beta_0} e^{v_{BE}/V_T}$$

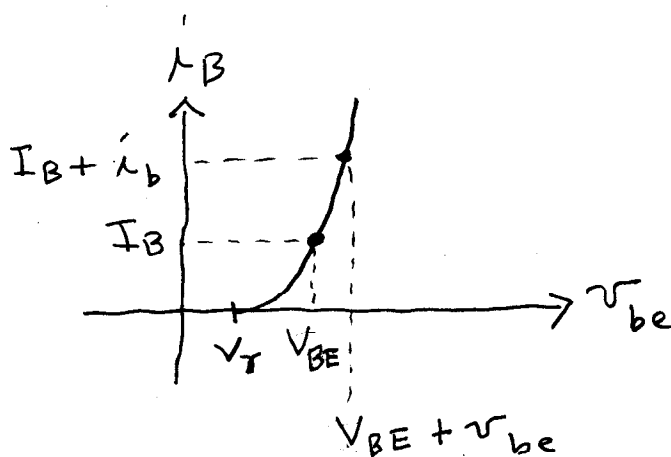Note that the  $1 + v_{CE}/V_A$  terms in  
 $I_S$  and  $\beta$  have cancelled.



6/28/4 (6)

The Q point is  $(V_{BE}, I_B)$ . We wish to relate the small-signal change in  $I_B$  to the small-signal change in  $V_{BE}$ . The slope of the curve at the Q point is used to do this

$$I_B = \frac{I_{S0}}{\beta_0} e^{V_{BE}/V_T}$$

$$\begin{aligned} \frac{dI_B}{dV_{BE}} &= \frac{1}{V_T} \frac{I_{S0}}{\beta_0} e^{V_{BE}/V_T} \\ &= \frac{I_B}{V_T} \end{aligned}$$

Let us define the resistance  $R_\pi$  by

$$\frac{1}{R_\pi} = \frac{dI_B}{dV_{BE}} = \frac{I_B}{V_T}$$

$$\Rightarrow R_\pi = \frac{V_T}{I_B}$$

We can relate a small-signal change in  $I_B$  to a small-signal change in



6/28/4 (7)

 $v_{be}$  as follows

$$\frac{1}{r_{\pi}} = \frac{\Delta \hat{i}_B}{\Delta v_{BE}} = \frac{\hat{i}_b}{v_{be}}$$

$$\Rightarrow \hat{i}_b = \frac{v_{be}}{r_{\pi}}$$

Notice that  $\hat{i}_b$  is not a function of  $v_{ce}$  because the Early effect cancels in the equation for  $\hat{i}_B$ .

Summary:

$$\hat{i}_b = \frac{v_{be}}{r_{\pi}}$$


$$\hat{i}_c = g_m v_{be} + \frac{v_{ce}}{r_o}$$

Let us define  $\hat{i}'_c = g_m v_{be}$  so that  $\hat{i}_c$  can be written

$$\hat{i}_c = \hat{i}'_c + \frac{v_{ce}}{r_o}$$

6/28/4 (8)

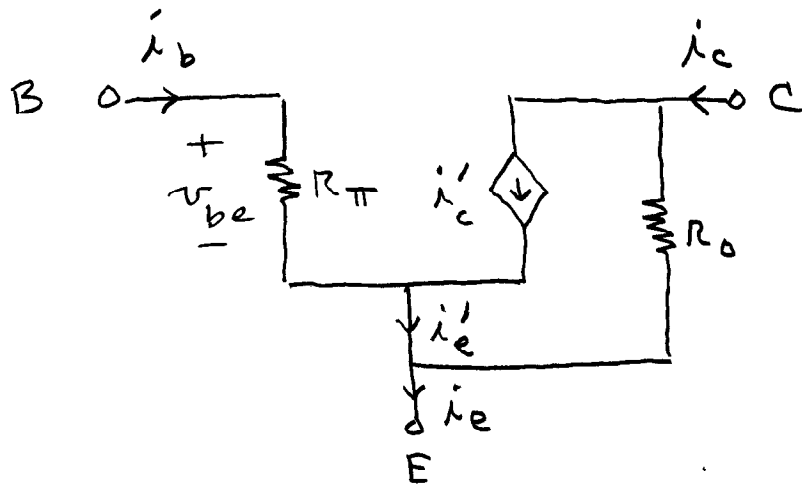The circuit which models these equations is



where  $i'_c = g_m v_{be}$

The above circuit is called the hybrid- $\pi$  model of the BJT.

We can relate  $g_m$  and  $R_\pi$  as follows:

$$g_m = \frac{I_c}{V_T} = \frac{\beta I_B}{V_T} = \frac{\beta}{R_\pi}$$

$$\Rightarrow \beta = g_m R_\pi$$

We can relate the currents as follows:

6/28/4 (9)

$$\hat{i}_c' = g_m v_{be} = g_m \hat{i}_b r_\pi = \beta \hat{i}_b$$

$$\Rightarrow \hat{i}_c' = \beta \hat{i}_b$$

$$\hat{i}_e' = \hat{i}_b + \hat{i}_c' = \frac{\hat{i}_c'}{\beta} + \hat{i}_c' = \frac{1+\beta}{\beta} \hat{i}_c'$$

$$\text{But } \alpha = \frac{\beta}{1+\beta} \Rightarrow \hat{i}_e' = \frac{\hat{i}_c'}{\alpha}$$

$$\Rightarrow \hat{i}_c' = \alpha \hat{i}_e'$$

Thus we have 3 equations for  $\hat{i}_c'$ :

$$\hat{i}_c' = g_m v_{be} = \beta \hat{i}_b = \alpha \hat{i}_e'$$

Either of these can be used in analyzing a BJT circuit.

Next, we convert the  $\pi$  model to the T model.

$$v_{be} = \hat{i}_b r_\pi = \frac{\hat{i}_c'}{\beta} r_\pi = \frac{\alpha \hat{i}_e'}{\beta} r_\pi$$

6/28/4 (10)


Let us define the resistance  $R_e$  by

$$R_e = \frac{\alpha}{\beta} R_{\pi} = \frac{\alpha}{\beta} \frac{V_T}{I_B} = \frac{\alpha V_T}{I_C} = \frac{V_T}{I_E}$$

$$\Rightarrow v_{be} = i_e' R_e$$

$$i_c' = \alpha i_e' + \frac{v_{ce}}{R_o}$$

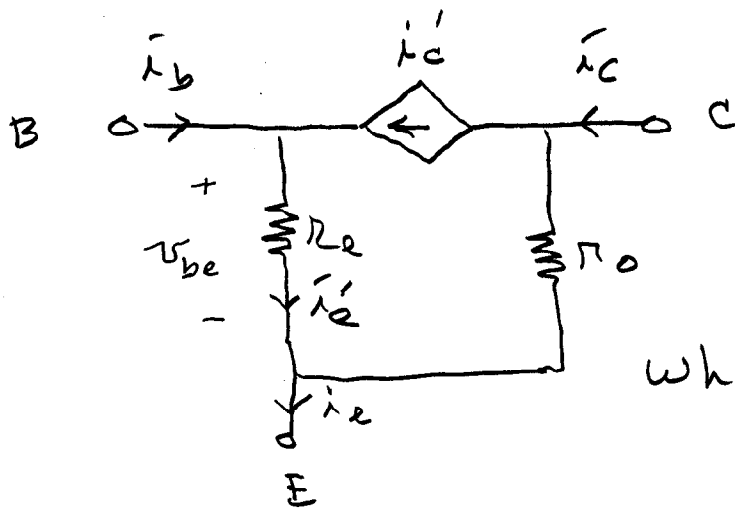The circuit which models these equations is




where  $i_c' = \alpha i_e'$

This is called the T model. In this circuit,  $i_c'$  can be calculated from one of the 3 equations

$$i_c' = g_m v_{be} = \beta i_b = \alpha i_e'$$

6/29/4 ①

## The Common Emitter Amplifier

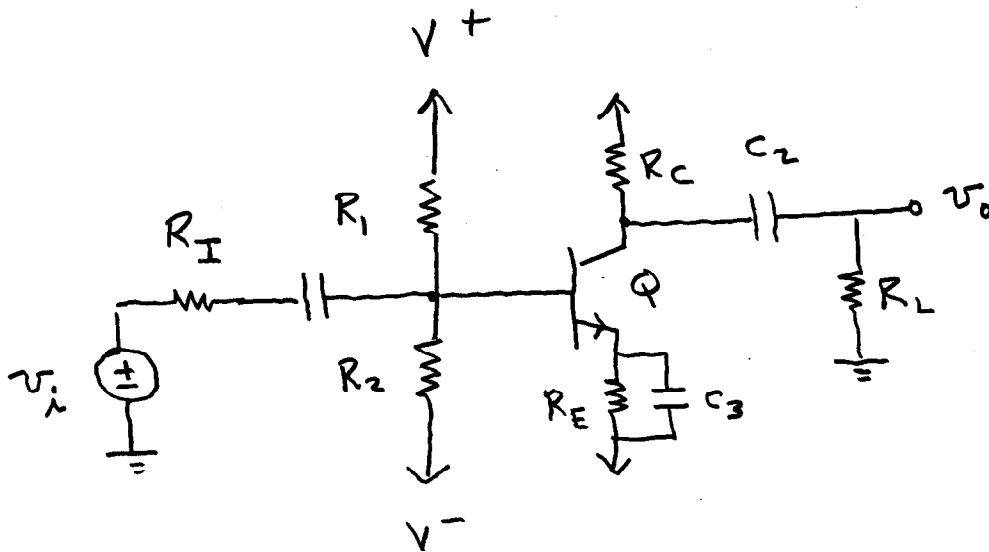


The Q point values are calculated with  $C_1$ ,  $C_2$ , and  $C_3$  open circuited. We assume this solution is known.

For a sinusoidal signal, the complex impedance of a capacitor is given by  $Z_c = 1/j\omega C$ . If  $\omega C$  is sufficiently large,  $|Z_c|$  can be made small enough to be considered an ac short circuit. We assume each C can be considered an ac short circuit.

6/29/4 (2)

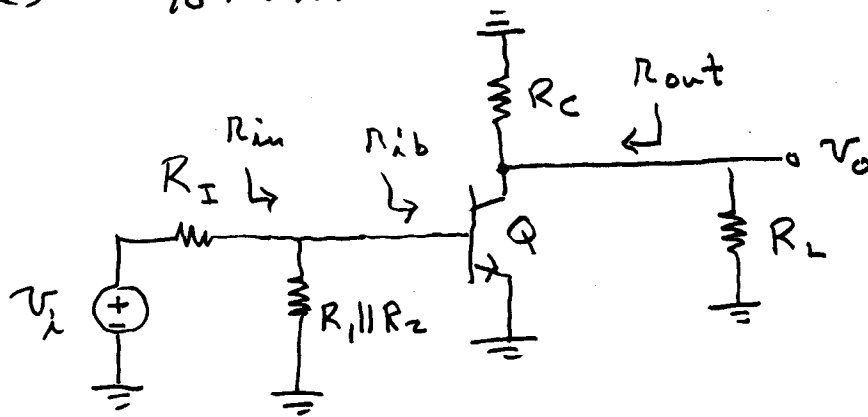The ac signal equivalent circuit is as follows:




The input resistance is given by

$$R_{in} = R_1 \parallel R_2 \parallel r_{ib}$$

where  $r_{ib}$  is the small-signal resistance looking into the base. From the  $\pi$  model, this is  $r_{ib} = r_{\pi} = V_T / I_B$ . Note that  $r_{ib} \neq r_{\pi}$  if the emitter is not grounded.

To solve for the output voltage, we make a Thevenin equivalent circuit looking out of the base


6/29/4 (3)

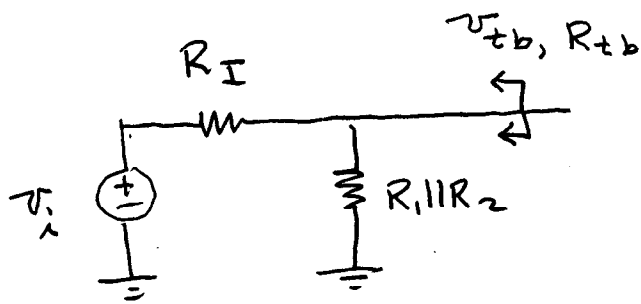

$$v_{tb} = v_i \frac{R_1 \parallel R_2}{R_I + R_1 \parallel R_2}$$

$$R_{tb} = R_I \parallel R_1 \parallel R_2$$


The new circuit is

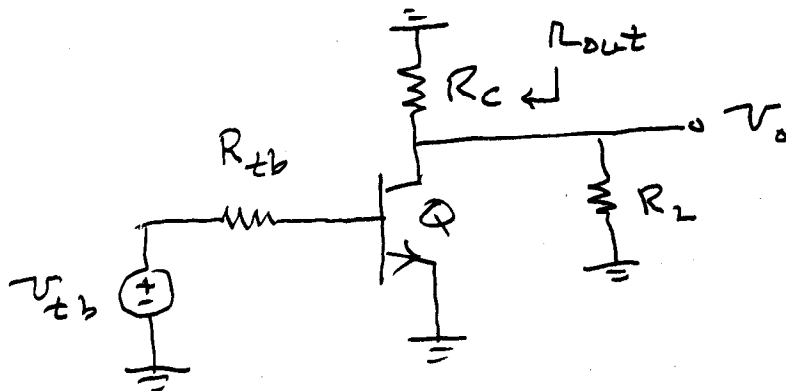

To solve for  $v_o$  and  $R_{out}$ , we replace  $Q$  with either the  $\pi$  or the  $T$  model. Let us first use the  $\pi$  model.

6/29/4

(4)

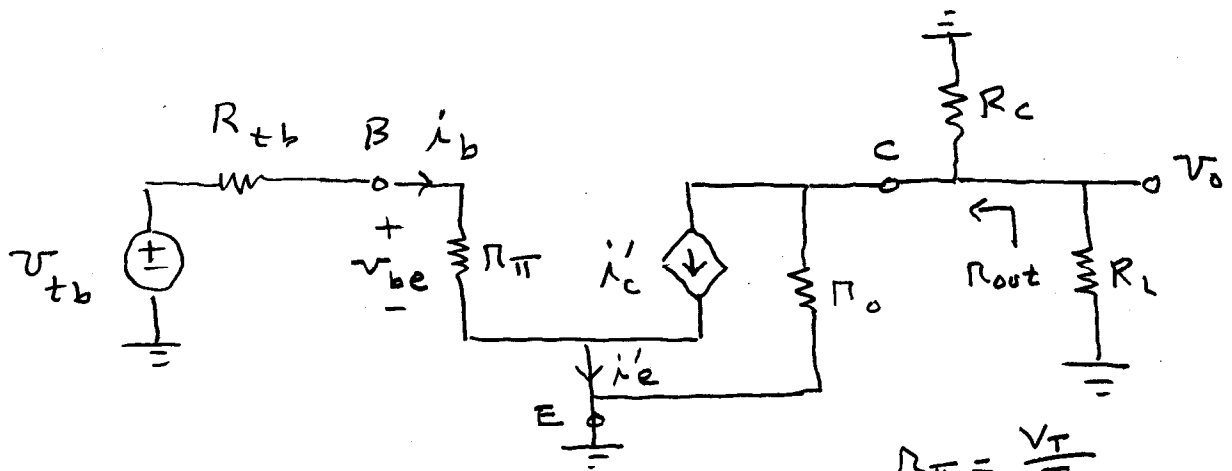

$$r_{\pi} = \frac{V_T}{I_B}$$

$$r_o = \frac{V_A + V_{CE}}{I_C}$$

$$v_o = -i'_c (r_o \parallel R_c \parallel R_L)$$

$$i'_c = \beta i_b = \beta \frac{v_{tb}}{R_{tb} + r_{\pi}}$$

$$\Rightarrow v_o = -\beta \frac{r_o \parallel R_c \parallel R_L}{R_{tb} + r_{\pi}} v_{tb}$$

$$= -\beta \frac{r_o \parallel R_c \parallel R_L}{R_{tb} + r_{\pi}} \frac{R_1 \parallel R_2}{R_I + R_1 \parallel R_2} v_i$$

Alternate solution ( $g_m = I_C / V_T$ )

$$i'_c = g_m v_{be} = g_m v_{tb} \frac{r_{\pi}}{R_{tb} + r_{\pi}}$$

But we remember that  $g_m r_{\pi} = \beta$

$$\Rightarrow i'_c = \beta \frac{v_{tb}}{R_{tb} + r_{\pi}}$$




6/29/4 (5)

This is the same solution obtained above. The output resistance is given by

$$R_{out} = R_o \parallel R_c$$

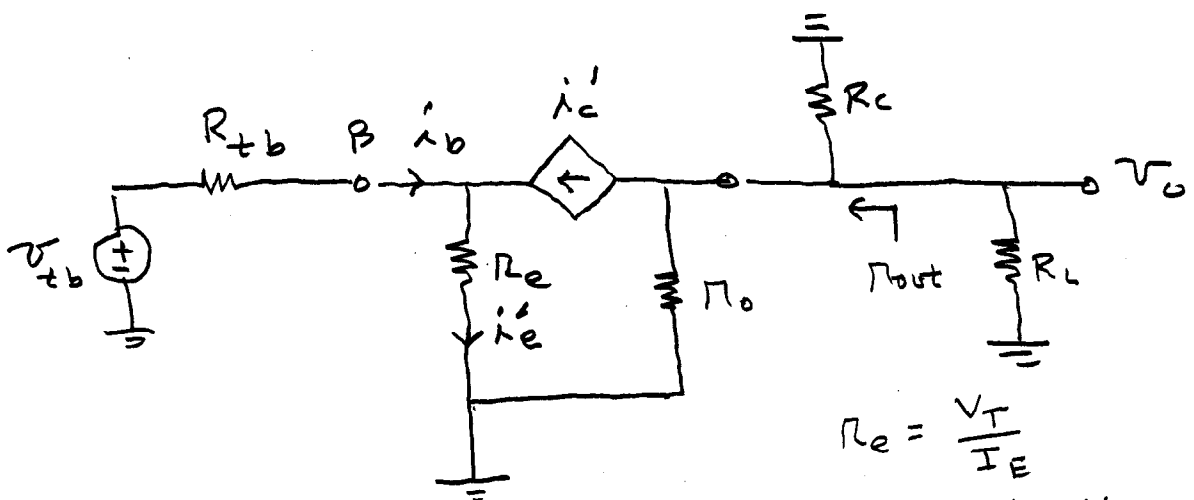Next, we repeat the solution with the T model.



$$R_e = \frac{V_T}{I_E}$$

$$R_o = \frac{V_A + V_{CE}}{I_C}$$

$$v_{tb} = i_b R_{tb} + i_e' R_e$$

$$= \frac{i_e'}{1+\beta} R_{tb} + i_e' R_e$$

$$\Rightarrow i_e' = \frac{v_{tb}}{\frac{R_{tb}}{1+\beta} + R_e}$$

$$v_o = -i_c' (R_o \parallel R_c \parallel R_L)$$

6/29/4 (6)

But  $\bar{i}'_c = \alpha \bar{i}'_e$

$\Rightarrow v_o = -\alpha \bar{i}'_e (r_o \parallel R_c \parallel R_L)$


$= -\alpha \frac{v_{tb}}{\frac{R_{tb}}{1+\beta} + r_e} (r_o \parallel R_c \parallel R_L)$

$= -\alpha \frac{r_o \parallel R_c \parallel R_L}{\frac{R_{tb}}{1+\beta} + r_e} \frac{R_I \parallel R_2}{R_I + R_I \parallel R_2} v_i$

$r_{out} = r_o \parallel R_c$

The two solutions are equivalent.

### The Common Collector Amplifier

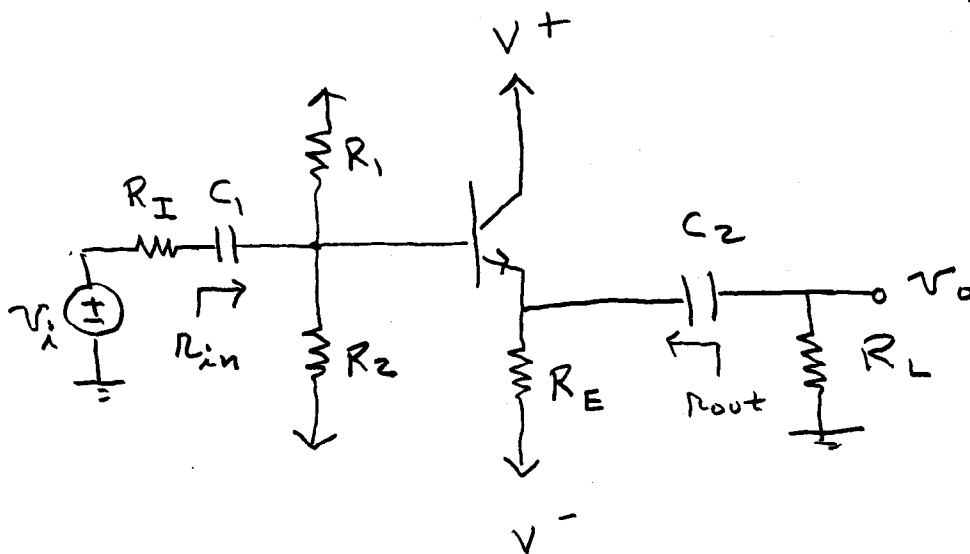


6/29/4 (7)

We assume the Q point solution. In the ac signal circuit, make a Thévenin equivalent looking out of the base as in the CE amplifier.

$$V_{tb} = V_i \frac{R_1 \parallel R_2}{R_I + R_1 \parallel R_2}$$

$$R_{tb} = R_I \parallel R_1 \parallel R_2$$

The pi model circuit is

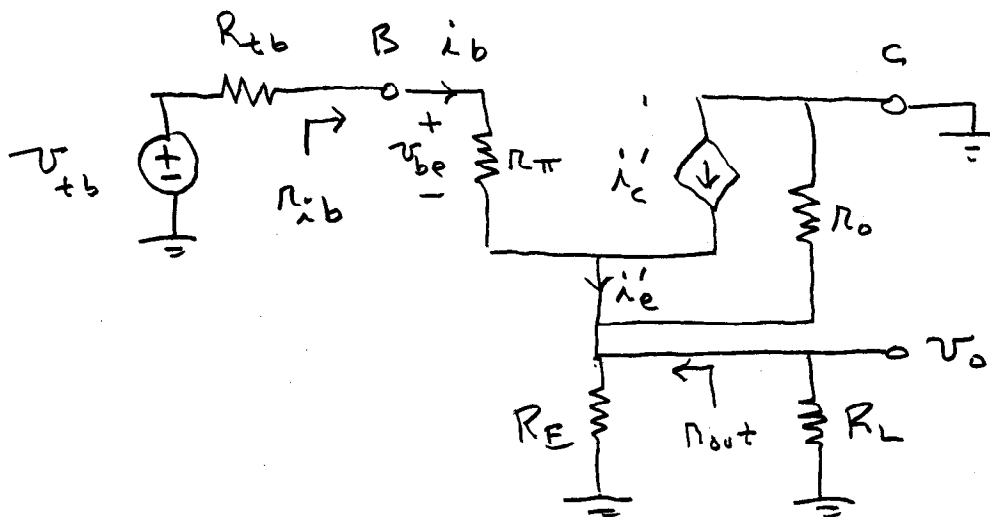

6/29/4 (8)

$$v_o = i_e' (R_o \parallel R_E \parallel R_L)$$

$$\begin{aligned} v_{tb} &= i_b' (R_{tb} + R_\pi) + i_e' (R_o \parallel R_E \parallel R_L) \\ &= \frac{i_e'}{1+\beta} (R_{tb} + R_\pi) + i_e' (R_o \parallel R_E \parallel R_L) \end{aligned}$$

$$\Rightarrow i_e' = \frac{v_{tb}}{\frac{R_{tb} + R_\pi}{1+\beta} + R_o \parallel R_E \parallel R_L}$$


$$\Rightarrow v_o = \frac{R_o \parallel R_E \parallel R_L}{\frac{R_{tb} + R_\pi}{1+\beta} + R_o \parallel R_E \parallel R_L} \cdot v_{tb}$$

$$= \frac{R_o \parallel R_E \parallel R_L}{\frac{R_{tb} + R_\pi}{1+\beta} + R_o \parallel R_E \parallel R_L} \cdot \frac{R_1 \parallel R_2}{R_I + R_1 \parallel R_2} v_i$$


Note that  $\frac{v_o}{v_i} \leq 1$

6/29/4 (9)

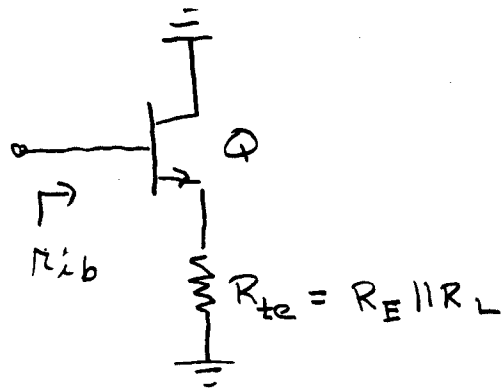To solve for  $R_{in}$ , we must solve for  $R_{ib}$ .



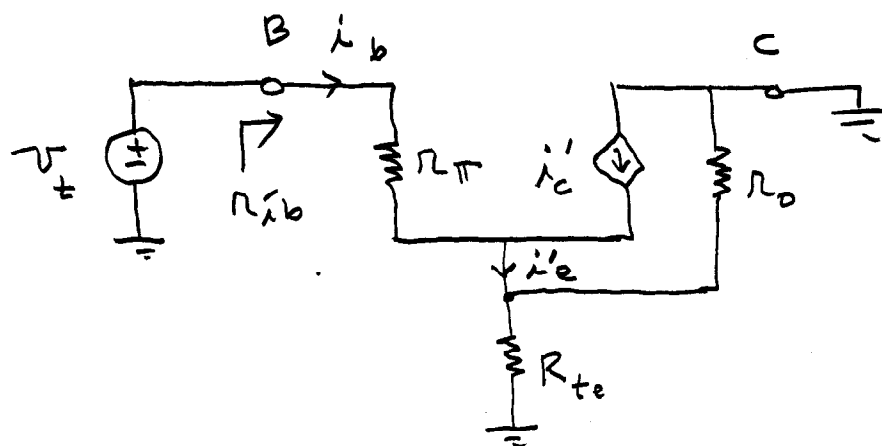Replace Q with the pi model and add a test source at the base.



$$R_{ib} = \frac{v_t}{i_b}$$

6/29/4 (16)

$$v_t = \hat{i}_b r_\pi + \hat{i}_e' (r_o \parallel R_{te})$$


$$= \hat{i}_b r_\pi + (1 + \beta) \hat{i}_b (r_o \parallel R_{te})$$

$$\Rightarrow r_{ib} = \frac{v_t}{\hat{i}_b} = r_\pi + (1 + \beta) (r_o \parallel R_{te})$$

The input resistance to the original circuit is

$$R_{in} = R_1 \parallel R_2 \parallel r_{ib}$$

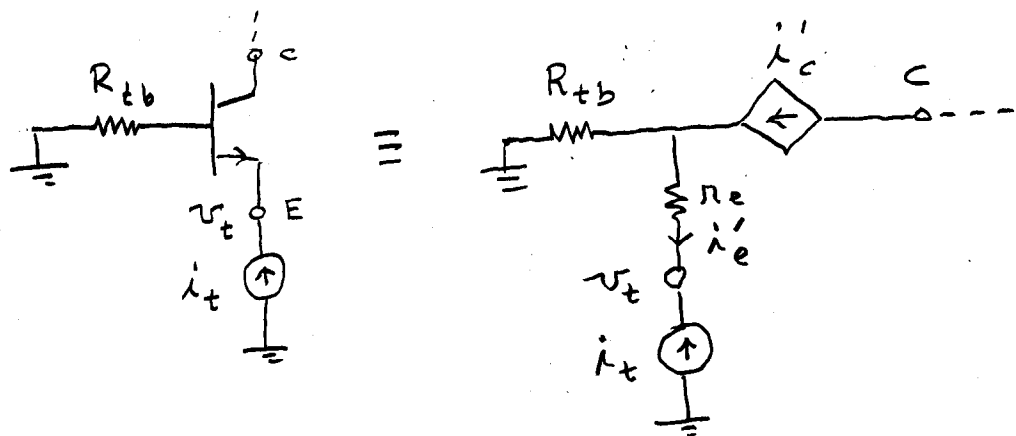To solve for  $r_{out}$ , we need the resistance seen looking up into the  $i_e'$  branch. We can use the T model and a test current source to solve for this. Set  $v_i = 0 \Rightarrow v_{tb} = 0$ .



6/29/4

(11)


$$v_t = i_t R_e + (i_t + i_c') R_{tb}$$

$$\text{But } i_c' = \alpha i_e' = -\alpha i_t$$

$$\Rightarrow v_t = i_t R_e + i_t (1-\alpha) R_{tb}$$

$$\text{Let } R_e' = \frac{v_t}{i_t} = R_e + (1-\alpha) R_{tb} = R_e + \frac{R_{tb}}{1+\beta}$$


The circuit for  $R_{out}$  is

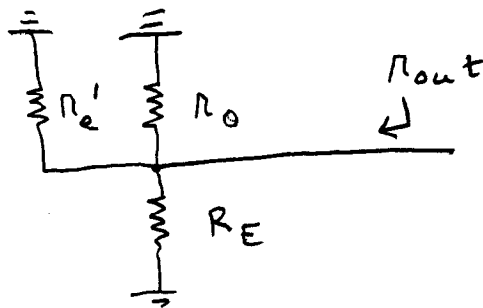

$$R_{out} = R_e' \parallel R_o \parallel R_E$$

6/29/4 (12)

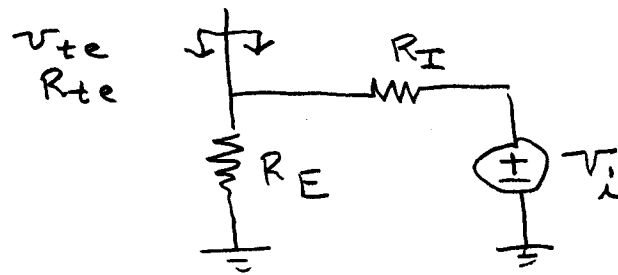We assume the Q point solution is known. For the ac analysis, we make a Thévenin equivalent looking out of the emitter.



$$v_{te} = v_i \frac{R_E}{R_I + R_E} \quad R_{te} = R_E \parallel R_I$$


In the ac circuit, neither end of  $r_o$  is grounded, so we omit it to obtain an approximate solution.

Either the pi or the T model can be used. We will use the T model.



6/29/4

13

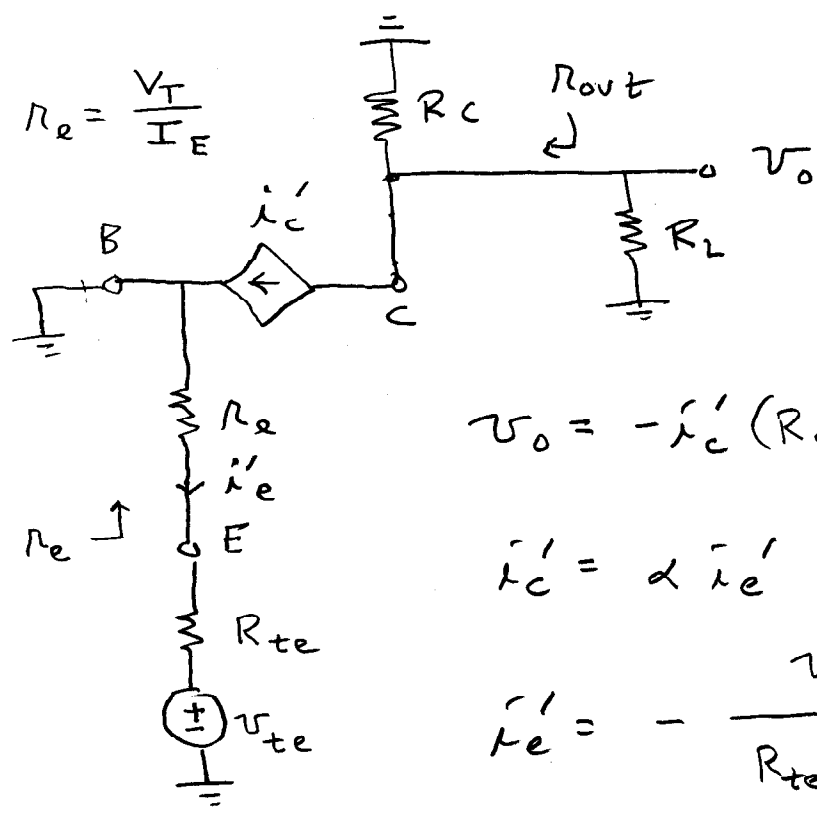

$$r_e = \frac{V_T}{I_E}$$

$$v_o = -i'_c (R_c \parallel R_L)$$

$$i'_c = \alpha i'_e$$

$$i'_e = - \frac{v_{te}}{R_{te} + r_e}$$

$$\Rightarrow v_o = + \alpha \frac{R_c \parallel R_L}{R_{te} + r_e} v_{te}$$


$$= + \alpha \frac{R_c \parallel R_L}{R_{te} + r_e} \frac{R_E}{R_I + R_E} v_i$$

$$R_{out} = R_c \parallel R_L$$

6/29/4

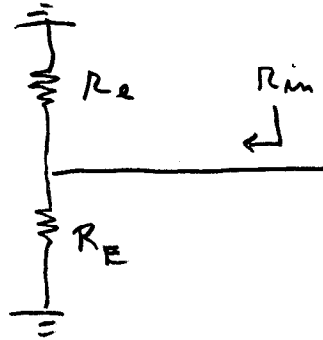(14)


The resistance seen looking up into the emitter node is  $r_e$ . Thus the equivalent circuit for  $R_{in}$  is




$$R_{in} = r_e \parallel R_E \quad r_e = \frac{V_T}{I_E}$$

6/30/4 (1)

# The CE-CC Amplifier

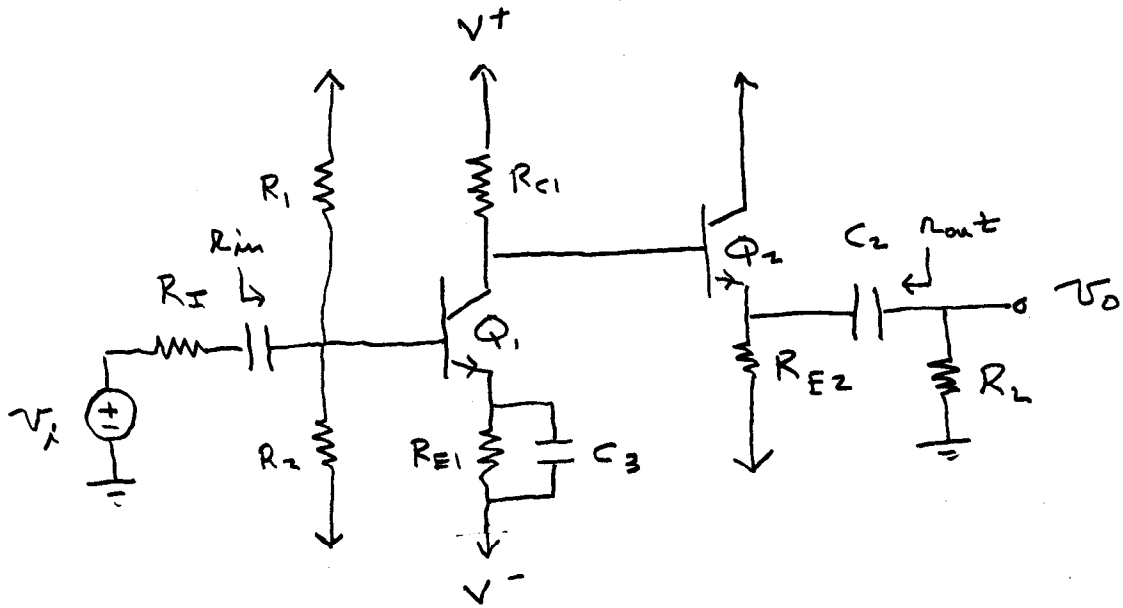

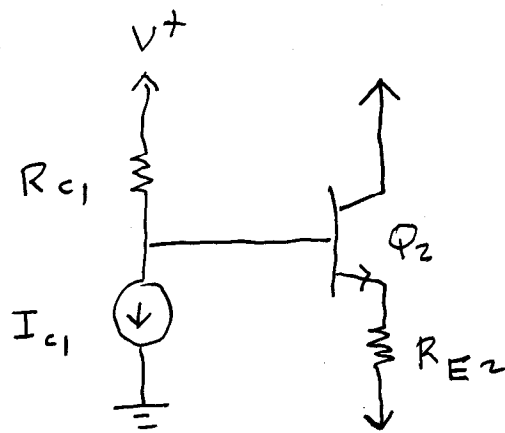
The dc bias solution for  $Q_1$  is the same as for the CE amp. The dc bias circuit for  $Q_2$  is



$$V_{BB2} = V^+ - I_{C1} R_{C1} \quad R_{BB2} = R_{C1}$$

Thus we can redraw the circuit to obtain

6/30/4 (2)

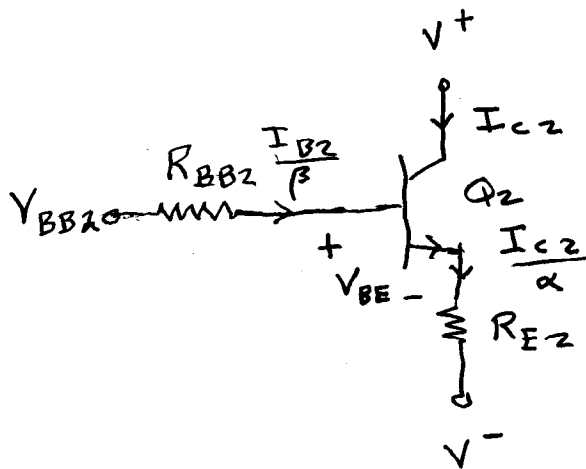

$$V_{BB2} - V^- = \frac{I_{C2}}{\beta} R_{BB2} + V_{BE} + \frac{I_{C2}}{\alpha} R_{E2}$$

$$\Rightarrow I_{C2} = \frac{V_{BB2} - V^- - V_{BE}}{\frac{R_{BB2}}{\beta} + \frac{R_{E2}}{\alpha}}$$

$$= \frac{V^+ - I_{C1} R_{C1} - V^- - V_{BE}}{\frac{R_{BB2}}{\beta} + \frac{R_{E2}}{\alpha}}$$

For  $Q_2$  to be in the active mode,  $V_{CB2}$  must be positive.

$$V_{CB2} = V_{C2} - V_{B2}$$

$$= V^+ - (V_{BE} + I_{E2} R_{E2} + V^-)$$


$$= V^+ - \left( V_{BE} + \frac{I_{C2}}{\alpha} R_{E2} + V^- \right)$$

6/30/4 (3)

The ac signal circuit is obtained by shorting all capacitors and setting  $V^+ = 0$  and  $V^- = 0$ . As with the CE amplifier, let

$$v_{tb1} = v_i \frac{R_1 \parallel R_2}{R_I + R_1 \parallel R_2} \quad R_{tb1} = R_I \parallel R_1 \parallel R_2$$

The ac signal circuit is

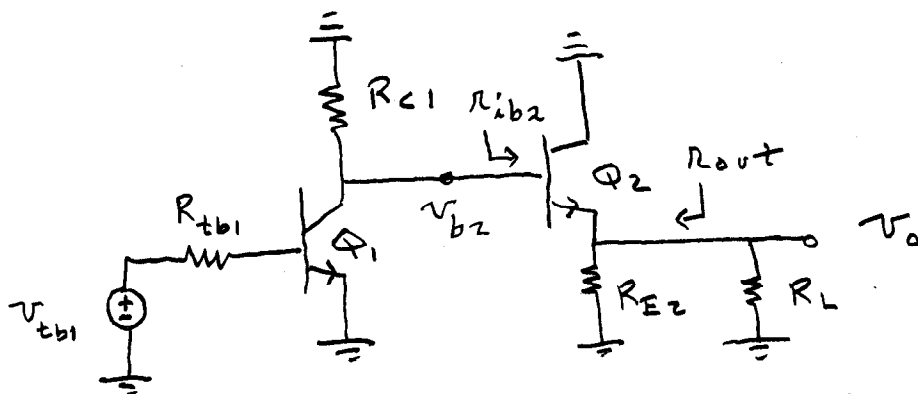

Note that  $r_{ib2}$  is the load resistor  $R_{L1}$  for  $Q_1$ . From our common-collector amplifier analysis, it is given by

$$r_{ib2} = r_{\pi 2} + (1 + \beta_2) \underbrace{(R_{o2} \parallel R_{E2} \parallel R_L)}_{R_{te2}}$$

6/30/4 (4)

Thus we can use our CE amplifier analysis to write

$$v_{b2} = -\beta_1 \frac{r_{o1} \parallel R_{c1} \parallel r_{ib2}}{R_{tb1} + R_{\pi 1}} v_{tb1}$$

Because there is no resistor between the  $v_{b2}$  node and the base of  $Q_2$ , it follows that

$$v_{tb2} = v_{b2} \quad R_{tb2} = 0$$

Thus we can use our CC amplifier analysis to write

$$v_o = \frac{r_{o2} \parallel R_{E2} \parallel R_L}{\frac{R_{\pi}}{1+\beta} + r_{o2} \parallel R_{E2} \parallel R_L} v_{b2}$$

The overall voltage gain is given by


$$\frac{v_o}{v_i} = \frac{v_{tb1}}{v_i} * \frac{v_{b2}}{v_{tb1}} * \frac{v_o}{v_{b2}}$$

where the 3 gain terms are found from the above analysis.


7/1/14 ①

The Thévenin Equivalent Circuit  
Seen Looking Into The  $i_e'$  Branch  
of the BJT Small-Signal Model

Consider the ac signal circuit

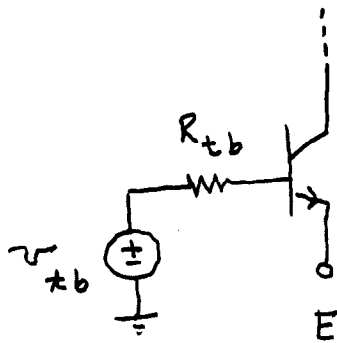


The T model is

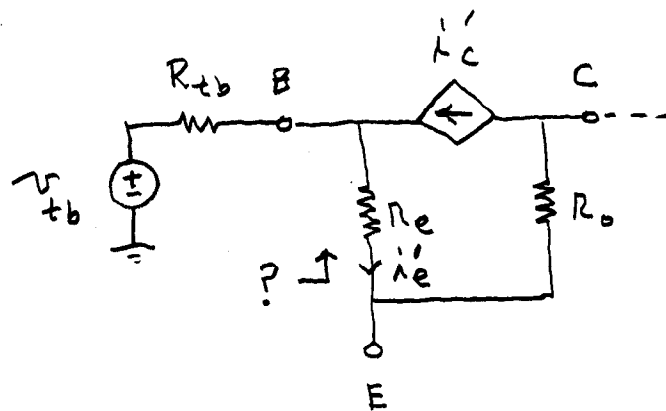

We wish to solve for the Thévenin  
equivalent circuit seen looking up  
into the  $i_e'$  branch, The part of  
the circuit which we need for this

7/1/4 (2)

is as follows

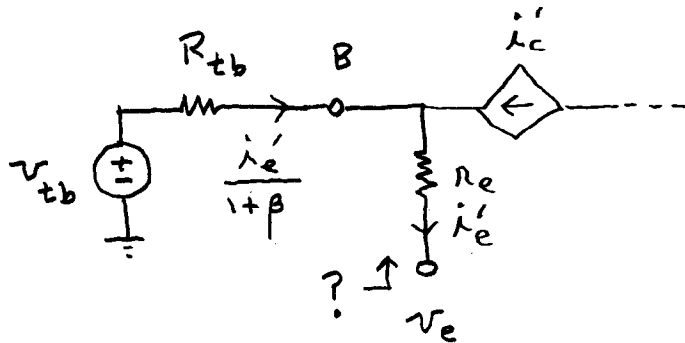

We can write

$$\begin{aligned} v_{tb} - v_e &= \frac{i'_e}{1+\beta} R_{tb} + i'_e R_e \\ &= i'_e \left( \frac{R_{tb}}{1+\beta} + R_e \right) \end{aligned}$$

Let us define  $R'_e$  as follows

$$R'_e = \frac{R_{tb}}{1+\beta} + R_e$$


$$\Rightarrow v_{tb} - v_e = i'_e R'_e$$

$$\Rightarrow v_e = v_{tb} - i'_e R'_e$$

The circuit which this equation applies to is



7/1/4 (3)

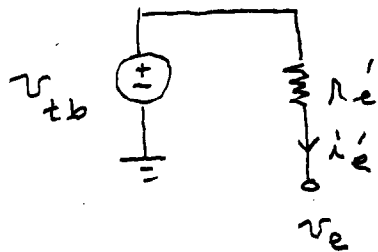


$$v_e' = v_{tb} - i_e' R_e'$$

$$R_e' = \frac{R_{tb}}{1+\beta} + R_e$$

This is the Thévenin equivalent circuit seen looking up into the  $i_e'$  branch.

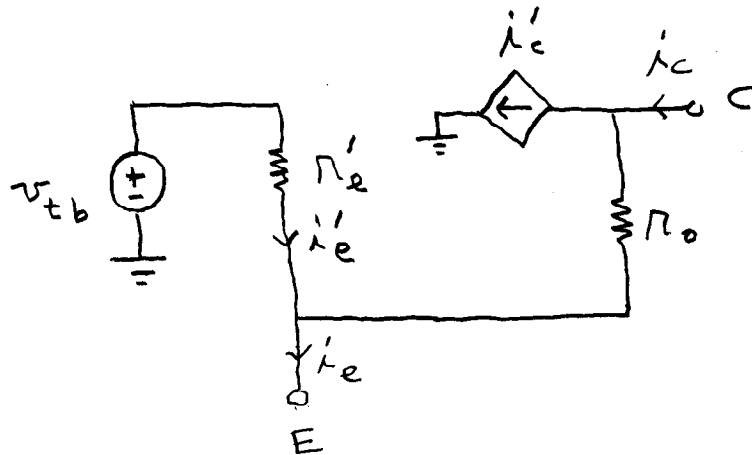We can now draw a simplified form of the T model as follows:



Note that the base node B has been absorbed. We use this model to solve the BJT differential amplifier.