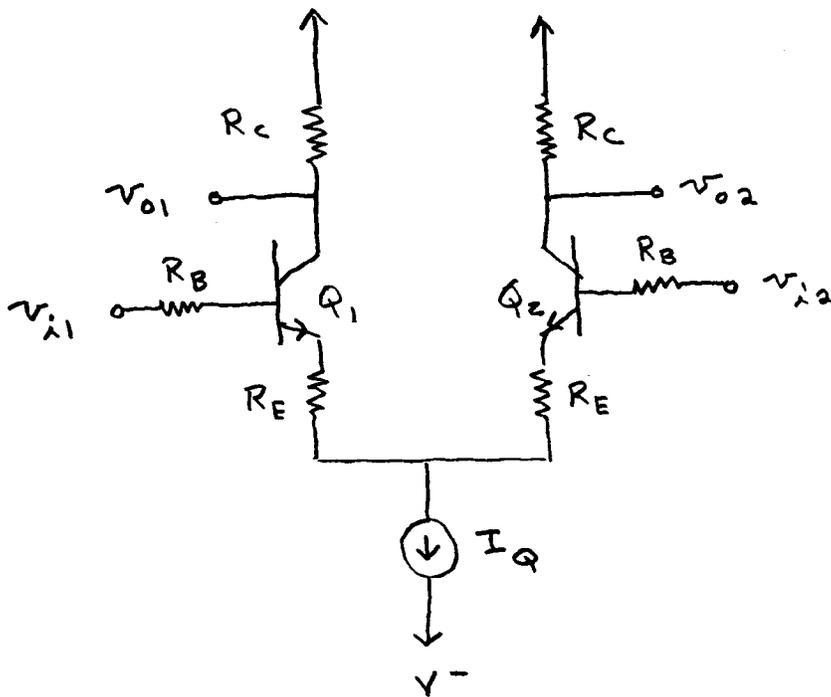


7/1/4

④

The BJT Differential Amplifier

 v^+ 

For the dc bias solution, set $v_{i1} = v_{i2} = 0$. If the BJTs are identical, I_Q splits equally between Q_1 and Q_2 .

$$\Rightarrow I_{E1} = I_{E2} = \frac{1}{2} I_Q$$


$$I_{C1} = I_{C2} = \frac{\alpha}{2} I_Q$$

7/1/4 (5)

For the BJT to be in the active mode, V_{CB} must be positive. It is given by

$$\begin{aligned} V_{CB} &= V_C - V_B \\ &= (V^+ - I_C R_C) - (-I_B R_B) \\ &= V^+ - \frac{\alpha}{2} I_Q R_C + \frac{I_Q}{1+\beta} R_B \end{aligned}$$

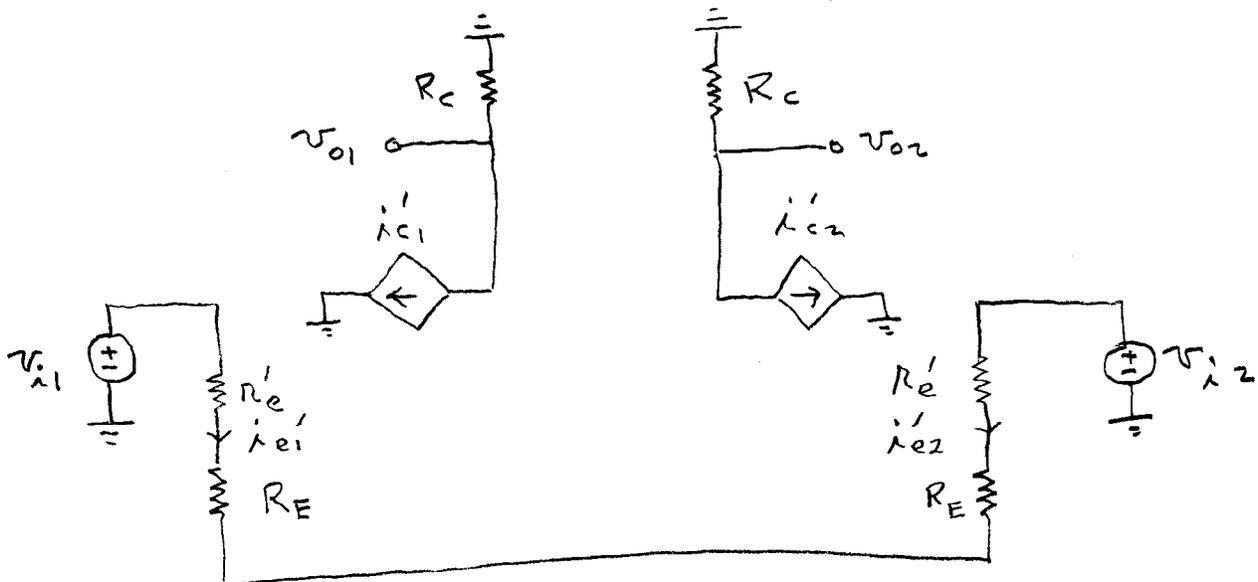For the ac small-signal analysis, we use the simplified T model. Because neither end of r_o is at signal ground, we omit it to obtain an approximate analysis. Set $V^+ = V^- = 0$ and $I_Q = 0$.



7/1/4 (6)

$$v_{o1} = -i_{c1}' R_c$$

$$v_{o2} = -i_{c2}' R_c$$

$$i_{c1}' = \alpha i_{e1}'$$

$$i_{c2}' = \alpha i_{e2}'$$

$$i_{e1}' = \frac{v_{i1} - v_{i2}}{2(R_e' + R_E)}$$

$$i_{e2}' = -i_{e1}'$$

$$\Rightarrow v_{o1} = -\frac{\alpha R_c}{2(R_e' + R_E)} (v_{i1} - v_{i2})$$

$$v_{o2} = -v_{o1}$$

$$R_e' = \frac{R_B}{1+\beta} + R_e = \frac{R_B}{1+\beta} + \frac{V_T}{I_E}$$

Thus we see that the output voltages are proportional to the difference between the two input voltages.


The differential output voltage is given by

$$v_o = v_{o1} - v_{o2}$$

$$= -\frac{\alpha R_c}{R_e' + R_E} (v_{i1} - v_{i2})$$

7/6/4 ①

Example

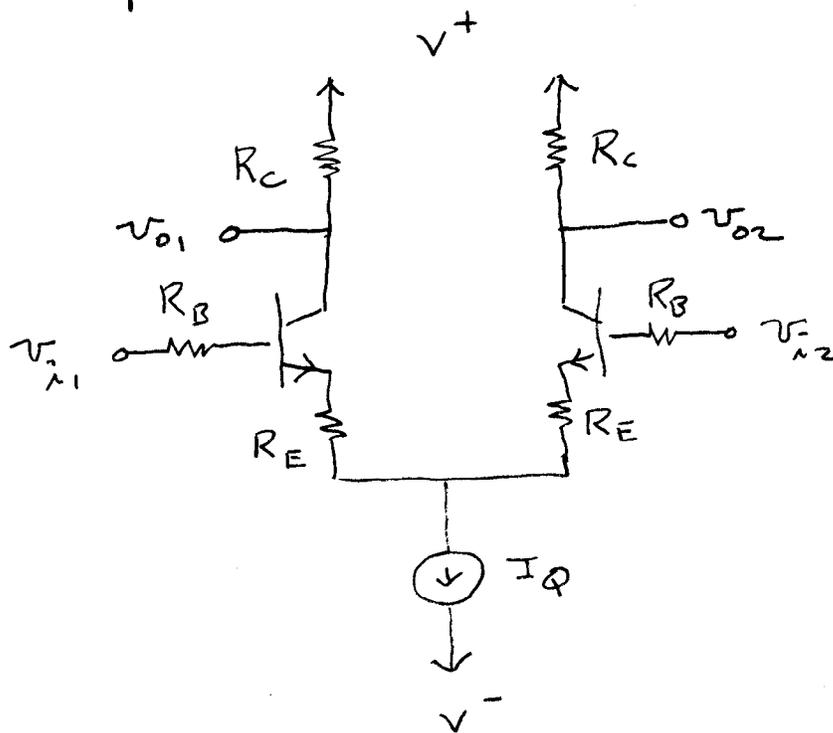

$$\begin{aligned}
 V^+ &= +15\text{V} & V^- &= -15\text{V} & I_Q &= 2\text{mA} \\
 R_C &= 7.5\text{k}\Omega & R_B &= 100\Omega & R_E &= 50\Omega \\
 \beta &= 99 & \alpha &= 0.99 & V_T &= 25\text{mV}
 \end{aligned}$$

$$I_{E1} = I_{E2} = \frac{1}{2} I_Q = 1\text{mA}$$

$$r_e = \frac{V_T}{I_E} = 25\Omega$$

$$r_e' = \frac{R_B}{1+\beta} + r_e = 26\Omega$$

7/6/4 (2)

$$\begin{aligned}v_{o1} &= -\frac{\alpha R_c}{2(R_c' + R_E)} (v_{i1} - v_{i2}) \\ &= -48.85 (v_{i1} - v_{i2})\end{aligned}$$

$$v_{o2} = -v_{o1} = +48.85 (v_{i1} - v_{i2})$$

Differential Output

$$v_o = v_{o1} - v_{o2} = -97.70 (v_{i1} - v_{i2})$$

Method of Symmetrical Components

Another method of analyzing the diff amp is to use superposition of differential and common-mode components.

$$\text{Let } v_{i1} = \frac{1}{2} v_{id} + v_{icm}$$

$$v_{i2} = -\frac{1}{2} v_{id} + v_{icm}$$


7/6/4 (3)

where v_{id} is the differential input signal and v_{icm} is the common-mode input signal. These are given by

$$v_{id} = v_{i1} - v_{i2}$$

$$v_{icm} = \frac{1}{2} (v_{i1} + v_{i2})$$

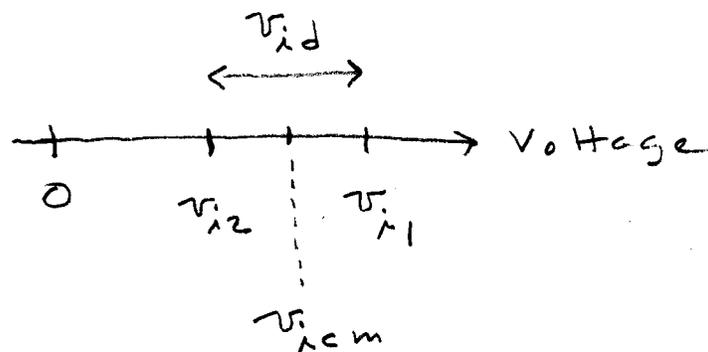Graphical interpretation for $v_{i1} > v_{i2}$




We can use superposition of v_{id} and v_{icm} to solve for v_{o1} and v_{o2} .

7/6/4 (4)


First let $v_{icm} = 0$

$$\Rightarrow v_{i1} = \frac{1}{2} v_{id} \quad v_{i2} = -\frac{1}{2} v_{id}$$

The ac signal circuit is

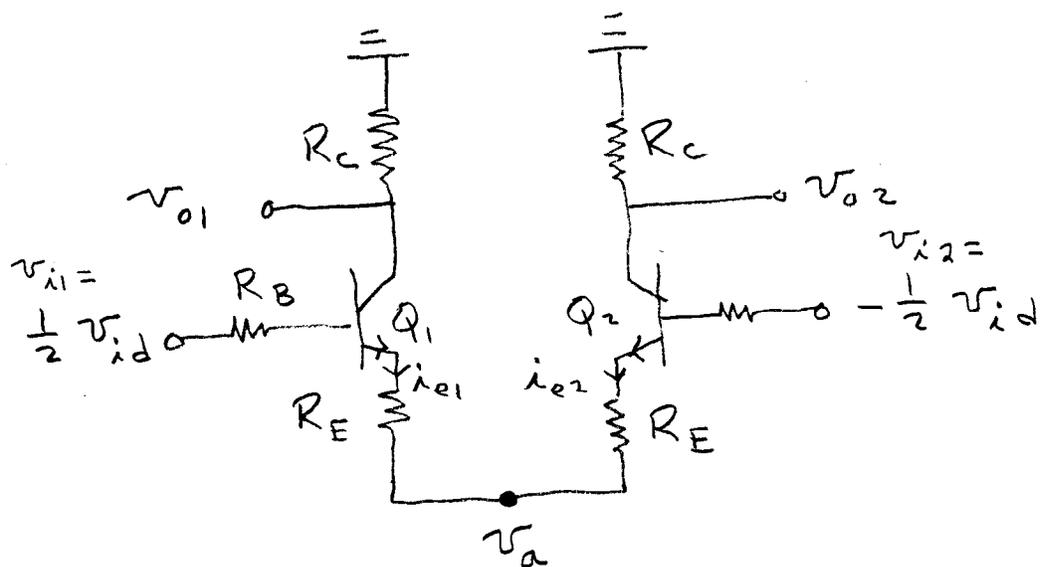


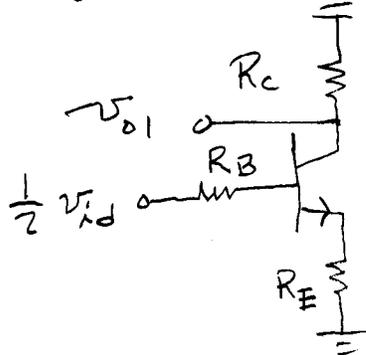v_{i1} forces v_a to increase while v_{i2} forces v_a to decrease. The net effect is $v_a = 0$. Thus we obtain the equivalent circuit.



7/6/4 (5)

The simplified T model is

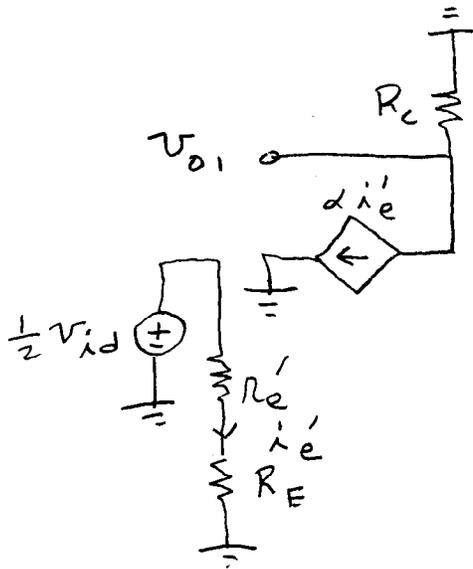

$$i_e' = \frac{1}{2} v_{id} \frac{1}{r_e' + R_E}$$

$$v_{o1} = -\alpha i_e' R_C$$

$$= -\frac{\alpha R_C}{2(r_e' + R_E)} (v_{i1} - v_{i2})$$

This is the same answer.

By symmetry $v_{o1} = -v_{o2}$

Now, let $v_{i1} = v_{i2} = v_{icm}$. By

symmetry $i_{e1} = i_{e2}$. But by

KCL $i_{e1} + i_{e2} = 0 \Rightarrow i_{e1} = i_{e2} = 0$. There

is no output voltage due to v_{icm} .

Now suppose $R_E = 0$. Because $v_a = 0$ for the differential inputs, one side of R_o is grounded for both Q_1 and Q_2 . In this case, R_o combines in parallel with R_C and we have

7/6/4 (6)


$$\begin{aligned}
 v_{o1} &= - \frac{\alpha (r_o \parallel R_c)}{r_e'} (v_{i1} - v_{i2}) \\
 &= - \frac{\alpha (r_o \parallel R_c)}{\frac{R_B}{1+\beta} + r_e} (v_{i1} - v_{i2})
 \end{aligned}$$

$$v_{o2} = -v_{o1}$$

These are the same solutions obtained from the original circuit. The common-mode solution is zero because there is no resistor from the v_a node to ground. If such a resistor is present, the differential solution does not change but the common-mode solution is no longer zero.

7/7/4 ①

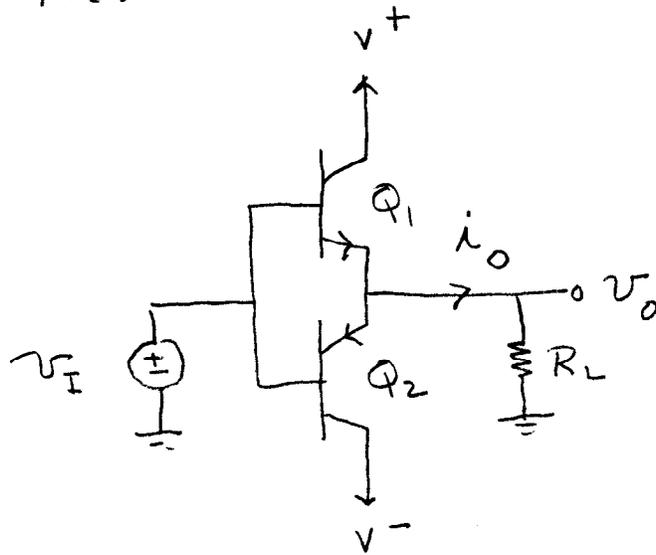The Complementary Common-Collector Amplifier




This stage is commonly used as the output stage in an op amp. It acts as a buffer stage. Q_1 supplies positive i_O and Q_2 supplies negative i_O .

For $-V_{\gamma} < v_I < +V_{\gamma}$, both Q_1 and Q_2 are cut off. In this case $v_O = 0$. For $v_I > V_{\gamma}$, Q_1 cuts on and Q_2 remains off. The output voltage is given by

$$v_O = v_I - V_{BE1}$$


7/7/4 (2)

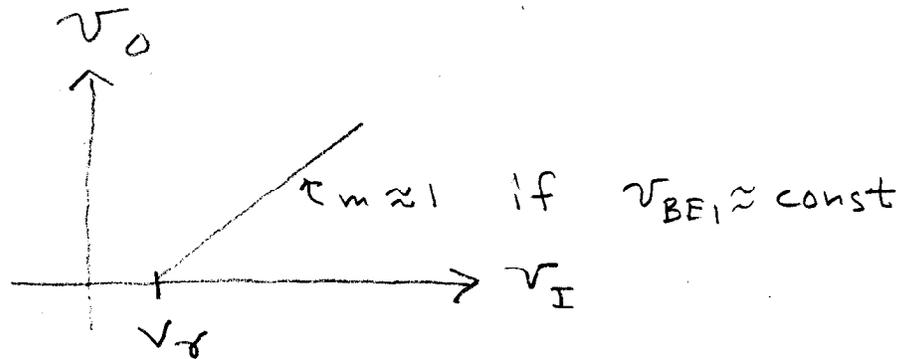If we assume $v_{BE1} \approx \text{constant}$,
 the plot of v_o versus v_I
 is




Now, for $v_I < -v_\gamma$, Q_2 cuts on
 and Q_1 remains off. In this
 case

$$v_o = v_I + v_{EB2}$$

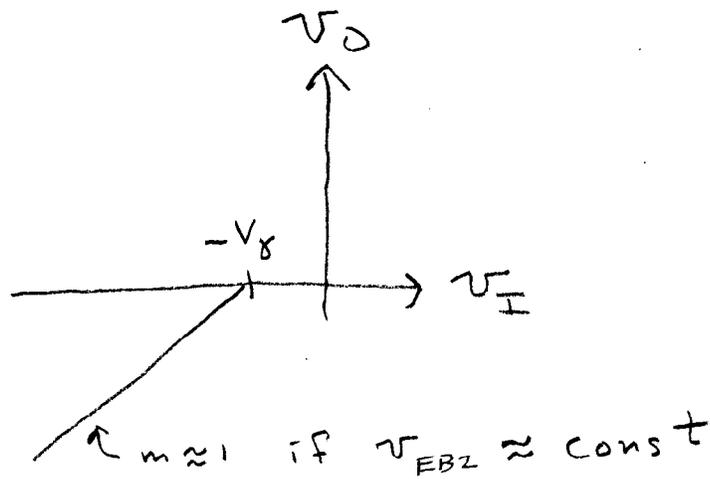


7/7/4 (3)

Putting the two curves together,
we get

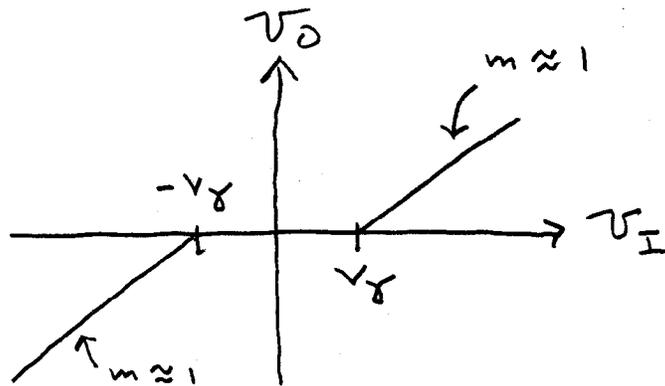


Now, suppose v_i is a sine wave.

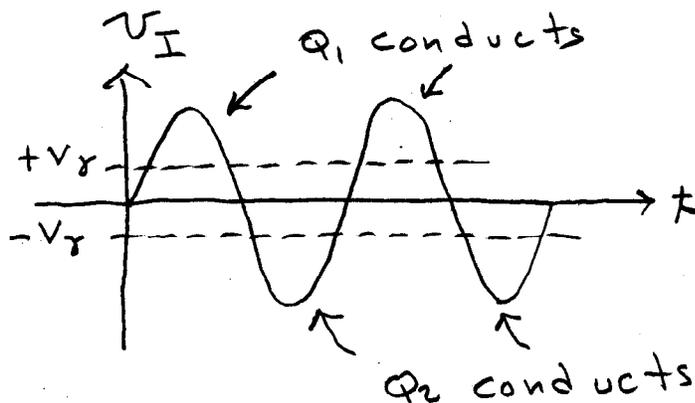


The output voltage appears as follows:

7/7/4 (4)

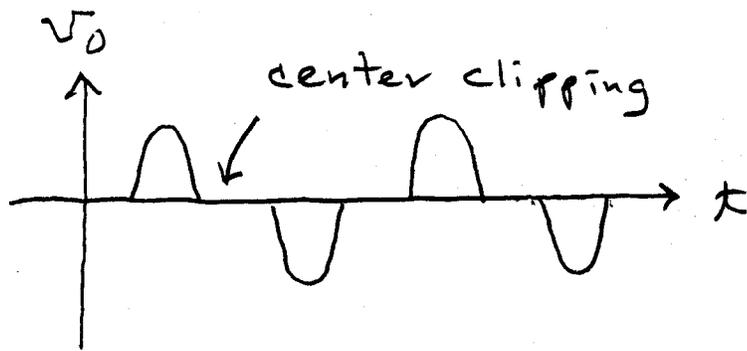


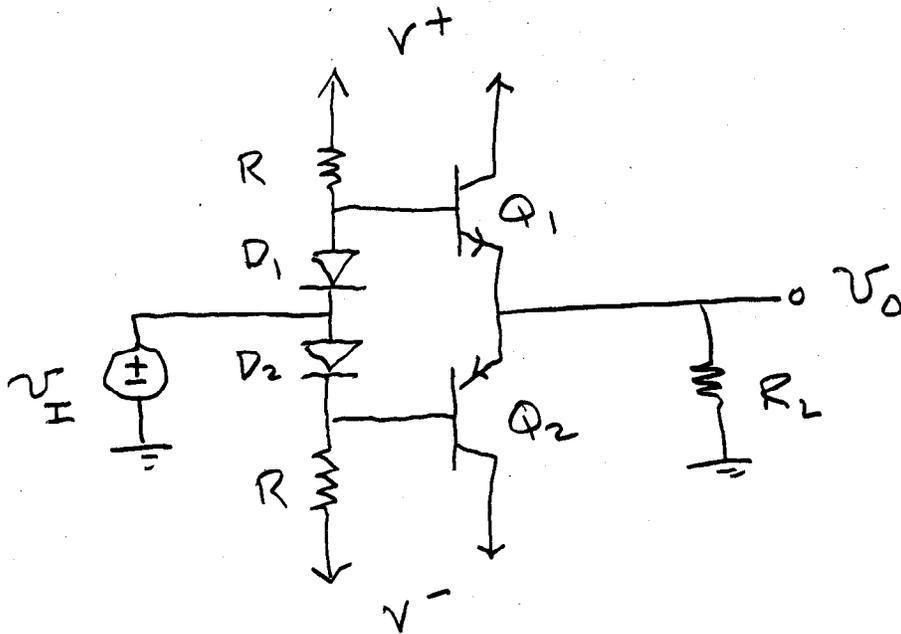To minimize the center clipping, Q_1 and Q_2 must be biased on when $v_I = 0$. A possible circuit is



7/7/4 (5)

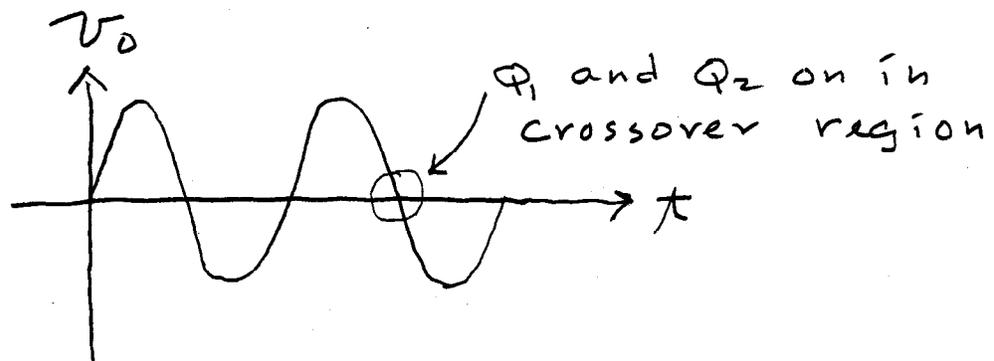The resistors supply current to D_1 and D_2 . The voltages across the diodes turn Q_1 and Q_2 on when $v_I = 0$. Thus the graph for v_o becomes



The ac small signal gain of the circuit is less than but close to unity. It is often approximated by unity.