

ECE 3040 Microelectronic Circuits Quiz 5


June 16, 2004

Professor Leach

Name _____

Instructions. Print your name in the space above. The quiz is closed-book and closed-notes. The quiz consists of 2 problems. **Honor Code Statement:** *I have neither given nor received help on this quiz.*
 Initials _____

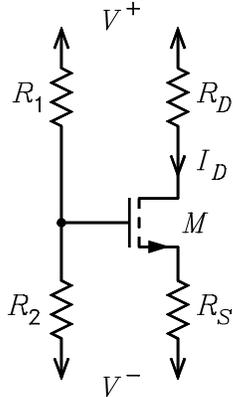- The MOSFET has the parameters $K = 0.0005 \text{ A/V}$ and $V_{TH} = 1.75 \text{ V}$. It is given that $V^+ = +18 \text{ V}$, $V^- = -18 \text{ V}$, $R_1 = 3 \text{ M}\Omega$, $R_S = 2 \text{ k}\Omega$, and $i_D = K (v_{GS} - V_{TH})^2$.
 - Solve for R_2 such that $I_D = 1.5 \text{ mA}$.
 - What is the maximum value that R_D can have for the MOSFET to remain in the saturation state?



Answers:

$$V_{GS} = \sqrt{\frac{I_D}{K}} + V_{TH} = 3.482 \text{ V} \quad V_G = V_{GS} + I_D R_S + V^- = -11.518 \text{ V}$$

$$I_{R_2} = I_{R_1} = \frac{V^+ - V_G}{R_1} = 9.839 \mu\text{A} \quad R_2 = \frac{V_G - V^-}{I_{R_2}} = 658.8 \text{ k}\Omega$$

$$V_{DS} = (V^+ - I_D R_D) - (V^- + I_D R_S) = 33 - I_D R_D \geq V_{GS} - V_{TH} = \sqrt{\frac{I_D}{K}} = 1.732 \text{ V}$$

$$\Rightarrow R_D \leq \frac{33 - 1.732}{I_D} = 20.85 \text{ k}\Omega$$

- The MOSFET drain current is given by the equation $i_D = K_0 (1 + \lambda v_{DS}) (v_{GS} - V_{TH})^2$. Describe how this equation is used to solve for the parameters g_m and r_0 in the hybrid-pi model. Assume the Q-point values I_D , V_{GS} , and V_{DS} . You should use graphs and equations, as appropriate, in your description. Label on the graphs how the parameters are defined.

Answers: g_m is the slope of the i_D versus v_{GS} curve at the Q point with v_{DS} held constant. r_0 is the reciprocal of the slope of the i_D versus v_{DS} curve at the Q point with v_{GS} held constant.