

ECE 3040 Microelectronic Circuits Quiz 7


June 30, 2004

Professor Leach

Name _____

Instructions. Print your name in the space above. The quiz is closed-book and closed-notes. The quiz consists of 2 problems. **Honor Code Statement:** *I have neither given nor received help on this quiz.* Initials _____

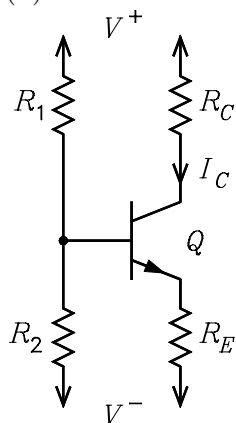1. The BJT has the parameters $\beta = 199$ and $V_{BE} = 0.65\text{ V}$. It is given that $V^+ = +15\text{ V}$, $V^- = -15\text{ V}$, $R_1 = 300\text{ k}\Omega$, and $R_2 = 33\text{ k}\Omega$.
 - (a) Solve for R_E such that $I_C = 2\text{ mA}$.
 - (b) What is the maximum value that R_C can have for the BJT to remain in the active mode?



Answers:

$$V_{BB} = \frac{V^+ R_2 + V^- R_1}{R_1 + R_2} = -12.027\text{ V} \quad R_{BB} = R_1 \parallel R_2 = 29.73\text{ k}\Omega$$

$$V_{BB} - V^- = \frac{I_C}{\beta} R_{BB} + V_{BE} + \frac{I_C}{\alpha} R_E \implies R_E = \alpha \left(\frac{V_{BB} - V^- - V_{BE}}{I_C} - \frac{R_{BB}}{\beta} \right) = 1007\ \Omega$$

$$\begin{aligned} V_{CB} &= (V^+ - I_C R_C) - \left(V_{BE} + \frac{I_C}{\alpha} R_E + V^- \right) > 0 \\ \implies R_C &= \frac{1}{I_C} \left[V^+ - \left(V_{BE} + \frac{I_C}{\alpha} R_E + V^- \right) \right] < 13.66\text{ k}\Omega \end{aligned}$$

2. The BJT active mode currents are given by the equations $i_C = I_{S0} (1 + v_{CE}/V_A) \exp(v_{BE}/V_T)$, $i_B = i_C/\beta$, and $\beta = \beta_0 (1 + v_{CE}/V_A)$. Describe how these equations are used to plot the transfer, output, and input characteristic curves. Show how the parameters g_m , r_0 , and r_π in the hybrid-pi model are defined on the curves. Assume the Q-point values I_C , V_{CE} , and V_{BE} . **Answers:** The plots of the characteristic curves are covered in the class notes. At the Q point, g_m is the slope of the transfer characteristic curve, r_0 is the reciprocal of the slope of the output characteristic curve, and r_π is the reciprocal of the slope of the input characteristic curve.