

## ECE 3050 Analog Electronics Quiz 4

September 16, 2009

Professor Leach      Last Name: \_\_\_\_\_ First Name: \_\_\_\_\_

**Instructions. Print** your name in the spaces above. Place a box around any answer. **Honor Code Statement:**

*I have neither given nor received help on this quiz.* Initials \_\_\_\_\_


Given equations:  $i'_c = g_m v_\pi = \alpha i'_e = \beta i_b$ ,  $g_m = I_C/V_T$ ,  $r_\pi = V_T/I_B$ , and  $r_e = V_T/I_E$ , and  $I_C = \alpha I_E = \beta I_B$ .

1 of 2. The signal circuit of a two-stage BJT amplifier is shown. It is given that  $I_{E1} = 1.25 \text{ mA}$ ,  $I_{E2} = 2.5 \text{ mA}$ ,  $\alpha = 0.99$ ,  $\beta = 99$ ,  $r_x = 0 \Omega$ ,  $r_0 = \infty$ ,  $V_T = 0.025 \text{ V}$ ,  $R_S = 50 \Omega$ ,  $R_C = 2.4 \text{ k}\Omega$ , and  $R_E = 300 \Omega$ .

(a) In terms of CE, CB, and CC, how would you describe this circuit?

(b) Solve for  $r_{in}$ .

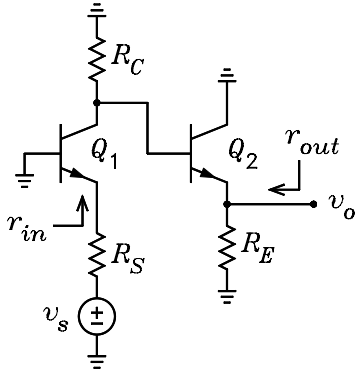(c) Denote the Thévenin equivalent circuit seen looking out of the base of  $Q_2$  by  $v_{tb2}$  and  $R_{tb2}$ . With  $Q_2$  erased, solve for  $v_{tb2}/v_s$  and  $R_{tb2}$ . Use any one of the small-signal circuits covered in class.



Let  $v_s := 1$       The value of  $v_o$  is the voltage gain.

$$r_{e1} := \frac{V_T}{I_{E1}} \quad r_{e1} = 20 \quad r_{e2} := \frac{V_T}{I_{E2}} \quad r_{e2} = 10 \quad r'_{e1} := r_{e1}$$

$$i'_{e1} := \frac{-v_s}{R_S + r'_{e1}} \quad i'_{e1} = -0.014 \quad v_{tb2} := -\alpha \cdot i'_{e1} \cdot R_C \quad v_{tb2} = 33.943$$

$$r_{in} := r'_{e1} \quad r_{in} = 20$$

2 of 2. Replace the circuit seen looking out of the base of  $Q_2$  with a voltage source labeled  $v_{tb2}$  in series with the resistance  $R_{tb2}$  found in problem 1.

(a) Solve for  $v_o/v_{tb2}$  and  $r_{out}$ . Use any one of the small-signal circuits covered in class. Note – you don't need a number for  $v_{tb2}$ , but you do need a number for  $R_{tb2}$ . Even if you don't know how to work problem 1, you should be able to tell the value of  $R_{tb2}$  by inspection of the circuit diagram given.

(b) Put the answers for problems 1 and 2 together to solve for  $v_o/v_s$ .

$$R_{tb2} := R_C \quad r'_{e2} := \frac{R_{tb2}}{1 + \beta} + r_{e2} \quad r'_{e2} = 34 \quad i'_{e2} := \frac{v_{tb2}}{r'_{e2} + R_E} \quad i'_{e2} = 0.102$$

$$v_{o1} := i'_{e2} \cdot R_E \quad v_{o1} = 30.488 \quad \text{Solution 1}$$

$$v_{o2} := v_{tb2} \cdot \frac{R_E}{r'_{e2} + R_E} \quad v_{o2} = 30.488 \quad \text{Solution 2}$$

$$r_{out} := R_{p2}(R_E, r'_{e2}) \quad r_{out} = 30.539$$