

ECE 3050 Analog Electronics Quiz 8

October 14, 2009

Professor Leach

Name _____

Instructions. Print your name in the space above. Place a box around your answers. Points will be subtracted if you do not express each numerical answer as a decimal number and if you do not put a box around answers. **Honor Code Statement:** *I have neither given nor received help on this quiz.* Initials _____

- (a) Draw the circuit diagram of an npn Wilson current mirror and explain its principle advantage over the other current mirrors. – The circuit diagram is in the class notes. The advantage is that it has a higher output resistance and, therefore, looks more like an ideal current source.

(b) In typical applications, why must a two resistor voltage divider be connected between a signal source and the input terminal to a transconductance op amp? – The input diff amp overloads at about 50 mV. When applying signals greater than this value, the input must be attenuated with a voltage divider.

(c) How is the gain of the transconductance op amp, i.e. current output divided by voltage input, varied in a circuit? – By varying the current I_{ABC} .

(d) Draw an op amp circuit that can be used to convert the current output of the transconductance op amp into a voltage while presenting a virtual ground load on the transconductance op amp. Give the equation for the voltage output of the circuit as a function of the current output of the transconductance op amp. – This is in the class notes.
- (a) Assume all current mirrors are perfect and neglect the Early effect. Adjacent to all unlabeled current arrows, label the current in terms of i_{c1} and solve for $i_{o(sc)}$ in terms of i_{c1} . – This is in the class notes. In addition, the notes give the dc currents in terms of I_{ABC} . It was optional on the quiz to include them because they cancel at $i_{o(sc)}$.

(b) If the Early effect is neglected, what is $i_{o(sc)}$ in terms of v_{i1} and v_{i2} ?

$$i_{o(sc)} = \frac{v_{i1} - v_{i2}}{2r_e} \text{ or } \frac{g_m}{2} (v_{i1} - v_{i2}) \quad r_e = \frac{2V_T}{I_{ABC}} \quad g_m = \frac{I_{ABC}}{2V_T}$$

