

ECE 3050 Analog Electronics Quiz 10

October 28, 2009

Professor Leach

Name _____

Instructions. Print your name in the space above. Place a box around your answers. Points will be subtracted if you do not express each numerical answer as a decimal number and if you do not put a box around answers. **Honor Code Statement:** *I have neither given nor received help on this quiz.* Initials _____

1. The figure shows a common-drain amplifier with body effect. It is given that $r_0 = 50 \text{ k}\Omega$ and $g_m = 2 \text{ mA/V}$ for each MOSFET. For M_1 , it is given that $g_{mb} = 0.5 \text{ mA/V}$. Reference equations: $r_s = g_m^{-1}$, $r_{sb} = g_{mb}^{-1}$, $g_{mb} = \chi g_m$, $r'_s = r_s / (1 + \chi)$
- (a) Solve for the small-signal Norton current $i_{o(sc)}$ as a function of the small-signal input voltage v_i .


$$i_{o(sc)} = \frac{v_i}{\frac{1 + \chi}{r'_s}} = g_m v_i = 0.002 v_i = \frac{v_i}{500}$$

- (b) Solve for the output resistance r_{out} .

$$r_{out} = r_{o1} \parallel r'_{s1} \parallel r_{o2} = 394 \Omega$$

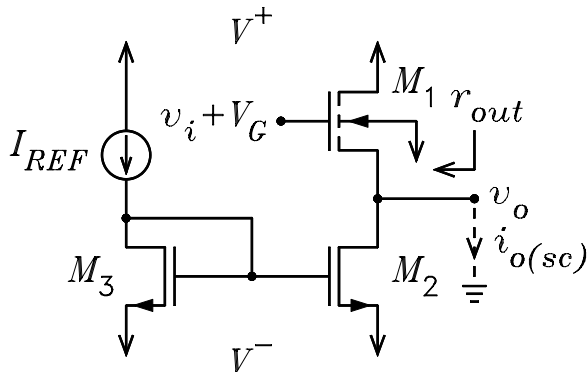- (c) A load resistor $R_L = 5 \text{ k}\Omega$ is connected from the output node to ac signal ground. Use the results from the preceding parts to solve for the small-signal output voltage v_o as a function of the small-signal input voltage v_i . Draw and label any circuits you use to solve for v_o .

$$v_o = i_{o(sc)} r_{out} \parallel R_L = 0.73 v_i$$



2. It is given that $v_i = 2\text{ V}$, $R_1 = 10\text{ k}\Omega$, $R_2 = 20\text{ k}\Omega$, $R_3 = 6\text{ k}\Omega$, and $R_4 = 4\text{ k}\Omega$.
 (a) Solve for the current i . Hint: write a single loop equation through the virtual short circuit.

$$i = \frac{v_i}{R_1 + R_3} = \frac{1}{8}\text{ mA} = 0.125\text{ mA}$$

- (b) Use the results of the preceding part to solve for v_o and the voltage at each of the other 4 nodes in the circuit.

$$v_o - i(R_2 + R_4) = 3\text{ V}$$

$$v_+ = v_- = -iR_4 = -0.5\text{ V}$$

$$v_{R_3} = -i(R_3 + R_4) = -1.25\text{ V}$$

$$v_{R_1} = v_{R_3} + v_i = 0.75\text{ V}$$

