

ECE 3050 Analog Electronics Quiz 13

November 18, 2009

Professor Leach


Name _____

Instructions. Print your name in the space above. Place a box around your answers. **Honor Code Statement:** *I have neither given nor received help on this quiz.* Initials _____

- 1 of 2. (a) What is the expression for the voltage gain V_o/V_i at very low frequencies? $V_o/V_i = -(R_2 + R_3)/R_1$
 (b) What is the expression for the voltage gain V_o/V_i at very high frequencies? $V_o/V_i = -R_3/R_1$
 (c) Solve for the transfer function $T(s) = V_o/V_i$. Use the two-terminal impedance theorem to write

$$T(s) = -\frac{R_2 + R_3}{R_1} \frac{1 + R_2 \parallel R_3 C s}{1 + R_2 C s}$$

- (d) What is the expression for the pole frequency of $T(s)$ in rad/s? $(R_2 C)^{-1}$
 (e) What is the expression for the zero frequency of $T(s)$ in rad/s? $[(R_2 \parallel R_3) C]^{-1}$
 (f) Sketch and label the straight line Bode magnitude plot for $|T(j\omega)|$. Low pass shelving Bode plot.

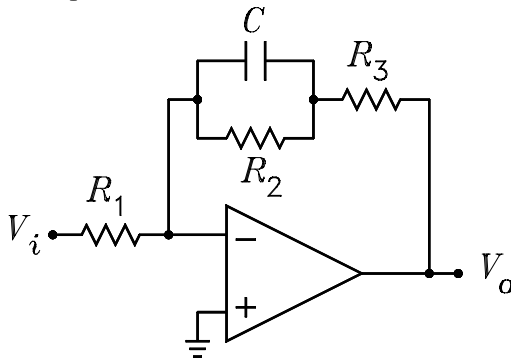

- 2 of 2. (a) What is the expression for the voltage gain V_o/V_i at very low frequencies? $1 + R_3/R_1$
 (b) What is the expression for the voltage gain V_o/V_i at very high frequencies? $1 + (R_2 \parallel R_3)/R_1$
 (c) Solve for the transfer function $T(s) = V_o/V_i$.

$$\frac{V_o}{V_i} = \left(1 + \frac{R_3}{R_1}\right) \frac{1 + (R_2 + R_1 \parallel R_3) C s}{1 + (R_2 + R_3) C s}$$

- (d) What is the expression for the pole frequency of $T(s)$ in rad/s? $(R_2 + R_3)C - 1$
 (e) What is the expression for the zero frequency of $T(s)$ in rad/s? $[(R_2 + R_1 \parallel R_3) C]^{-1}$
 (f) Sketch and label the straight line Bode magnitude plot for $|T(j\omega)|$. Low-pass shelving Bode plot.

