
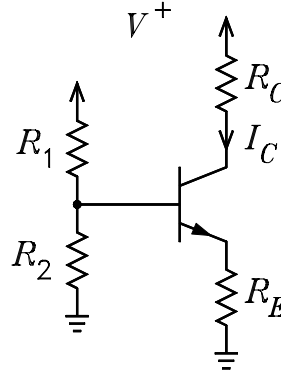


ECE3050 Homework Set 3

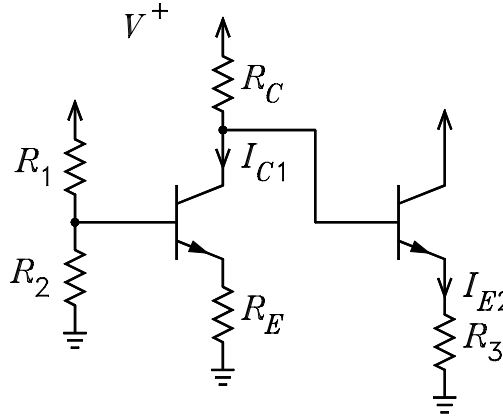1. (a) Write the bias equation and solve for  $I_C$  and  $V_{CB}$  for the values  $V^+ = 18\text{ V}$ ,  $R_E = 1\text{ k}\Omega$ ,  $R_1 = 130\text{ k}\Omega$ ,  $R_2 = 36\text{ k}\Omega$ ,  $R_C = 2.4\text{ k}\Omega$ ,  $V_{BE} = 0.7\text{ V}$ , and  $\beta = 99$ . (b) Is the BJT biased in the active mode? [ $I_C = 2.474\text{ mA}$ ,  $V_{CB} = 8.863\text{ V}$ ]



2. Add a second npn transistor to the circuit of problem 1 as shown below. (a) Show that  $I_{C1}$  does not change. (b) Show that  $V_{BB2} = V^+ - I_{C1}R_C$  and  $R_{BB2} = R_C$ . (c) For  $R_3 = 1\text{ k}\Omega$ , and the same  $V_{BE}$  and  $\beta$  as in problem 1, write the bias equation for the second transistor and solve for  $I_{E2}$ . (d) Solve for  $V_{CB}$  for both transistors and verify they are in the active mode. [ $I_{E2} = 11.10\text{ mA}$ ,  $V_{CB2} = 6.204\text{ V}$ ,  $V_{CB1} = 8.597\text{ V}$ ]



3. (a) Show that

$$V_{BB} = V^+ \frac{R_2}{R_1 + R_2 + R_C} - I_C \frac{R_C}{R_C + R_1 + R_2} \times R_2 \quad R_{BB} = (R_1 + R_C) \parallel R_2$$

$$V_{CC} = V^+ \frac{R_1 + R_2}{R_C + R_1 + R_2} - I_B \frac{R_2}{R_C + R_1 + R_2} \times R_C \quad R_{CC} = R_C \parallel (R_1 + R_2)$$

- (b) For  $\beta = 99$  and  $\beta = \infty$  and  $R_1 = 10\text{ k}\Omega$ ,  $R_2 = 47\text{ k}\Omega$ ,  $R_C = 1.5\text{ k}\Omega$ ,  $R_E = 2\text{ k}\Omega$ ,  $V_{BE} = 0.7\text{ V}$ , and  $V^+ = 9\text{ V}$ , write the bias equation and solve for  $I_C$  and  $V_{CB}$ . Verify that the BJT is biased in the active mode. [ $\beta = 99$ :  $I_C = 1.968\text{ mA}$  and  $V_{CB} = 1.194\text{ V}$ ,  $\beta = \infty$ :  $I_C = 2.025\text{ mA}$ ,  $V_{CB} = 1.019\text{ V}$ ]

