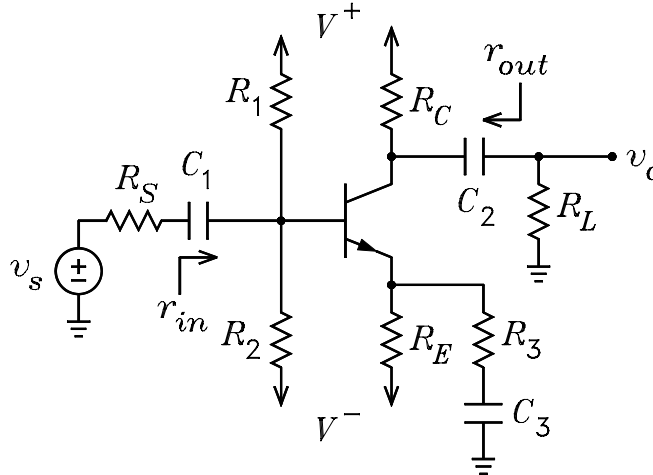


ECE3050 Homework Set 7


1. For the CE amplifier shown, let $R_S = 1\text{ k}\Omega$, $R_1 = 300\text{ k}\Omega$, $R_2 = 150\text{ k}\Omega$, $R_3 = 50\ \Omega$, $R_C = 4.3\text{ k}\Omega$, $R_E = 5.6\text{ k}\Omega$, $R_L = 20\text{ k}\Omega$, $V^+ = 15\text{ V}$, $V^- = -15\text{ V}$, $V_{BE} = 0.65\text{ V}$, $\beta = 99$, $r_x = 20\ \Omega$, $r_0 = 50\text{ k}\Omega$, and $V_T = 25\text{ mV}$.

- (a) Show that $I_E = 1.417\text{ mA}$ and $V_{CB} = 15.386\text{ V}$.
- (b) Use the r_0 approximations to show that $v_o/v_s = -43.74$, $r_{out} = 4.169\text{ k}\Omega$, and $r_{in} = 6.315\text{ k}\Omega$.
- (c) Show that the clipping levels are $v_O^+ = 4.964\text{ V}$ and $v_O^- = -15.62\text{ V}$.
- (d) Show that the emitter current which results in symmetrical clipping is $I_E = 2.222\text{ mA}$.
- (e) Show that the clipping levels for $I_E = 2.222\text{ mA}$ are $v_O^+ = -v_O^- = 7.786\text{ V}$.



2. For the CC amplifier example shown, let $R_s = 1\text{ k}\Omega$, $R_1 = 300\text{ k}\Omega$, $R_2 = 150\text{ k}\Omega$, $R_E = 5.6\text{ k}\Omega$, $R_L = 1\text{ k}\Omega$, $V^+ = 15\text{ V}$, $V^- = -15\text{ V}$, $V_{BE} = 0.65\text{ V}$, $\beta = 99$, $r_x = 20\ \Omega$, $r_0 = 50\text{ k}\Omega$, $V_{CEsat} = 0.2\text{ V}$, and $V_T = 25\text{ mV}$. In the ac signal circuit, combine r_0 in parallel with R_E from the emitter to ground. This can be done because $R_{tc} = 0$, which puts r_0 in parallel with R_E .

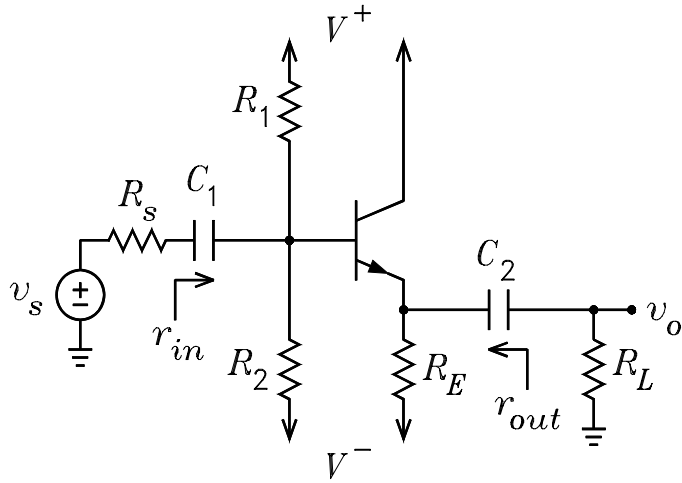- (a) Show that $I_E = 1.417\text{ mA}$, $V_{CB} = 21.417\text{ V}$.
- (b) Show that $v_o/v_s = 0.958$, $r_{out} = 27.596\ \Omega$, and $r_{in} = 46.01\text{ k}\Omega$.
- (c) Show that the clipping levels are $v_O^+ = 3.31\text{ V}$ and $v_O^- = -1.20\text{ V}$.
- (d) Show that the emitter current which results in symmetrical clipping is $I_E = 2.661\text{ mA}$.
- (e) Show that the clipping levels for $I_E = 2.661\text{ mA}$ are $v_O^+ = -v_O^- = 2.257\text{ V}$.



3. For the CB amplifier shown, let $R_s = 50\ \Omega$, $R_1 = 300\ \text{k}\Omega$, $R_2 = 150\ \text{k}\Omega$, $R_C = 4.3\ \text{k}\Omega$, $R_E = 5.6\ \text{k}\Omega$, $R_L = 20\ \text{k}\Omega$, $V^+ = 15\ \text{V}$, $V^- = -15\ \text{V}$, $V_{BE} = 0.65\ \text{V}$, $\beta = 99$, $r_x = 20\ \Omega$, $r_0 = 50\ \text{k}\Omega$, and $V_T = 25\ \text{mV}$.

- (a) Show that $I_E = 1.417\ \text{mA}$ and $V_{CB} = 15.386\ \text{V}$.
 (b) Use the r_0 approximations to show that $v_o/v_s = 50.552$, $r_{out} = 4.202\ \text{k}\Omega$, and $r_{in} = 17.79\ \Omega$.

