
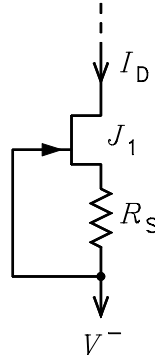


ECE3050 – Assignment 15

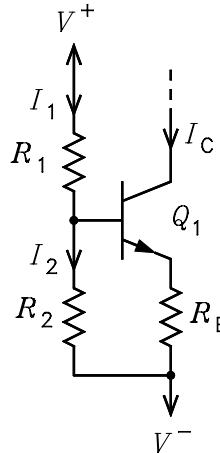1. The figure shows a JFET current source used as the tail supply for a diff amp. It is given that $V^- = -15\text{ V}$, $\beta = 0.004\text{ A/V}^2$, and $V_{TO} = -3\text{ V}$. Use the equations $I_D = \beta(V_{GS} - V_{TO})^2$ and $V_{GS} = -I_D R_S$ to solve for the drain current I_D .



2. The figure shows a BJT current source. It is given that $V^+ = 24\text{ V}$, $V^- = -24\text{ V}$, $V_T = 25\text{ mV}$, $I_S = 7.5 \times 10^{-15}\text{ A}$, and $\beta = 49$. (Note that $\beta = 49$ is a low current gain, but it forces you to consider the base current.)



- (a) Solve for V_{BE} for $I_C = 3\text{ mA}$. Answer: $V_{BE} = 0.668\text{ V}$.
- (b) Solve for R_E such that the voltage across R_E is V_{BE} . Answer: $R_E = 218\ \Omega$.
- (c) If $I_2 = 10I_B$, solve for R_2 . Answer: $R_2 = 2.18\text{ k}\Omega$.
- (d) Solve for R_1 . Answer: $R_1 = 69.3\text{ k}\Omega$.
- (e) If $V_A = 70\text{ V}$, $V_C = -1\text{ V}$, and $r_x = 40\ \Omega$, solve for r'_e , r_0 , and r_{ic} . Answers: $r'_e = 51.3\ \Omega$, $r_0 = 30.8\text{ k}\Omega$, $r_{ic} = 149\text{ k}\Omega$.
- (f) If the Early effect is neglected, i.e. assume that $\lambda = 0$ so that $\beta = \beta_0$, solve for R_S for $I_D = 2\text{ mA}$. Note that $I_Q = I_D$ for the diff amp tail supply. Answer: $R_S = 1.15\text{ k}\Omega$.
- (g) If $\lambda = 0.02\text{ V}^{-1}$ and the voltage at the JFET drain is $V_D = -1\text{ V}$, solve for the value of β (it is greater than β_0), r_0 , and r_{id} . Note that $R_Q = r_{id}$ for the diff amp tail supply. Answers: $r_0 = 30.9\text{ k}\Omega$, $r_{id} = 254\text{ k}\Omega$.