
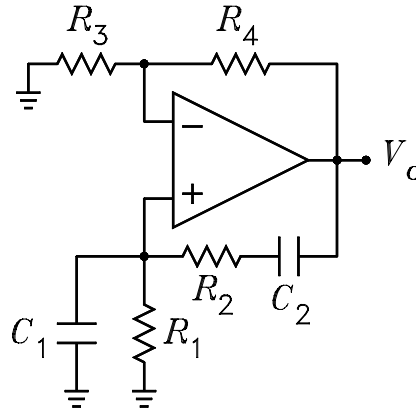


ECE3050 Assignment 19

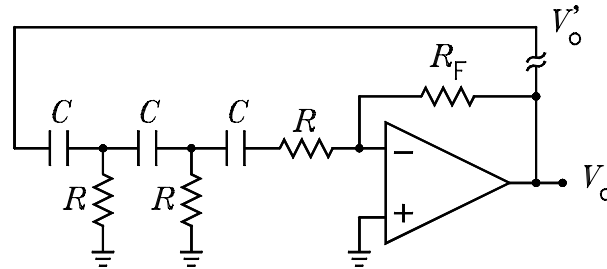1. The circuit shows a Wein bridge oscillator. If  $R_1 = R_2$ ,  $C_1 = 0.1 \mu\text{F}$ ,  $C_2 = 0.22 \mu\text{F}$ , and  $R_4 = 10 \text{ k}\Omega$ , specify  $R_1$ ,  $R_2$ , and  $R_3$  for the circuit to have stable oscillations at  $f = 1000 \text{ Hz}$ . Answers:  $R_1 = R_2 = 1073 \Omega$  and  $R_3 = 6875 \Omega$ .




2. The figure shows a phase-shift oscillator with the feedback loop broken.



By writing node equations, it can be shown that the loop-gain transfer function is given by

$$\frac{V_o'}{V_o} = -\frac{R_F}{R} \frac{(RCs)^3}{(RCs)^3 + 6(RCs)^2 + 5(RCs) + 1}$$

- (a) To solve for the frequency of oscillation, what do you set  $V_o'/V_o$  equal to? Answer:  $1\angle 0^\circ$ . (b) Use the transfer function to solve for the frequency of oscillation. Answer:  $f_0 = 1/(2\pi\sqrt{6}RC)$ . (c) Use the transfer function to solve for value of  $R_F/R$  in order for  $|V_o'/V_o| = 1\angle 0^\circ$  at  $f = f_0$ . Answer:  $R_F/R_1 = 29$ .
3. The figure shows a phase shift oscillator. If  $C = 0.1 \mu\text{F}$ , specify  $R$  and  $R_F$  for the circuit to have stable oscillations at  $f = 200 \text{ Hz}$ . Answers:  $R = 3249 \Omega$  and  $R_F = 94.21 \text{ k}\Omega$ .

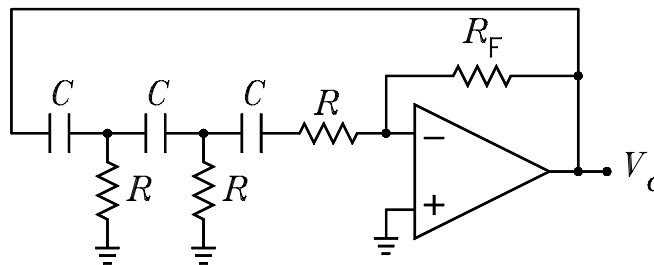

4. The loop-gain transfer function of a particular oscillator circuit is given by

$$\frac{V_o}{V'_o} = K \frac{s}{(s/100)^2 + 0.5(s/100) + 1}$$

At what frequency does the circuit oscillate and what must be the value of  $K$  for stable oscillations? Answers:  $f = 15.9\text{ Hz}$  and  $K = 0.005$ .