

The Common-Collector Amplifier

Basic Circuit

Fig. 1 shows the circuit diagram of a single stage common-collector amplifier. The object is to solve for the small-signal voltage gain, input resistance, and output resistance.

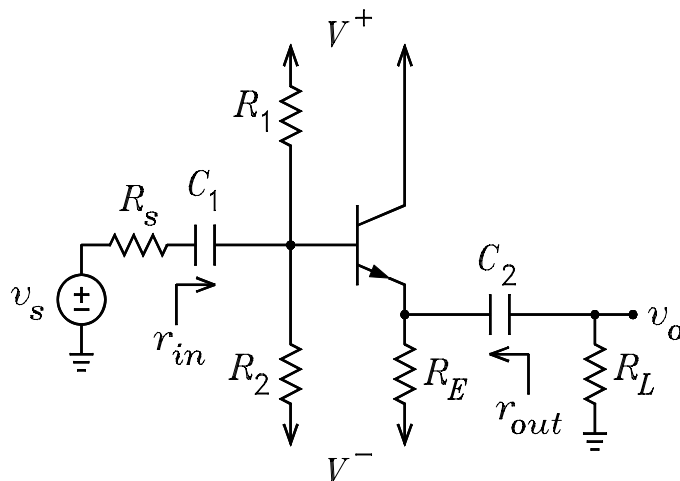


Figure 1: Common-collector amplifier.

DC Solution

(a) Replace the capacitors with open circuits. Look out of the 3 BJT terminals and make Thévenin equivalent circuits as shown in Fig. 2.

$$V_{BB} = \frac{V^+R_2 + V^-R_1}{R_1 + R_2} \quad R_{BB} = R_1 \parallel R_2$$

$$V_{EE} = V^- \quad R_{EE} = R_E \quad V_{CC} = V^+ \quad R_{CC} = R_C$$

(b) Make an “educated guess” for V_{BE} . Write the loop equation between the V_{BB} and the V_{EE} nodes.

$$V_{BB} - V_{EE} = I_B R_{BB} + V_{BE} + I_E R_{EE} = \frac{I_C}{\beta} R_{BB} + V_{BE} + \frac{I_C}{\alpha} R_{EE}$$

(c) Solve the loop equation for the currents.

$$I_C = \alpha I_E = \beta I_B = \frac{V_{BB} - V_{EE} - V_{BE}}{R_{BB}/\beta + R_{EE}/\alpha}$$

(d) Verify that $V_{CB} > 0$ for the active mode.

$$V_{CB} = V_C - V_B = (V_{CC} - I_C R_{CC}) - (V_{BB} - I_B R_{BB}) = V_{CC} - V_{BB} - I_C (R_{CC} - R_{BB}/\beta)$$

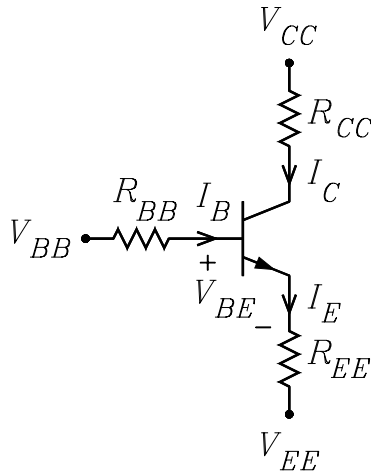


Figure 2: Bias circuit.

Small-Signal or AC Solutions

(a) Redraw the circuit with $V^+ = V^- = 0$ and all capacitors replaced with short circuits as shown in Fig. 3.

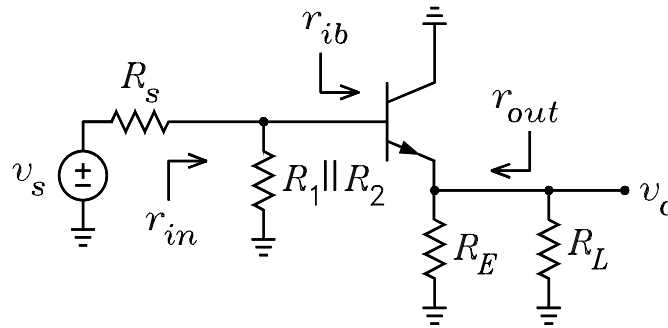


Figure 3: Signal circuit.

(b) Calculate g_m , r_π , r_e , and r_0 from the DC solution.

$$g_m = \frac{I_C}{V_T} \quad r_\pi = \frac{V_T}{I_B} \quad r_e = \frac{V_T}{I_E} \quad r_0 = \frac{V_A + V_{CE}}{I_C}$$

(c) Replace the circuits looking out of the base with a Thévenin equivalent circuit as shown in Fig. 4.

$$v_{tb} = v_s \frac{R_1 \parallel R_2}{R_s + R_1 \parallel R_2} \quad R_{tb} = R_1 \parallel R_2$$

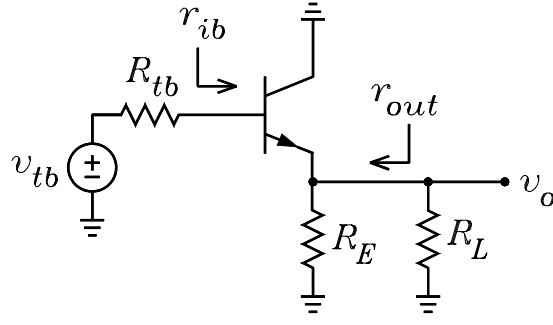


Figure 4: Signal circuit with Thévenin base circuit.

Exact Solution

(a) Replace the BJT in Fig. 4 with the Thévenin base emitter circuits as shown in Fig. 5. Solve for $v_{e(oc)}$.

$$v_{e(oc)} = v_{tb} \frac{r_0 + R_{tc}/(1 + \beta)}{r'_e + r_0 + R_{tc}/(1 + \beta)} \quad R_{tc} = 0$$

Note that the Thévenin resistance R_{tc} looking out of the collector is zero in the original circuit. The exact solution gives the correct answer even if $R_{tc} \neq 0$.

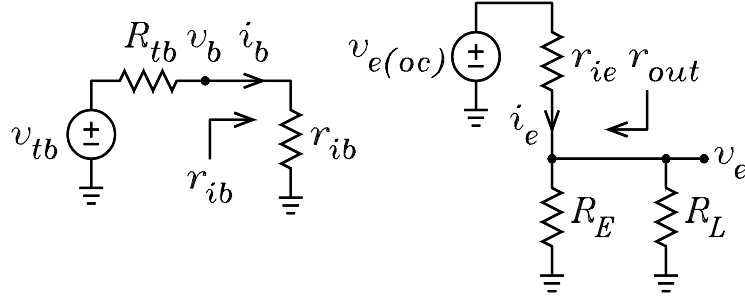


Figure 5: Base and emitter equivalent circuits.

(b) Solve for v_o .

$$v_o = v_{e(oc)} \frac{R_E \parallel R_L}{r_{ie} + R_E \parallel R_L} = v_s \frac{R_1 \parallel R_2}{R_s + R_1 \parallel R_2} \frac{r_0 + R_{tc}/(1 + \beta)}{r'_e + r_0 + R_{tc}/(1 + \beta)} \frac{R_E \parallel R_L}{r_{ie} + R_E \parallel R_L}$$

$$r_{ie} = r'_e \frac{r_0 + R_{tc}}{r'_e + r_0 + R_{tc}/(1 + \beta)} \quad r'_e = \frac{R_{tb} + r_x + r_\pi}{1 + \beta} = \frac{R_{tb} + r_x}{1 + \beta} + r_e$$

(c) Solve for the voltage gain.

$$A_v = \frac{v_o}{v_s} = \frac{R_1 \parallel R_2}{R_s + R_1 \parallel R_2} \frac{r_0 + R_{tc}/(1 + \beta)}{r'_e + r_0 + R_{tc}/(1 + \beta)} \frac{R_E \parallel R_L}{r_{ie} + R_E \parallel R_L}$$

(d) Solve for r_{in} .

$$r_{in} = R_1 \parallel R_2 \parallel r_{ib} \quad r_{ib} = r_x + r_\pi + R_{te} \frac{(1 + \beta) r_0 + R_{tc}}{r_0 + R_{te} + R_{tc}} \quad R_{te} = R_E \parallel R_L$$

(e) Solve for r_{out} .

$$r_{out} = r_{ie} \parallel R_E$$

(f) Special case for $r_0 = \infty$.

$$v_{e(oc)} = v_{tb} \quad r_{ib} = r_x + r_\pi + (1 + \beta) R_{te} \quad r_{ie} = r'_e$$

Example 1 For the CC amplifier in Fig. 1, it is given that $R_S = 5 \text{ k}\Omega$, $R_1 = 120 \text{ k}\Omega$, $R_2 = 100 \text{ k}\Omega$, $R_E = 5.6 \text{ k}\Omega$, $R_L = 20 \text{ k}\Omega$, $V^+ = 15 \text{ V}$, $V^- = -15 \text{ V}$, $V_{BE} = 0.65 \text{ V}$, $\beta = 99$, $\alpha = 0.99$, $r_x = 20 \Omega$, $V_A = 100 \text{ V}$ and $V_T = 0.025 \text{ V}$. Solve for A_v , r_{in} , and r_{out} .

Solution. Because the dc bias circuits are the same as for the common-emitter amplifier example, the bias values, r_e , g_m , and r_π are the same. Because V_{CE} is different, a new value of r_0 must be calculated. The collector-to-emitter voltage is given by

$$V_{CE} = V_C - V_E = V^+ - \left(V_{BB} - \frac{I_E}{1 + \beta} R_{BB} - V_{BE} \right) = 17.01 \text{ V}$$

Thus r_0 has the value

$$r_0 = \frac{V_A + V_{CE}}{\alpha I_E} = 55.93 \text{ k}\Omega$$

In the signal circuit, the Thévenin voltage and resistance seen looking out of the base are given by

$$v_{tb} = \frac{R_1 \parallel R_2}{R_S + R_1 \parallel R_2} v_s = 0.916 v_s \quad R_{tb} = R_S \parallel R_1 \parallel R_2 = 4.58 \text{ k}\Omega$$

The Thévenin resistances seen looking out of the emitter and the collector are

$$R_{te} = R_E \parallel R_3 = 4.375 \text{ k}\Omega \quad R_{tc} = 0$$

Next, we calculate r'_e , $v_{e(oc)}$, r_{ie} , and r_{ib} , where $R_{tc} = 0$.

$$r'_e = \frac{R_{tb} + r_x}{1 + \beta} + r_e = 57.83 \Omega$$

$$v_{e(oc)} = \frac{r_0 + R_{tc} / (1 + \beta)}{r'_e + r_0 + R_{tc} / (1 + \beta)} v_{tb} = 0.999 v_{tb}$$

$$r_{ie} = r'_e \frac{r_0 + R_{tc}}{r'_e + r_0 + R_{tc} / (1 + \beta)} = 57.77 \Omega$$

$$r_{ib} = r_x + (1 + \beta) r_e + R_{te} \frac{(1 + \beta) r_0 + R_{tc}}{r_0 + R_{te} + R_{tc}} = 407 \text{ k}\Omega$$

The output voltage is given by

$$v_o = \frac{R_{te}}{r_{ie} + R_{te}} v_{e(oc)} = 0.987 \times 0.999 \times 0.916 v_s = 0.903 v_s$$

Thus the voltage gain is

$$A_v = 0.903$$

The input and output resistances are given by

$$r_{in} = R_1 \parallel R_2 \parallel r_{ib} = 48.1 \text{ k}\Omega \quad r_{out} = r_{ie} \parallel R_E \parallel R_L = 57.02 \Omega$$

Alternate Solutions

These solutions are exact because the Thévenin resistance R_{tc} looking out of the collector is zero. If $R_{tc} \neq 0$, replace r_0 with an open circuit in all formulas, i.e. let $r_0 = \infty$. In this case, the solutions are no longer exact, they are approximate.

Emitter Equivalent Circuit Solution

(a) After making the Thévenin equivalent circuits looking out of the base, replace the BJT with the emitter equivalent circuit as shown in Fig. 6.

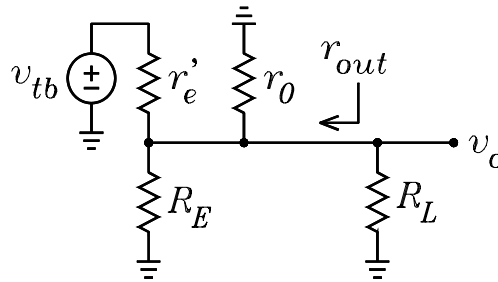


Figure 6: Simplified T model.

(b) Solve for r'_e .

$$r'_e = \frac{R_{tb} + r_x}{1 + \beta} + r_e \quad R_{tb} = R_S \parallel R_1 \parallel R_2$$

(c) Solve for v_o .

$$v_o = v_{tb} \frac{r_0 \parallel R_E \parallel R_L}{r'_e + r_0 \parallel R_E \parallel R_L} = v_s \frac{R_1 \parallel R_2}{R_s + R_1 \parallel R_2} \frac{r_0 \parallel R_E \parallel R_L}{r'_e + r_0 \parallel R_E \parallel R_L}$$

(d) Solve for the voltage gain.

$$A_v = \frac{v_o}{v_s} = \frac{R_1 \parallel R_2}{R_s + R_1 \parallel R_2} \frac{r_0 \parallel R_E \parallel R_L}{r'_e + r_0 \parallel R_E \parallel R_L}$$

(e) Solve for r_{in} . Because the base node is absorbed, use the formula for r_{ib} .

$$r_{in} = R_1 \parallel R_2 \parallel r_{ib} \quad r_{ib} = r_x + (1 + \beta)(r_e + r_0 \parallel R_{te}) \quad R_{te} = R_E \parallel R_L$$

(f) Solve for r_{out} .

$$r_{out} = r_0 \parallel r'_e \parallel R_E$$

Example 2 Use the simplified T-model solutions to calculate the values of A_v , r_{in} , and r_{out} for Example 1.

$$A_v = 0.916 \times 0.986 = 0.903$$

$$r_{in} = 48.51 \text{ k}\Omega \quad r_{out} = 57.18 \Omega$$

π Model Solution

(a) After making the Thévenin equivalent circuits looking out of the base and emitter, replace the BJT with the π model as shown in Fig. 7.

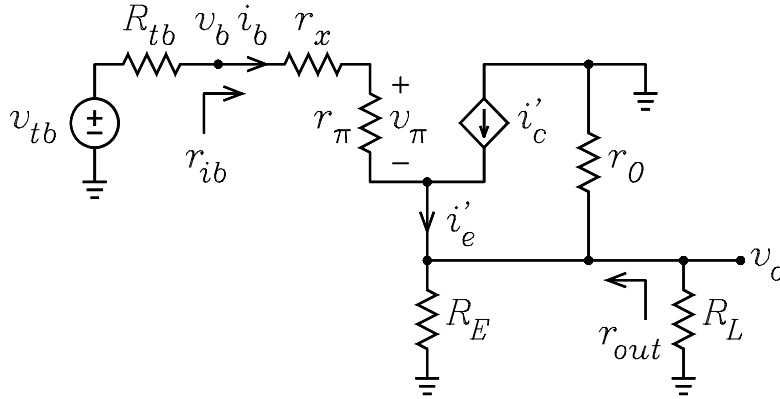


Figure 7: Hybrid- π model.

(b) Solve for i'_e .

$$v_{tb} = i_b (R_{tb} + r_x + r_\pi) + i'_e r_o \parallel R_E \parallel R_L = \frac{i'_e}{1 + \beta} (R_{tb} + r_x + r_\pi) + i'_e r_o \parallel R_E \parallel R_L$$

$$\Rightarrow i'_e = \frac{v_{tb}}{\frac{R_{tb} + r_x + r_\pi}{1 + \beta} + r_o \parallel R_E \parallel R_L}$$

(c) Solve for v_o .

$$v_o = i'_e r_o \parallel R_E \parallel R_L = \frac{v_{tb}}{\frac{R_{tb} + r_x + r_\pi}{1 + \beta} + r_o \parallel R_E \parallel R_L} r_o \parallel R_E \parallel R_L$$

$$= v_s \frac{R_1 \parallel R_2}{R_s + R_1 \parallel R_2} \frac{r_o \parallel R_E \parallel R_L}{\frac{R_{tb} + r_x + r_\pi}{1 + \beta} + r_o \parallel R_E \parallel R_L}$$

(d) Solve for the voltage gain.

$$A_v = \frac{v_o}{v_s} = \frac{R_1 \parallel R_2}{R_s + R_1 \parallel R_2} \frac{r_o \parallel R_E \parallel R_L}{\frac{R_{tb} + r_x + r_\pi}{1 + \beta} + r_o \parallel R_E \parallel R_L}$$

(e) Solve for r_{ib} and r_{in} .

$$v_b = i_b (r_x + r_\pi) + i'_e r_o \parallel R_E \parallel R_L = i_b (r_x + r_\pi) + (1 + \beta) i_b r_o \parallel R_E \parallel R_L$$

$$= i_b [r_x + r_\pi + (1 + \beta) r_o \parallel R_E \parallel R_L]$$

$$r_{ib} = \frac{v_b}{i_b} = r_x + r_\pi + (1 + \beta) r_o \parallel R_E \parallel R_L$$

$$r_{in} = R_1 \parallel R_2 \parallel r_{ib}$$

(f) Solve for r_{out} . First, solve for the open-circuit output voltage. This is the output voltage with $R_L = \infty$.

$$v_{o(oc)} = v_{tb} \frac{r_0 \parallel R_E}{\frac{R_{tb} + r_x + r_\pi}{1 + \beta} + r_0 \parallel R_E}$$

Next, solve for the short-circuit output current. This is the output current with $R_L = 0$. The output current is given by

$$i_o = \frac{v_o}{R_L} = \frac{v_{tb}}{\frac{R_{tb} + r_x + r_\pi}{1 + \beta} + r_0 \parallel R_E \parallel R_L} \frac{r_0 \parallel R_E \parallel R_L}{R_L} = \frac{v_{tb}}{\frac{R_{tb} + r_x + r_\pi}{1 + \beta} + r_0 \parallel R_E \parallel R_L} \frac{r_0 \parallel R_E}{R_L + r_0 \parallel R_E}$$

Now, let $R_L = 0$ to obtain

$$i_{o(sc)} = \frac{v_{tb}}{\frac{R_{tb} + r_x + r_\pi}{1 + \beta}}$$

The output resistance is given by

$$r_{out} = \frac{v_{o(oc)}}{i_{o(sc)}} = \frac{r_0 \parallel R_E}{\frac{R_{tb} + r_x + r_\pi}{1 + \beta} + r_0 \parallel R_E} \frac{R_{tb} + r_x + r_\pi}{1 + \beta} = \left(\frac{R_{tb} + r_x + r_\pi}{1 + \beta} \right) \parallel r_0 \parallel R_E$$

Note this is simply $r'_e \parallel r_0 \parallel R_E$, an answer that is obvious using the emitter equivalent circuit.

Example 3 Use the π -model solutions to calculate the values of A_v , r_{in} , and r_{out} for Example 1.

$$A_v = 0.916 \times 0.986 = 0.903$$

$$r_{in} = 48.51 \text{ k}\Omega \quad r_{out} = 57.18 \Omega$$

T Model Solution

(a) After making the Thévenin equivalent circuits looking out of the base and emitter, replace the BJT with the T model as shown in Fig. 8.

(b) Solve for i'_e .

$$v_{tb} = i_b (R_{tb} + r_x) + i'_e (r_e + r_0 \parallel R_E \parallel R_L) = \frac{i'_e}{1 + \beta} (R_{tb} + r_x) + i'_e (r_e + r_0 \parallel R_E \parallel R_L)$$

$$\Rightarrow i'_e = \frac{v_{tb}}{\frac{R_{tb} + r_x}{\beta} + r_e + r_0 \parallel R_E \parallel R_L}$$

(c) Solve for v_o .

$$v_o = i'_e r_0 \parallel R_E \parallel R_L = \frac{v_{tb}}{\frac{R_{tb} + r_x}{\beta} + r_e + r_0 \parallel R_E \parallel R_L} r_0 \parallel R_E \parallel R_L$$

$$= v_s \frac{R_1 \parallel R_2}{R_s + R_1 \parallel R_2} \frac{r_0 \parallel R_E \parallel R_L}{\frac{R_{tb} + r_x}{\beta} + r_e + r_0 \parallel R_E \parallel R_L}$$

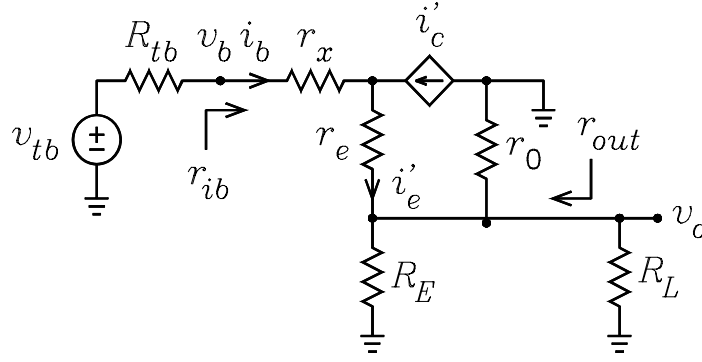


Figure 8: T model circuit.

(d) Solve for the voltage gain.

$$A_v = \frac{v_o}{v_s} = \frac{R_1 \parallel R_2}{R_s + R_1 \parallel R_2} \frac{r_o \parallel R_E \parallel R_L}{\frac{R_{tb} + r_x}{\beta} + r_e + r_o \parallel R_E \parallel R_L}$$

(e) Solve for r_{ib} and r_{in} .

$$\begin{aligned} v_b &= i_b r_x + i'_e (r_e + r_o \parallel R_E \parallel R_L) = i_b r_x + (1 + \beta) i_b (r_e + r_o \parallel R_E \parallel R_L) \\ &= i_b [r_x + (1 + \beta) (r_e + r_o \parallel R_E \parallel R_L)] \end{aligned}$$

$$r_{ib} = \frac{v_b}{i_b} = r_x + (1 + \beta) (r_e + r_o \parallel R_E \parallel R_L)$$

$$r_{in} = R_1 \parallel R_2 \parallel r_{ib}$$

(f) Solve for r_{out} . First, solve for the open-circuit output voltage. This is the output voltage with $R_L = \infty$.

$$v_{o(oc)} = v_{tb} \frac{r_o \parallel R_E}{\frac{R_{tb} + r_x}{\beta} + r_e + r_o \parallel R_E}$$

Next, solve for the short-circuit output current. This is the output current with $R_L = 0$. The output current is given by

$$i_o = \frac{v_o}{R_L} = \frac{v_{tb}}{\frac{R_{tb} + r_x}{1 + \beta} + r_e + r_o \parallel R_E} \frac{r_o \parallel R_E \parallel R_L}{R_L} = \frac{v_{tb}}{\frac{R_{tb} + r_x}{1 + \beta} + r_e r_o \parallel R_E} \frac{r_o \parallel R_E}{R_L + r_o \parallel R_E}$$

Now, let $R_L = 0$ to obtain

$$i_{o(sc)} = \frac{v_{tb}}{\frac{R_{tb} + r_x}{1 + \beta} + r_e}$$

The output resistance is given by

$$r_{out} = \frac{v_{o(oc)}}{i_{o(sc)}} = \frac{r_o \parallel R_E}{\frac{R_{tb} + r_x}{1 + \beta} + r_e + r_o \parallel R_E} \left(\frac{R_{tb} + r_x}{1 + \beta} + r_e \right) = \left(\frac{R_{tb} + r_x}{1 + \beta} + r_e \right) \parallel r_o \parallel R_E$$

This is the same answer obtained from the emitter equivalent circuit.

Example 4 Use the T-model solutions to calculate the values of A_v , r_{in} , and r_{out} for Example 1.

$$A_v = 0.916 \times 0.986 = 0.903$$
$$r_{in} = 48.51 \text{ k}\Omega \quad r_{out} = 57.18 \text{ }\Omega$$