

The Common-Gate Amplifier

Basic Circuit

Fig. 1 shows the circuit diagram of a single stage common-gate amplifier. The object is to solve for the small-signal voltage gain, input resistance, and output resistance.

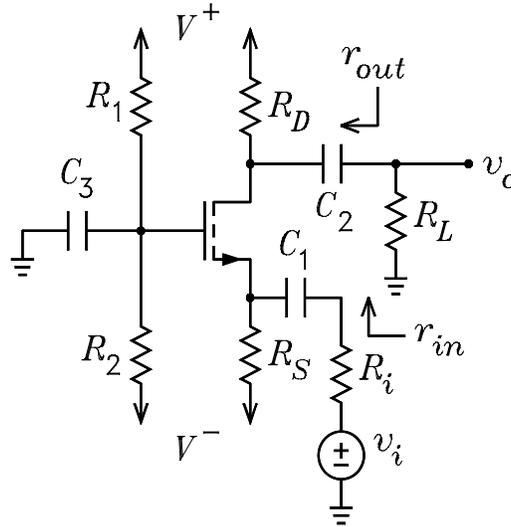


Figure 1: Common-gate amplifier.

DC Solution

(a) Replace the capacitors with open circuits. Look out of the 3 MOSFET terminals and make Thévenin equivalent circuits as shown in Fig. 2.

$$V_{GG} = \frac{V^+ R_2 + V^- R_1}{R_1 + R_2} \quad R_{GG} = R_1 \parallel R_2$$

$$V_{SS} = V^- \quad R_{SS} = R_S \quad V_{DD} = V^+ \quad R_{DD} = R_D$$

(b) Write the loop equation between the V_{GG} and the V_{SS} nodes.

$$V_{GG} - V_{SS} = V_{GS} + I_S R_{SS} = V_{GS} + I_D R_{SS}$$

(c) Use the equation for the drain current to solve for V_{GS} .

$$V_{GS} = \sqrt{\frac{I_D}{K}} + V_{TO}$$

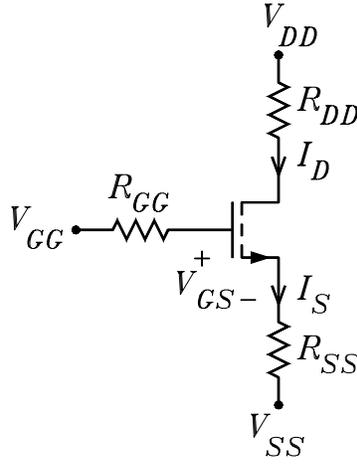


Figure 2: Bias circuit.

(d) Solve the equations simultaneously.

$$I_D R_{SS} + \sqrt{\frac{I_D}{K}} + [(V_{GG} - V_{SS}) - V_{TO}] = 0$$

(e) Let $V_1 = (V_{GG} - V_{SS}) - V_{TO}$. Solve the quadratic for I_D .

$$I_D = \left(\frac{\sqrt{1 + 4KV_1 R_{SS}} - 1}{2R_{SS}\sqrt{K}} \right)^2$$

(d) Verify that $V_{DS} > V_{GS} - V_{TO} = \sqrt{I_D/K}$ for the active mode.

$$V_{DS} = V_D - V_S = (V_{DD} - I_D R_{DD}) - (V^- + I_D R_{SS}) = V_{DD} - V_{SS} - I_D R_{DD}$$

Small-Signal or AC Solutions

(a) Redraw the circuit with $V^+ = V^- = 0$ and all capacitors replaced with short circuits as shown in Fig. 3.

(b) Calculate g_m , r_s , and r_0 from the DC solution..

$$g_m = 2\sqrt{KI_D} \quad r_s = \frac{1}{g_m} \quad r_0 = \frac{\lambda^{-1} + V_{DS}}{I_D}$$

(c) Replace the circuit looking out of the source with a Thévenin equivalent circuit as shown in Fig. 4.

$$v_{ts} = v_i \frac{R_S}{R_s + R_S} \quad R_{ts} = R_s \parallel R_S$$

Exact Solution

(a) Replace the circuit seen looking into the drain with its Norton equivalent circuit as shown in Fig. 5. Solve for $i_{d(sc)}$.

$$i_{d(sc)} = -G_{ms} v_{ts} = -G_{ms} v_i \frac{R_S}{R_s + R_S}$$

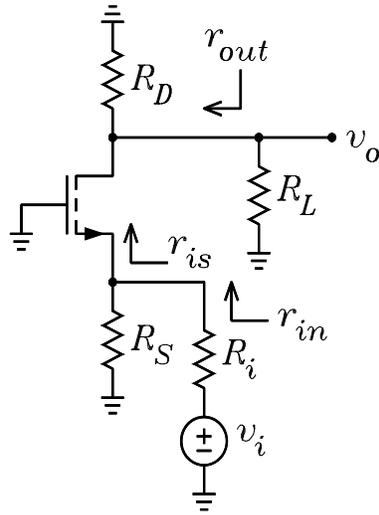


Figure 3: Signal circuit.

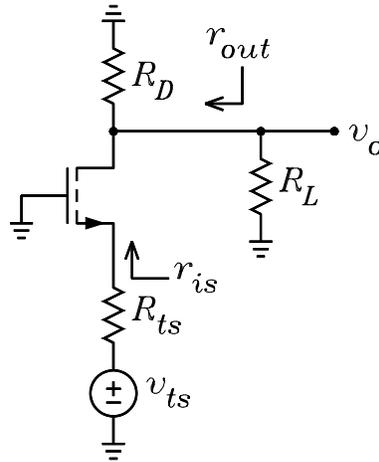


Figure 4: Signal circuit with Thévenin source circuit.

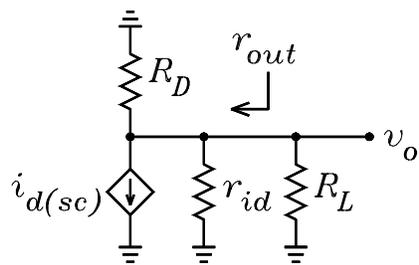


Figure 5: Norton collector circuit.

$$G_{ms} = \frac{1}{R_{ts} + r_s \parallel r_0}$$

(b) Solve for v_o .

$$v_o = -i_{d(sc)} r_{id} \parallel R_D \parallel R_L = G_{ms} v_i \frac{R_S}{R_s + R_S} r_{id} \parallel R_D \parallel R_L$$

$$r_{id} = \frac{r_0 + r_s \parallel R_{ts}}{1 - R_{ts} / (r_s + R_{te})} = r_0 \left(1 + \frac{R_{ts}}{r_s} \right) + R_{ts}$$

(b) Solve for the voltage gain.

$$A_v = \frac{v_o}{v_i} = \frac{R_S}{R_s + R_S} G_{ms} \times r_{id} \parallel R_D \parallel R_L$$

(c) Solve for r_{in} .

$$r_{in} = R_1 \parallel R_2 \parallel r_{is} \quad r_{is} = r'_e \frac{r_0 + R_D \parallel R_L}{r'_e + r_0}$$

(d) Solve for r_{out} .

$$r_{out} = r_{id} \parallel R_D$$

Example 1 For the CS amplifier of Fig. ??, it is given that $R_i = 50 \Omega$, $R_1 = 5 \text{ M}\Omega$, $R_2 = 1 \text{ M}\Omega$, $R_D = 10 \text{ k}\Omega$, $R_S = 3 \text{ k}\Omega$, $R_3 = 50 \Omega$, $R_L = 20 \text{ k}\Omega$, $V^+ = 24 \text{ V}$, $V^- = -24 \text{ V}$, $K_0 = 0.001 \text{ A/V}^2$, $V_{TO} = 1.75 \text{ V}$, $\lambda = 0.016 \text{ V}^{-1}$. Solve for the gain $A_v = v_o/v_i$, the input resistance r_{in} , and the output resistance r_{out} . The capacitors can be assumed to be ac short circuits at the operating frequency.

Solution. For the dc bias solution, replace all capacitors with open circuits. The Thévenin voltage and resistance seen looking out of the gate are

$$V_{GG} = \frac{V^+ R_2 + V^- R_1}{R_1 + R_2} = -16 \text{ V} \quad R_{BB} = R_1 \parallel R_2 = 833.3 \text{ k}\Omega$$

The Thévenin voltage and resistance seen looking out of the source are $V_{SS} = V^-$ and $R_{SS} = R_S$. To calculate I_D , we neglect the Early effect by setting $K = K_0$. The bias equation for I_D is

$$I_D = \left(\frac{\sqrt{1 + 4K V_1 R_{SS}} - 1}{2\sqrt{K} R_{SS}} \right)^2 = 1.655 \text{ mA}$$

To test for the active mode, we calculate the drain-source voltage

$$V_{DS} = V_D - V_S = (V^+ - I_D R_D) - (V^- + I_D R_{SS}) = 26.491 \text{ V}$$

This must be greater than $V_{GS} - V_{TO} = \sqrt{I_D/K} = 1.286 \text{ V}$. It follows that the MOSFET is biased in its active mode.

For the small-signal ac analysis, we need g_m , r_s , and r_0 . When the Early effect is accounted for, the new value of K is given by

$$K = K_0 (1 + \lambda V_{DS}) = 1.424 \times 10^{-3} \text{ A/V}^2$$

Note that this is an approximation because the Early effect was neglected in calculating V_{DS} . However, the approximation should be close to the true value. It follows that g_m , r_s , and r_0 are given by

$$g_m = 2\sqrt{K I_D} = 3.07 \times 10^{-3} \text{ A/V} \quad r_s = \frac{1}{g_m} = 325.758 \Omega$$

$$r_0 = \frac{\lambda^{-1} + V_{DS}}{I_D} = 53.78 \text{ k}\Omega$$

For the small-signal analysis, V^+ and V^- are zeroed and the three capacitors are replaced with ac short circuits. The Thévenin voltage and resistance seen looking out of the gate are given by

$$v_{tg} = v_i \frac{R_S}{R_i + R_S} = 0.984v_i \quad R_{ts} = R_i \parallel R_S = 49.18 \Omega$$

The Thévenin resistances seen looking out of the gate and the drain are

$$R_{tg} = 0 \Omega \quad R_{td} = R_D \parallel R_L = 6.667 \text{ k}\Omega$$

Next, we calculate G_{ms} and r_{id}

$$G_{ms} = \frac{1}{R_{ts} + r_s \parallel r_0} = \frac{1}{372.978} \text{ S}$$

$$r_{id} = r_0 \left(1 + \frac{R_{ts}}{r_s} \right) + R_{ts} = 61.95 \text{ k}\Omega$$

The output voltage is given by

$$v_o = G_{ms} \times (r_{id} \parallel R_{td}) v_{tg} = G_{mg} \times (r_{id} \parallel R_{td}) \times 0.984v_i = 15.873v_i$$

Thus the voltage gain is

$$A_v = \frac{v_o}{v_i} = 15.873$$

The input and output resistances are given by

$$r_{is} = r_s \frac{r_0 + R_{td}}{r_0 + r_s} = 363.932 \Omega \quad r_{in} = r_{is} \parallel R_2 = 324.56 \Omega$$

$$r_{out} = r_{id} \parallel R_D = 8.61 \text{ k}\Omega$$

Approximate Solutions

These solutions assume that $r_0 = \infty$ except in calculating r_{id} . In this case, $i_{d(sc)} = i'_d = i'_s$.

Source Equivalent Circuit Solution

(a) After making the Thévenin equivalent circuit looking out of the source, replace the MOSFET with the source equivalent circuit as shown in Fig. 6.

(b) Solve for i'_d .

$$0 - v_{ts} = i'_s (r_s + R_{ts}) = i'_d (r_s + R_{ts}) \implies i'_d = -v_{ts} \frac{1}{r_s + R_{ts}}$$

(c) Solve for v_o .

$$v_o = -i'_d r_{id} \parallel R_D \parallel R_L = v_{ts} \frac{1}{r_s + R_{ts}} r_{id} \parallel R_D \parallel R_L = v_i \frac{R_S}{R_s + R_S} \frac{1}{r_s + R_{ts}} r_{id} \parallel R_D \parallel R_L$$

(d) Solve for the voltage gain.

$$A_v = \frac{v_o}{v_i} = \frac{R_S}{R_s + R_S} \frac{1}{r_s + R_{ts}} r_{id} \parallel R_D \parallel R_L$$

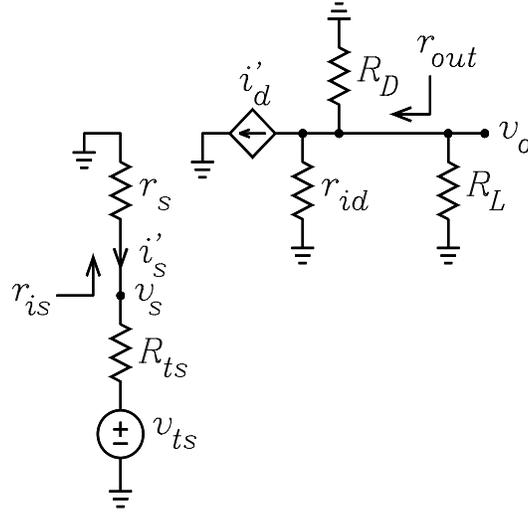


Figure 6: Source equivalent circuit.

(e) Solve for r_{is} and r_{in} .

$$0 - v_s = i'_s r_s \implies i'_s = -\frac{v_s}{r_s}$$

$$r_{is} = \frac{v_s}{-i'_s} = r_s$$

$$r_{in} = r_s \parallel R_S$$

(f) Solve for r_{out} .

$$r_{out} = r_{id} \parallel R_D$$

Example 2 Use the simplified T -model solutions to calculate the values of A_v , r_{in} , and r_{out} for Example 1.

$$A_v = 0.984 \times (2.667 \times 10^{-3}) \times (5.931 \times 10^3) = 15.56$$

$$r_{in} = 325.65 \Omega \quad r_{id} = 61.95 \text{ k}\Omega \quad r_{out} = 8.61 \text{ k}\Omega$$

π Model Solution

(a) After making the Thévenin equivalent circuit looking out of the source, replace the MOSFET with the π model as shown in Fig. 7.

(b) Solve for i'_d .

$$0 - v_{ts} = v_\pi + i'_s R_{ts} = \frac{i'_d}{g_m} + i'_d R_{ts} \implies i'_d = \frac{-v_{ts}}{\frac{1}{g_m} + R_{ts}}$$

(c) Solve for v_o .

$$v_o = -i'_d r_{id} \parallel R_D \parallel R_L = \frac{v_{ts}}{\frac{1}{g_m} + R_{ts}} r_{id} \parallel R_D \parallel R_L = v_i \frac{R_S}{R_S + R_S} \frac{r_{id} \parallel R_D \parallel R_L}{\frac{1}{g_m} + R_{ts}}$$

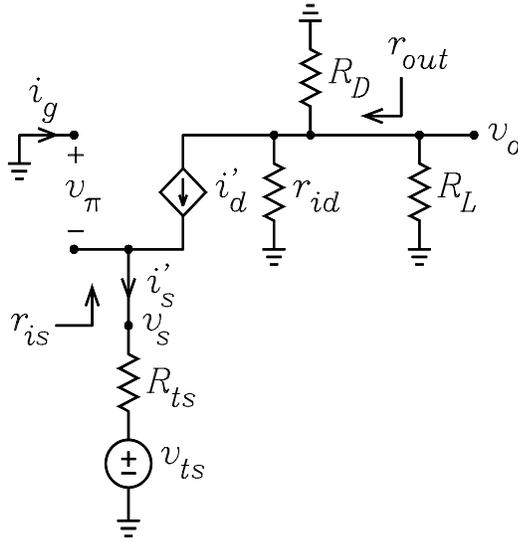


Figure 7: Hybrid π model circuit.

(d) Solve for the voltage gain.

$$A_v = \frac{v_o}{v_i} = \frac{R_S}{R_s + R_S} \frac{r_{id} \| R_D \| R_L}{\frac{1}{g_m} + R_{ts}}$$

(e) Solve for r_{out} .

$$r_{out} = r_{id} \| R_D$$

(f) Solve for r_{is} and r_{in} .

$$0 - v_s = v_\pi = \frac{i'_d}{g_m} \implies i'_d = -g_m v_s$$

$$r_{is} = \frac{v_s}{-i'_s} = \frac{1}{g_m}$$

$$r_{in} = r_{is} \| R_S$$

Example 3 Use the π -model solutions to calculate the values of A_v , r_{in} , and r_{out} for Example 1.

$$A_v = 0.984 \times (2.667 \times 10^{-3}) \times (5.931 \times 10^3) = 15.56$$

$$r_{in} = 325.65 \Omega \quad r_{id} = 61.95 \text{ k}\Omega \quad r_{out} = 8.61 \text{ k}\Omega$$

T Model Solution

(a) After making the Thévenin equivalent circuit looking out of the source, replace the MOSFET with the T model as shown in Fig.8.

(b) Solve for i'_d .

$$0 - v_{ts} = i'_s (r_s + R_{ts}) = i'_d (r_s + R_{ts}) \implies i'_d = \frac{-v_{ts}}{r_s + R_{ts}}$$

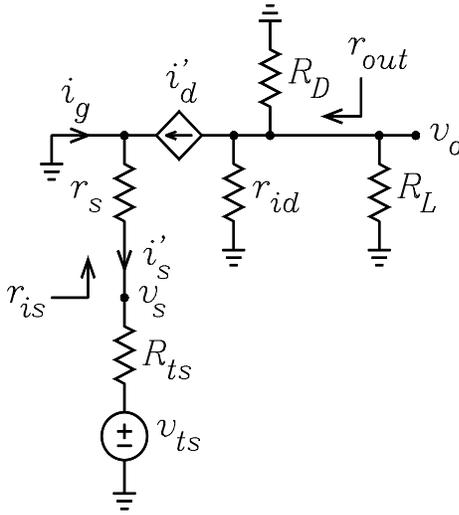


Figure 8: T model circuit.

(c) Solve for v_o .

$$v_o = -i'_d r_{id} \parallel R_D \parallel R_L = \frac{v_{ts}}{r_s + R_{ts}} r_{id} \parallel R_D \parallel R_L = v_i \frac{R_S}{R_s + R_S} \frac{r_{id} \parallel R_D \parallel R_L}{r_s + R_{ts}}$$

(d) Solve for the voltage gain.

$$A_v = \frac{v_o}{v_i} = \frac{R_S}{R_s + R_S} \frac{r_{id} \parallel R_D \parallel R_L}{r_s + R_{ts}}$$

(e) Solve for r_{is} and r_{in} .

$$0 - v_s = i'_s r_s \implies i'_s = \frac{-v_s}{r_s}$$

$$r_{is} = \frac{v_s}{-i'_s} = r_s$$

$$r_{in} = R_S \parallel r_{is}$$

(f) Solve for r_{out} .

$$r_{out} = r_{id} \parallel R_D$$

Example 4 Use the T-model solutions to calculate the values of A_v , r_{in} , and r_{out} for Example 1.

$$A_v = 0.984 \times (2.667 \times 10^{-3}) \times (5.931 \times 10^3) = 15.56$$

$$r_{in} = 325.65 \Omega \quad r_{id} = 61.95 \text{ k}\Omega \quad r_{out} = 8.61 \text{ k}\Omega$$