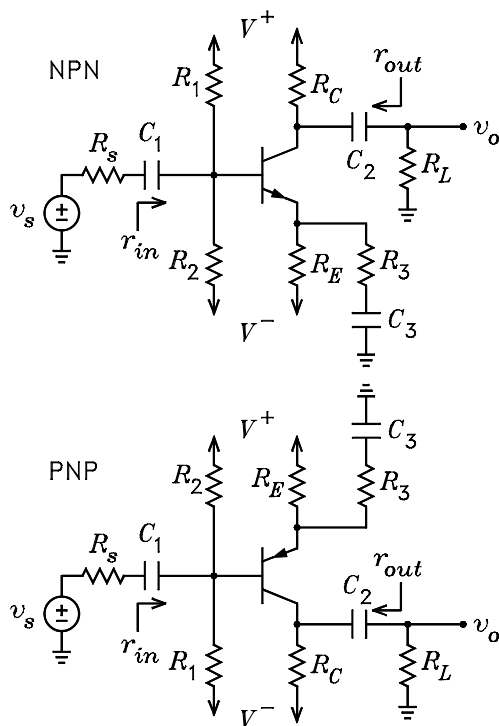


CE Amplifier Example

This example makes use of the expressions derived in class for the common-collector amplifier. For the circuits in the figure, it is given that $V^+ = 10\text{ V}$, $V^- = -10\text{ V}$, $R_s = 5\text{ k}\Omega$, $R_1 = 100\text{ k}\Omega$, $R_2 = 120\text{ k}\Omega$, $R_E = 2\text{ k}\Omega$, $R_3 = 51\text{ k}\Omega$, $R_C = 2.4\text{ k}\Omega$, $R_L = 10\text{ k}\Omega$, $V_{BE\text{npn}} = V_{EB\text{pnp}} = 0.65\text{ V}$, $V_T = 0.025\text{ V}$, $\alpha = 0.99$, $\beta = 99$, $r_x = 20\ \Omega$, and $r_0 = 50\text{ k}\Omega$. The capacitors are ac short circuits and dc open circuits. The equations below are written for the NPN circuit. By symmetry, the solutions are the same for the PNP circuit.



DC Solution

The dc solution is the same as for the CC amplifier and is repeated. To solve for I_E , replace the capacitors with open circuits. Look out the base and emitter and form Thévenin equivalent circuits. We have

$$\begin{aligned}
 V_{BB} &= \frac{V^+R_2 + V^-R_1}{R_1 + R_2} = 10\frac{120\text{ k}\Omega}{100\text{ k}\Omega + 120\text{ k}\Omega} - 10\frac{100\text{ k}\Omega}{100\text{ k}\Omega + 120\text{ k}\Omega} = \frac{10}{11} \\
 R_{BB} &= R_1 \parallel R_2 = 100\text{ k}\Omega \parallel 120\text{ k}\Omega = 54.55\text{ k}\Omega \\
 V_{EE} &= V^- \\
 R_{EE} &= R_E
 \end{aligned}$$

Write the base-emitter loop bias equation and solve for I_E to obtain

$$I_E = \frac{V_{BB} - V_{BE} - V_{EE}}{R_{BB}/(1 + \beta) + R_{EE}} = \frac{10/11 - 0.65 - (-10)}{54.55\text{ k}\Omega/(1 + 99) + 2\text{ k}\Omega} = 4.031\text{ mA}$$

The ac emitter intrinsic resistance is

$$r_e = \frac{V_T}{I_E} = \frac{25\text{ mV}}{4.031\text{ mA}} = 6.202\ \Omega$$

AC Solution – Method 1

This is based on the “full-blown” or first method given in class. Zero the dc supplies and short the capacitors. Look out the base and make a Thévenin equivalent circuit. We have

$$\begin{aligned}v_{tb} &= v_s \frac{R_1 \parallel R_2}{R_s + R_1 \parallel R_2} = v_s \frac{100 \text{ k}\Omega \parallel 120 \text{ k}\Omega}{5 \text{ k}\Omega + 100 \text{ k}\Omega \parallel 120 \text{ k}\Omega} = \frac{v_s}{1.092} = 0.9160 v_s \\R_{tb} &= R_s \parallel R_1 \parallel R_2 = 5 \text{ k}\Omega \parallel 100 \text{ k}\Omega \parallel 120 \text{ k}\Omega = 4.580 \text{ k}\Omega\end{aligned}$$

The Thévenin equivalent circuit looking into the i'_e branch is v_{tb} in series with r'_e , where

$$r'_e = \frac{R_{tb} + r_x}{1 + \beta} + r_e = \frac{4.580 \text{ k}\Omega + 20}{1 + 99} + 6.202 = 52.20 \Omega$$

The resistance looking out of the emitter is

$$R_{te} = R_E \parallel R_3 = 2 \text{ k}\Omega \parallel 51 = 49.73$$

The resistance looking out of the collector is

$$R_{tc} = R_C \parallel R_L = 2.4 \text{ k}\Omega \parallel 10 \text{ k}\Omega = 1.936 \text{ k}\Omega$$

The collector output resistance is

$$r_{ic} = \frac{r_0 + r'_e \parallel R_{te}}{1 - \alpha R_{te} / (r'_e + R_{te})} = \frac{50 \text{ k}\Omega + 52.20 \parallel 49.73}{1 - 0.99 \times 49.73 / (49.73 + 52.20)} = 97.76 \text{ k}\Omega$$

The short circuit collector output current is

$$\begin{aligned}i_{c(sc)} &= G_{mb} v_{tb} = \frac{\alpha}{r'_e + R_{te}} \frac{r_0 - R_{te} / \beta}{r_0 + r'_e \parallel R_{te}} v_{tb} \\ &= \frac{0.99}{52.20 + 49.73} \frac{50 \text{ k}\Omega - 49.73 / 99}{50 \text{ k}\Omega + 52.20 \parallel 49.73} v_{tb} = \frac{v_{tb}}{103.0} = \frac{v_s}{112.4}\end{aligned}$$

The output voltage is given by

$$v_o = -i_{c(sc)} r_{ic} \parallel R_{tc} = \frac{-v_s}{112.4} 97.76 \text{ k}\Omega \parallel 1.936 \text{ k}\Omega = -16.89 v_s$$

Thus the voltage gain is

$$\frac{v_o}{v_s} = -16.87$$

The output resistance is

$$r_{out} = R_c \parallel r_{ic} = 2.4 \text{ k}\Omega \parallel 97.76 \text{ k}\Omega = 2.342 \text{ k}\Omega$$

The resistance looking into the base is

$$\begin{aligned}r_{ib} &= r_x + (1 + \beta) r_e + R_{te} \frac{(1 + \beta) r_0 + R_{tc}}{r_0 + R_{te} + R_{tc}} \\ &= 20 + (1 + 99) 6.202 + 49.73 \frac{(1 + 99) 50 \text{ k}\Omega + 1.936 \text{ k}\Omega}{50 \text{ k}\Omega + 49.73 + 1.936 \text{ k}\Omega} \\ &= 5.425 \text{ k}\Omega\end{aligned}$$

The input resistance is

$$r_{in} = R_1 \parallel R_2 \parallel r_{ib} = 100 \text{ k}\Omega \parallel 120 \text{ k}\Omega \parallel 5.425 \text{ k}\Omega = 4.934 \text{ k}\Omega$$

AC Solution – Method 2

This is based on the r_0 approximations where the current through r_0 is neglected in calculating $i_{c(sc)}$ but not in calculating r_{ic} . In this case, $i_{c(sc)}$ is

$$i_{c(sc)} = \frac{\alpha}{r'_e + R_{te}} v_{tb} = \frac{0.99}{52.20 + 49.73} v_{tb} = \frac{v_{tb}}{103.0} = \frac{v_s}{111.3}$$

The output voltage is

$$v_o = -i_{c(sc)} r_{ic} \parallel R_{tc} = \frac{-v_s}{111.3} \times 97.76 \text{ k}\Omega \parallel 1.936 \text{ k}\Omega = -16.89 v_s$$

Thus the voltage gain is

$$\frac{v_o}{v_s} = -16.89$$

This is 0.12% higher than for the “full-blown” method. This illustrates how accurate the approximate method is.

The solutions for r_{out} and r_{in} are the same as for Method 1.