

**Common-Base Amplifier Example** using the  $r_0$  approximations.


$R_P(x,y) := \frac{x \cdot y}{x + y}$  Function for calculating parallel resistors.

$R_1 := 100000$      $R_2 := 120000$      $R_C := 4300$      $R_E := 5600$      $R_S := 100$      $R_L := 10000$


$V_{plus} := 15$      $V_{minus} := -15$      $V_{BE} := 0.65$      $V_T := 0.025$      $\beta := 99$      $\alpha := 0.99$

$r_x := 20$      $r_0 := 50000$

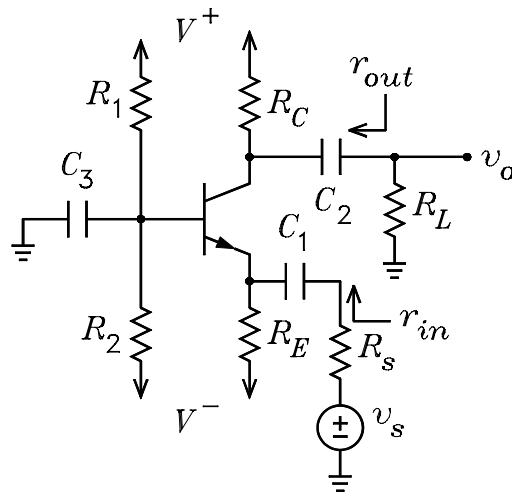$v_s := 1$     With  $v_s = 1$ , the voltage gain is equal to  $v_o$ .



**DC Bias Circuit**

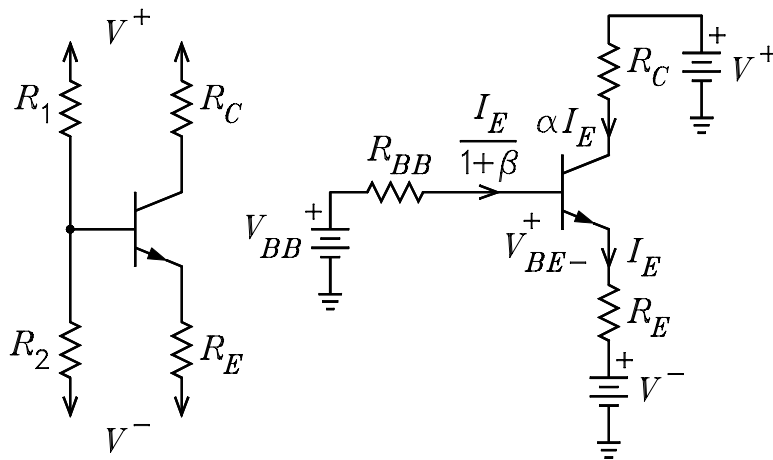

$$V_{BB} := \frac{V_{\text{plus}} \cdot R_2 + V_{\text{minus}} \cdot R_1}{R_1 + R_2} \quad V_{BB} = 1.364$$

$$R_{BB} := R_p(R_1, R_2) \quad R_{BB} = 5.455 \cdot 10^4$$

$$I_E := \frac{V_{BB} - V_{BE} - V_{\text{minus}}}{\frac{R_{BB}}{1 + \beta} + R_E} \quad I_E = 2.557 \cdot 10^{-3}$$

$$r_e := \frac{V_T}{I_E} \quad r_e = 9.777$$


### Test for Active Mode

$$V_C := V_{\text{plus}} - \alpha \cdot I_E \cdot R_C \quad V_C = 4.115$$

$$V_B := V_{BB} - \frac{I_E}{1 + \beta} \cdot R_{BB} \quad V_B = -0.031$$

$$V_{CB} := V_C - V_B \quad V_{CB} = 4.146 \quad \text{This is } > 0, \text{ thus active mode.}$$

### AC Signal Circuit

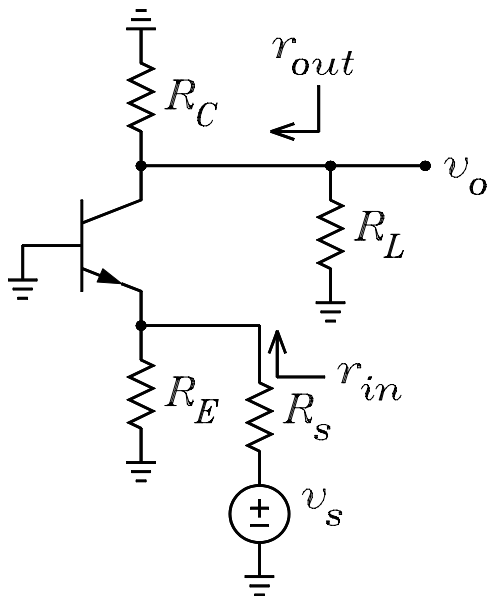



$$v_{te} := v_s \cdot \frac{R_E}{R_S + R_E} \quad v_{te} = 0.982$$

$$R_{te} := R_P(R_E, R_S) \quad R_{te} = 98.246$$

$$R_{tb} := 0$$

$$r'_e := \frac{R_{tb} + r_x}{1 + \beta} + r_e \quad r'_e = 9.977$$

### Circuits for $v_o$

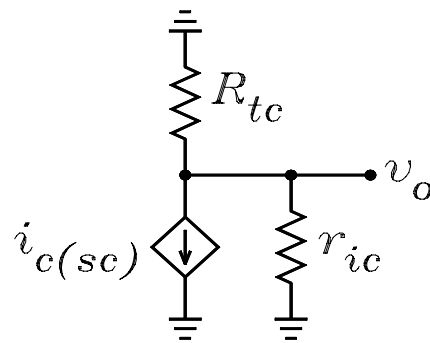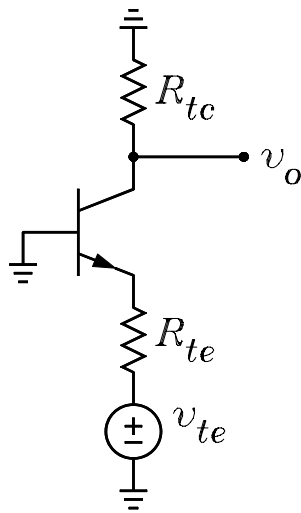

$$R_{tc} := R_P(R_C, R_L) \quad R_{tc} = 3.007 \cdot 10^3$$

$$i'_e := \frac{-v_{te}}{r'_e + R_{te}} \quad i'_e = -9.078 \cdot 10^{-3}$$


$$r_{ic} := \frac{r_0 + R_P(r'_e, R_{te})}{1 - \frac{\alpha \cdot R_{te}}{r'_e + R_{te}}} \quad r_{ic} = 4.938 \cdot 10^5$$

$$i_{csc} := \alpha \cdot i'_e \cdot v_{te} \quad i_{csc} = -8.83 \cdot 10^{-3}$$

$$v_o := -i_{csc} \cdot R_P(R_{tc}, r_{ic}) \quad v_o = 26.39$$


This is the voltage gain.

**Circuit for  $r_{out}$**

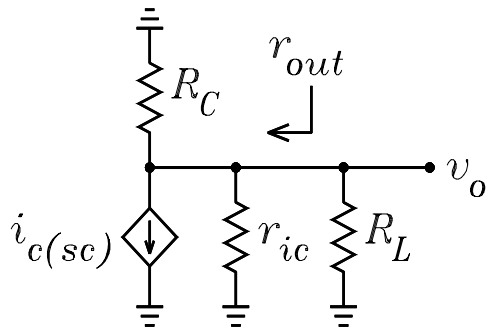

$$r_{out} := R P(R_C, r_{ic}) \quad r_{out} = 4.263 \cdot 10^3$$

**Circuit for  $r_{in}$**

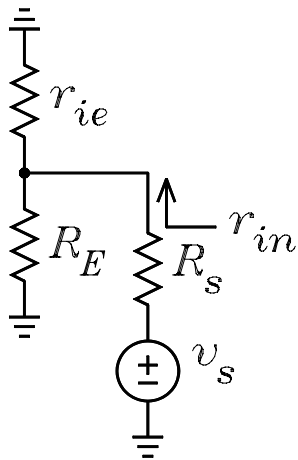

$$r_{ie} := r'_e \quad r_{ie} = 9.977$$

$$r_{in} := R P(r_{ie}, R_E) \quad r_{in} = 9.96$$