

ECE 3050 Analog Electronics Quiz 4

February 4, 2009

Professor Leach Last Name: _____ First Name: _____


Instructions. Print your name in the spaces above. Place a box around any answer. **Honor Code Statement:**
I have neither given nor received help on this quiz. Initials _____

The figure shows the signal circuit of a common-emitter amplifier. It is given that $R_s = 300\ \Omega$, $R_1 = 20\ \text{k}\Omega$, $R_2 = 10\ \text{k}\Omega$, $R_3 = 200\ \Omega$, $R_C = 24\ \text{k}\Omega$, $R_E = 2\ \text{k}\Omega$, $R_4 = 75\ \Omega$, and $R_L = 12\ \text{k}\Omega$. The BJT has the parameters and bias values $\beta = 99$, $\alpha = 0.99$, $r_x = 100\ \Omega$, $I_C = 1.5\ \text{mA}$, $V_{CE} = 10\ \text{V}$, $V_A = \infty$, and $V_T = 0.025\ \text{V}$.

$$r_\pi = \frac{V_T}{I_B} \quad r_e = \frac{V_T}{I_E} \quad g_m = \frac{I_C}{V_T} \quad r'_\pi = r_x + r_\pi + (1 + \beta) R_{te}$$

$$r_0 = \frac{V_A + V_{CE}}{I_C} \quad r'_e = \frac{R_{tb} + r_x}{1 + \beta} + r_e \quad r_{ic} = \frac{r_0 + r'_e \parallel R_{te}}{1 - \alpha \frac{R_{te}}{r'_e + R_{te}}}$$

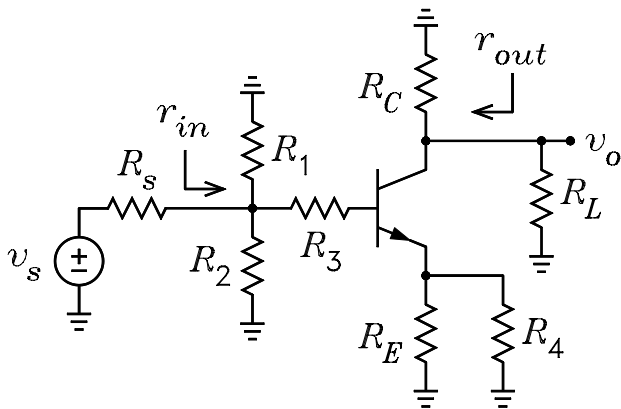- (a) Solve for v_{tb}/v_s , R_{tb} , and R_{te} . For the values given, why is r_0 an open circuit?
- (b) Solve for the voltage gain $A_v = v_o/v_s$.
- (c) Solve for the output resistance r_{out} .
- (d) Solve for the input resistance r_{in} .



Next page for solutions.

$$\begin{aligned}
R_s &:= 300 & R_1 &:= 20000 & R_2 &:= 10000 & R_3 &:= 200 & R_C &:= 24000 & R_E &:= 2000 \\
R_4 &:= 75 & R_L &:= 12000 & \beta &:= 99 & \alpha &:= 0.99 & r_x &:= 100 & I_C &:= 0.0015 \\
V_T &:= 0.025 & I_B &:= \frac{I_C}{\beta} & I_E &:= \frac{I_C}{\alpha} & g_m &:= \frac{I_C}{V_T} & r_\pi &:= \frac{V_T}{I_B} & r_e &:= \frac{V_T}{I_E} & v_s &:= 1
\end{aligned}$$

Part (a)

$$v_{tb} := v_s \cdot \frac{R_{p2}(R_1, R_2)}{R_s + R_{p2}(R_1, R_2)} \quad v_{tb} = 0.957 \quad R_{tb} := R_{p3}(R_s, R_1, R_2) + R_3 \quad R_{tb} = 4.871 \cdot 10^2$$

$$R_{te} := R_{p2}(R_E, R_4) \quad R_{te} = 72.289$$

Part (b) using the simplified π model

$$r'_\pi := r_x + r_\pi + (1 + \beta) \cdot R_{te} \quad r'_\pi = 8.979 \cdot 10^3$$

$$i_b := \frac{v_{tb}}{R_{tb} + r'_\pi} \quad i_b = 1.011 \cdot 10^{-4} \quad i'_c := \beta \cdot i_b \quad i'_c = 1.001 \cdot 10^{-2}$$

$$v_o := -i'_c \cdot R_{p2}(R_C, R_L) \quad v_o = -80.065 \quad \text{This is the voltage gain}$$

Part (b) using the simplified T model

$$r'_e := \frac{R_{tb} + r_x}{1 + \beta} + r_e \quad r'_e = 22.371$$

$$i'_e := \frac{v_{tb}}{r'_e + R_{te}} \quad i'_e = 1.011 \cdot 10^{-2} \quad i'_c := \alpha \cdot i'_e \quad i'_c = 1.001 \cdot 10^{-2}$$

$$v_o := -i'_c \cdot R_{p2}(R_C, R_L) \quad v_o = -80.065 \quad \text{This is the voltage gain}$$

Part (c)

$$r_{out} := R_C \quad r_{out} = 2.4 \cdot 10^4$$

Part (d)

$$r_{ib} := r'_\pi \quad r_{in} := R_{p3}(R_1, R_2, R_3 + r_{ib}) \quad r_{in} = 3.862 \cdot 10^3$$