

ECE 3050 Analog Electronics Quiz 5

February 11, 2009

Professor Leach Last Name: _____ First Name: _____


Instructions. Print your name in the spaces above. Place a box around any answer. **Honor Code Statement:**
I have neither given nor received help on this quiz. Initials _____

For the transistors in this problem, assume the parameters $\beta = 100$, $g_m = 1/25 \text{ S}$, $r_x = 0$, $r_\pi = 2.5 \text{ k}\Omega$, $r_e = 24.75 \Omega$, and $r_0 = \infty$ (an open circuit).

$$r_\pi = \frac{V_T}{I_B} \quad r_e = \frac{V_T}{I_E} \quad g_m = \frac{I_C}{V_T} \quad r'_\pi = r_x + r_\pi + (1 + \beta) R_{te}$$

$$r_0 = \frac{V_A + V_{CE}}{I_C} \quad r'_e = \frac{R_{te} + r_x}{1 + \beta} + r_e \quad r_{ic} = \frac{r_0 + r'_e \parallel R_{te}}{1 - \alpha \frac{R_{te}}{r'_e + R_{te}}}$$

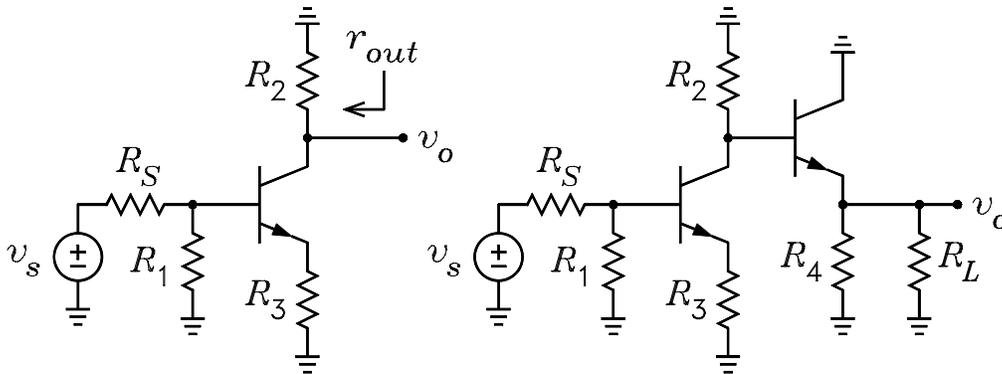- (a) The figure on the left shows the signal circuit of a CE amplifier. It is given that $R_S = 1 \text{ k}\Omega$, $R_1 = 10 \text{ k}\Omega$, $R_2 = 3 \text{ k}\Omega$, and $R_3 = 75 \Omega$. Solve for the small-signal Thévenin equivalent circuit seen looking into its output terminal. The circuit should be in the form of a voltage source $A_1 v_s$ in series with a resistor r_{out} , where you must give numerical values for A_1 and r_{out} .
- (b) A load resistor $R_L = 300 \Omega$ is connected from the output to ground. Use the Thévenin equivalent circuit found in part (a) to solve for the new value of v_o .
- (c) The figure on the right shows the signal circuit of the CE amplifier with a CC stage added between the CE stage and the 300Ω load resistor. If $R_4 = 2 \text{ k}\Omega$, solve for the new value of v_o .
- (d) Why does the voltage gain increase with the addition of a CC stage which has a voltage gain by itself that is less than unity?



Over for solutions.

Quiz 5

$$R_S := 1000 \quad R_1 := 10000 \quad R_2 := 3000 \quad R_3 := 75 \quad R_4 := 2000 \quad R_L := 300$$

$$\beta := 100 \quad g_m := \frac{1}{25} \quad r_\pi := 2500 \quad r_e := 24.75 \quad v_s := 1$$

Part (a)

First Solution:

$$r'_\pi := r_\pi + (1 + \beta) \cdot R_3 \quad r'_\pi = 1.008 \cdot 10^4 \quad v_{tb1} := v_s \cdot \frac{R_1}{R_S + R_1} \quad v_{tb1} = 0.909$$

$$R_{tb1} := R_{p2}(R_S, R_1) \quad R_{tb1} = 9.091 \cdot 10^2 \quad i_{b1} := \frac{v_{tb1}}{R_{tb1} + r'_\pi} \quad i_{b1} = 8.276 \cdot 10^{-5}$$

$$i'_{c1} := \beta \cdot i_{b1} \quad i'_{c1} = 8.276 \cdot 10^{-3} \quad v_{o1} := -i'_{c1} \cdot R_2 \quad v_{o1} = -24.829$$

$$r_{out} := R_2 \quad r_{out} = 3 \cdot 10^3$$

Second Solution:

$$r'_{e1} := \frac{R_{tb1}}{1 + \beta} + r_e \quad r'_{e1} = 33.751 \quad i'_{e1} := \frac{v_{tb1}}{r'_{e1} + R_3} \quad i'_{e1} = 8.359 \cdot 10^{-3}$$

$$i'_{c1} := \frac{\beta}{1 + \beta} \cdot i'_{e1} \quad i'_{c1} = 8.277 \cdot 10^{-3} \quad v_{o1} := -i'_{c1} \cdot R_2 \quad v_{o1} = -24.83$$

Part (b)

$$v_{o2} := v_{o1} \cdot \frac{R_L}{r_{out} + R_L} \quad v_{o2} = -2.257$$

Part (c)

$$r'_{e2} := \frac{r_{out}}{1 + \beta} + r_e \quad r'_{e2} = 54.453 \quad v_{o3} := v_{o1} \cdot \frac{R_{p2}(R_4, R_L)}{r'_{e2} + R_{p2}(R_4, R_L)} \quad v_{o3} = -20.542$$

Part (d)

Because the CC stage has a much lower output resistance than the CE stage.