

ECE 3050 Analog Electronics Quiz 6

February 18, 2009

Professor Leach

Name _____

Instructions. Print your name in the space above. **Honor Code:** *I have neither given nor received help on this quiz.* Initials _____


1. The figure shows a BJT diff amp. It is given that $V^+ = +24\text{ V}$, $V^- = -24\text{ V}$, $R_B = 150\ \Omega$, $R_E = 75\ \Omega$, $R_C = 24\text{ k}\Omega$, $R_Q = 23\text{ k}\Omega$, $V_T = 0.025\text{ V}$, $V_A = \infty$, $V_{BE} = 0.65\text{ V}$, $\beta = 74$, $I_E = 0.5\text{ mA}$, $r_e = 50\ \Omega$, $r_x = 30\ \Omega$, and $r'_e = 52.4\ \Omega$.

$$r_e = \frac{V_T}{I_E} = 50\ \Omega \quad r'_e = \frac{R_B + r_x}{1 + \beta} + r_e = 52.4\ \Omega \quad g_m = \frac{I_C}{V_T} = 0.01973\text{ S} \quad r_\pi = \frac{V_T}{I_B} = 3.75\text{ k}\Omega$$

$$r'_\pi = r_x + r_\pi + (1 + \beta) R_{te} \quad r_0 = \frac{V_A + V_{CE}}{I_C} = \infty \quad r_{ic} = \frac{r_0 + r'_e || R_{te}}{1 - \alpha \frac{R_{te}}{r'_e + R_{te}}} = \infty$$

Before starting the problem, note that the answers for some of the numerical calculations are given with the above formulas.

- For $v_{i2} = 0$, solve for the small-signal Thévenin resistance R_{te1} looking out of the emitter of Q_1 .
- For $v_{i2} = 0$, solve for the small-signal voltage gain v_{o1}/v_{i1} .
- For $v_{i1} = 0$, solve for the small-signal voltage gain v_{o1}/v_{i2} . If you are clever, it is possible to make use of the solution for v_{o1}/v_{i1} to simplify the numerical calculations.
- Make use of the solutions from the parts above to write the solutions for the small-signal gains v_{o2}/v_{i2} and v_{o2}/v_{i1} .

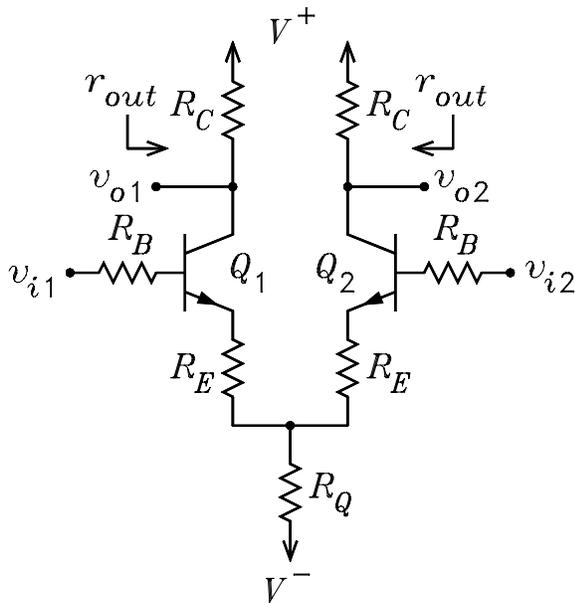

$$V_T := 0.025 \quad r_x := 30 \quad V_p := 24 \quad R_C := 24000 \quad \beta := 74 \quad \alpha := \frac{\beta}{1 + \beta} \quad \alpha = 0.987$$

$$V_n := -24 \quad R_B := 150 \quad R_E := 75 \quad R_Q := 23000 \quad V_{BE} := 0.65$$

$$I_E := \frac{0 - V_{BE} - (V_n)}{\frac{R_B}{\beta} + \frac{(R_E + 2 \cdot R_Q)}{\alpha}} \quad I_E = 5 \cdot 10^{-4} \quad V_C := V_p - \alpha \cdot I_E \cdot R_C \quad V_C = 12.16$$

$$r_e := \frac{V_T}{I_E} \quad r_e = 50 \quad r'_e := \frac{R_B + r_x}{1 + \beta} + r_e \quad r'_e = 52.4$$

$$I_B := \frac{\alpha \cdot I_E}{\beta} \quad r_\pi := \frac{V_T}{I_B} \quad r_\pi = 3.75 \cdot 10^3 \quad I_C := \alpha \cdot I_E \quad g_m := \frac{I_C}{V_T} \quad g_m = 1.973 \cdot 10^{-2}$$

$$g_m^{-1} = 50.675 \quad R_{te} := R_E + R_{p2}(R_Q, R_E + r'_e) \quad R_{te} = 2.017 \cdot 10^2$$

$$A_{v11} := \frac{\alpha}{r'_e + R_{te}} \cdot (-R_C) \quad A_{v11} = -93.193$$

$$A_{v12} := -A_{v11} \cdot \frac{R_Q}{R_Q + r'_e + R_E} \quad A_{v12} = 92.679$$

$$A_{v22} := A_{v11} \quad A_{v22} = -93.193 \quad A_{v21} := A_{v12} \quad A_{v21} = 92.679$$