

ECE 3050 Analog Electronics Quiz 10


March 25, 2009

Professor Leach

Name _____

Instructions. Print your name in the space above. **Honor Code:** *I have neither given nor received help on this quiz.* Initials _____

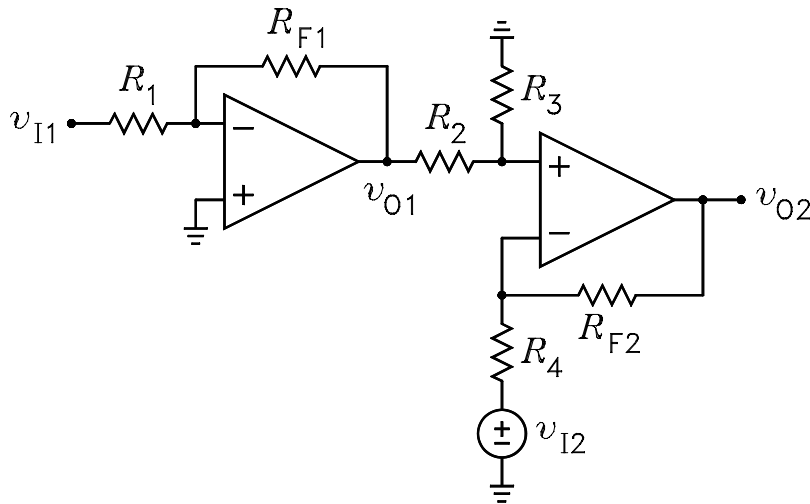- The figure shows an op amp circuit. It is given that $R_1 = 20\text{ k}\Omega$, $R_2 = 4\text{ k}\Omega$, $R_3 = 6\text{ k}\Omega$, $R_4 = 3\text{ k}\Omega$, $R_{F1} = 180\text{ k}\Omega$, $R_{F2} = 30\text{ k}\Omega$.
 - Solve for v_{O1} as a function of v_{I1} .
 - Solve for v_{O2} as a function of v_{I1} and v_{I2} .




$$R_1 := 20000 \quad R_2 := 4000 \quad R_3 := 6000 \quad R_4 := 3000 \quad R_{F1} := 180000 \quad R_{F2} := 30000$$

$$A_{11} := \frac{-R_{F1}}{R_1} \quad A_{11} = -9 \quad A_{12} := A_{11} \cdot \frac{R_3}{R_2 + R_3} \cdot \left(1 + \frac{R_{F2}}{R_4}\right) \quad A_{12} = -59.4$$

$$A_{22} := \frac{-R_{F2}}{R_4} \quad A_{22} = -10 \quad v_{O1} = A_{11} \cdot v_{I1} \quad v_{O2} = A_{12} \cdot v_{I1} + A_{22} \cdot v_{I2}$$

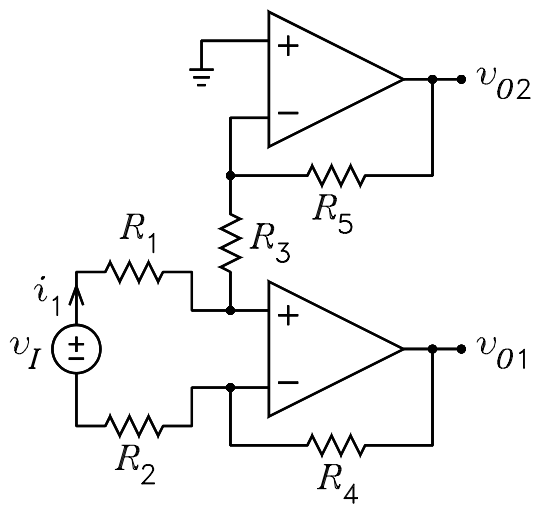- The figure shows an op amp circuit. It is given that $R_1 = R_2 = 10\text{ k}\Omega$, $R_3 = R_4 = 40\text{ k}\Omega$ and $v_I = 2\text{ V}$.
 - Solve for i_1 .
 - Solve for v_{O1} .
 - Solve for R_5 such that $v_{O2} = -v_{O1}$.



$$\begin{aligned}
 R_1 &:= 10000 & R_2 &:= 10000 & R_3 &:= 40000 & R_4 &:= 40000 & v_I &:= 2 \\
 i_1 &:= \frac{v_I}{R_1 + R_2} & i_1 &= 1 \cdot 10^{-4} & v_{O1} &:= i_1 \cdot (R_3 + R_4) & v_{O1} &= 8 \\
 v_{O2} &:= -v_{O1} & R_5 &:= \frac{-v_{O2}}{i_1} & R_5 &= 8 \cdot 10^4
 \end{aligned}$$