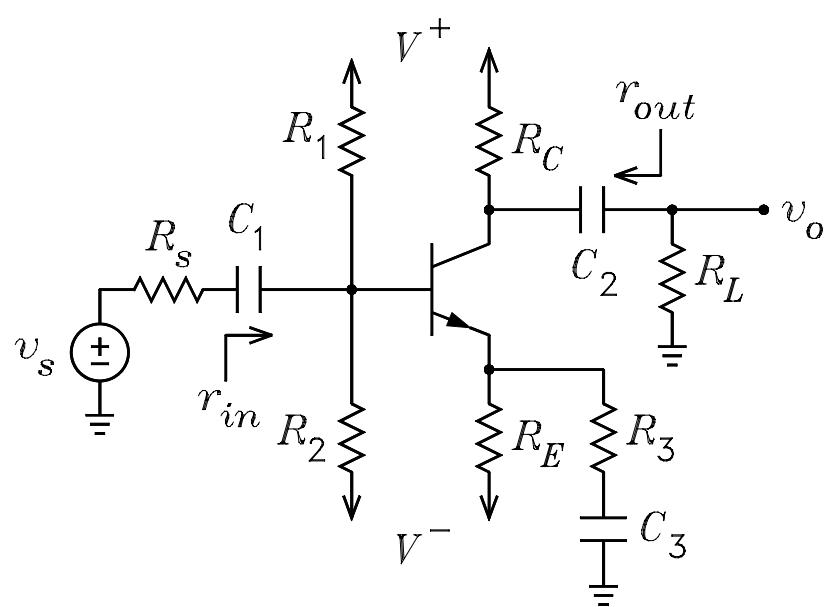


## Common-Emitter Amplifier Example


$$R_P(x,y) := \frac{x \cdot y}{x + y} \quad \text{Function for calculating parallel resistors.}$$

$$\begin{aligned} R_1 &:= 100000 & R_2 &:= 120000 & R_C &:= 4300 & R_E &:= 5600 & R_S &:= 5000 & R_L &:= 10000 \\ V_p &:= 15 & V_m &:= -15 & V_{BE} &:= 0.65 & V_T &:= 0.025 & \beta &:= 99 & \alpha &:= 0.99 \\ r_x &:= 20 & r_0 &:= 50000 & R_3 &:= 100 \end{aligned}$$

$v_s := 1$       With  $v_s = 1$ , the voltage gain is equal to  $v_o$ .



DC Bias Solution

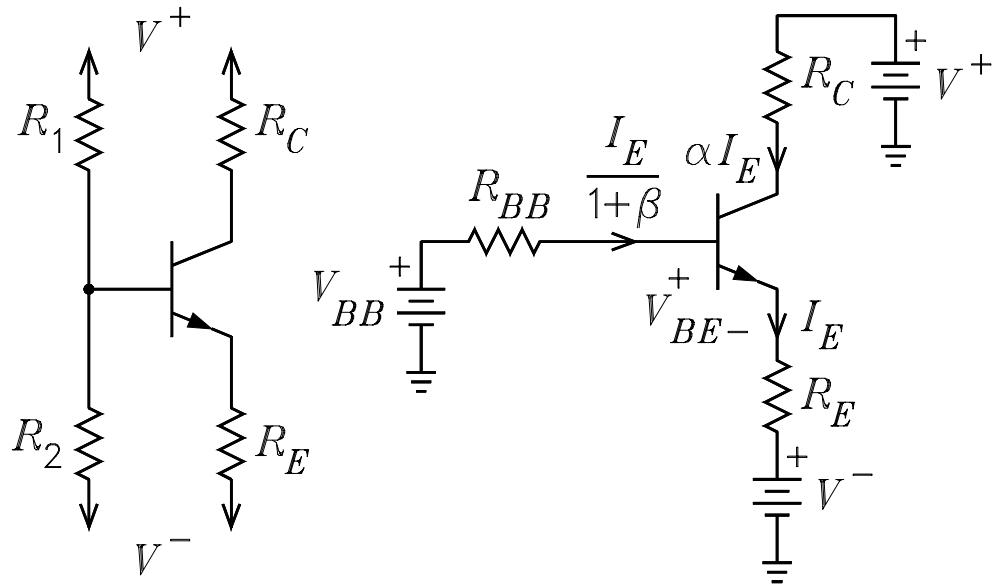

$$V_{BB} := \frac{V_p \cdot R_2 + V_m \cdot R_1}{R_1 + R_2} \quad V_{BB} = 1.3636$$

$$R_{BB} := R_P(R_1, R_2) \quad R_{BB} = 5.4545 \cdot 10^4$$

$$I_E := \frac{V_{BB} - V_{BE} - V_m}{\frac{R_{BB}}{1+\beta} + R_E} \quad I_E = 2.557 \cdot 10^{-3}$$



$$V_C := V_p - \alpha \cdot I_E \cdot R_C \quad V_C = 4.1151$$

$$V_B := V_{BE} + I_E \cdot R_E + V_m \quad V_B = -0.0311$$

$$V_C - V_B = 4.1461 \quad \text{Thus active mode.}$$

$$r_e := \frac{V_T}{I_E} \quad r_e = 9.7773$$

Exact AC Solution

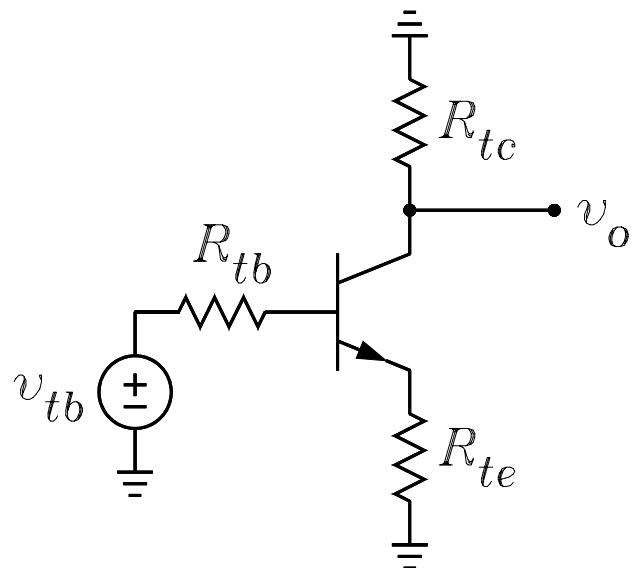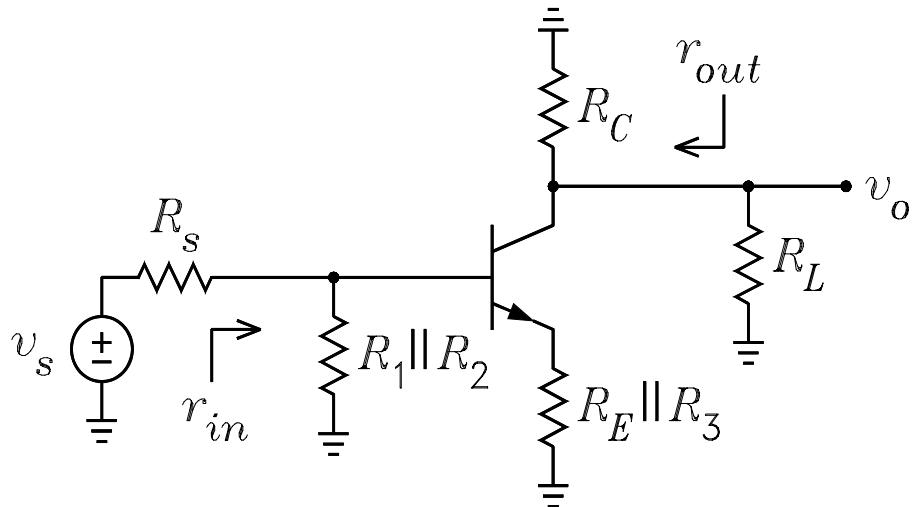


$$v_{tb} := v_s \cdot \frac{R_P(R_1, R_2)}{R_S + R_P(R_1, R_2)} \quad v_{tb} = 0.916$$

$$R_{tb} := R_P(R_S, R_P(R_1, R_2)) \quad R_{tb} = 4.5802 \cdot 10^3$$

$$R_{te} := R_P(R_E, R_3) \quad R_{te} = 98.2456$$

$$r'_e := \frac{R_{tb} + r_x}{1 + \beta} + r_e \quad r'_e = 55.7788$$
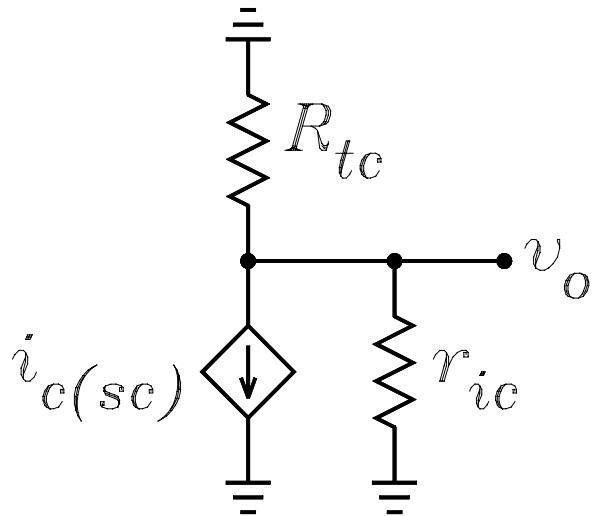
$$R_{tc} := R_P(R_C, R_L) \quad R_{tc} = 3.007 \cdot 10^3$$




$$r_{ic} := \frac{r_0 + R_P(r'_e, R_{te})}{1 - \frac{\alpha \cdot R_{te}}{r'_e + R_{te}}} \quad r_{ic} = 1.3577 \cdot 10^5$$

$$i_{csc} := \frac{v_{tb}}{r'_e + R_P(R_{te}, r_0)} \cdot \left( \alpha - \frac{R_{te}}{R_{te} + r_0} \right) \quad i_{csc} = 5.8835 \cdot 10^{-3}$$

$$v_o := -i_{csc} \cdot R_P(R_C, R_P(r_{ic}, R_L)) \quad v_o = -17.3084$$


$$A_v := v_o \quad A_v = -17.3084 \quad \text{This is the voltage gain.}$$

Circuit for  $r_{out}$ :

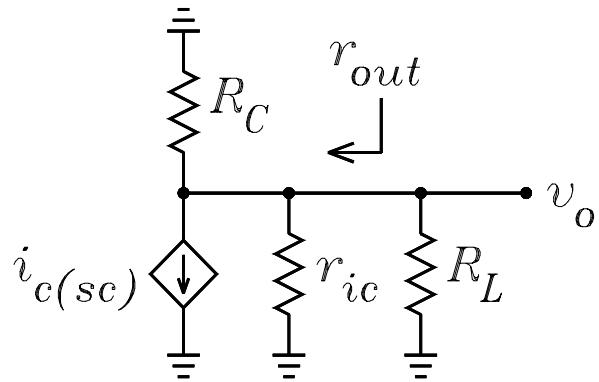

$$r_{out} := R_P(R_C, r_{ic}) \quad r_{out} = 4.168 \cdot 10^3$$

Circuit for  $r_{in}$ :

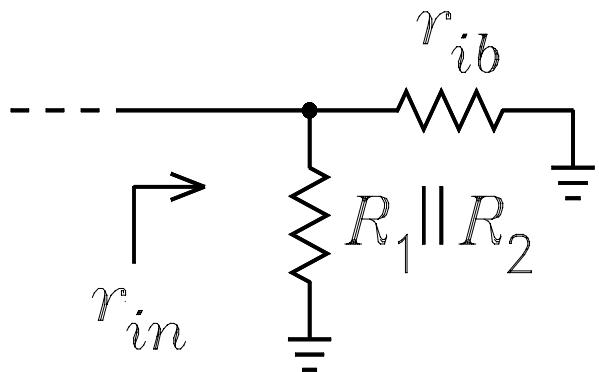

$$r_{ib} := r_x + (1 + \beta) \cdot (r_e + R_P(R_{te}, r_0 + R_{tc})) - \frac{\beta \cdot R_{te} \cdot R_{tc}}{R_{tc} + r_0 + R_{te}}$$

$$r_{ib} = 1.0253 \cdot 10^4$$

$$r_{in} := R_P(r_{ib}, R_P(R_1, R_2)) \quad r_{in} = 8.6309 \cdot 10^3$$

Exact AC solution based on the pi model that is the subject of a homework problem.

$$r_\pi := (1 + \beta) \cdot r_e \quad R' := R_{tb} + r_x + r_\pi$$

$$A_v := -\frac{\frac{\beta}{R'} - \frac{1+\beta}{R'}}{\frac{1}{r_0} + \frac{\beta}{R'} - \frac{1+\beta}{R'} + \frac{1}{R_{te}} + \frac{1}{r_0}}$$

$$A_v = -18.895 \quad \text{This is } v_o/v_{tb}.$$

$$G_{mb}$$

$$v_o := A_v \cdot \frac{R_P(R_1, R_2)}{R_S + R_P(R_1, R_2)} \quad v_o = -17.3084 \quad \text{Same gain as calculated using } G_{mb} \text{ and } r_{ic} \text{ above.}$$

The following solution is based on the  $r_0$  approximations where  $r_0$  is neglected in calculating  $i_{csc}$  but not neglected in calculating  $r_{ic}$ .

$$G_{mb} := \frac{a}{r'_e + R_{te}}$$

$$i_{csc} := v_{tb} \cdot G_{mb} \quad i_{csc} = 5.8878 \cdot 10^{-3}$$

$$v_o := -i_{csc} \cdot R_P(R_C, R_P(r_{ic}, R_L)) \quad v_o = -17.3211$$

$$A_v := v_o \quad A_v = -17.3211 \quad \text{This is the voltage gain. It is 0.075% lower than the exact solutions found above.}$$

$$r_{out} := R_P(r_{ic}, R_C) \quad r_{out} = 4.168 \cdot 10^3$$

$$r_{ib} := r_x + (1 + \beta) \cdot (r_e + R_{te}) \quad r_{ib} = 1.0822 \cdot 10^4$$

$$r_{in} := R_P(r_{ib}, R_P(R_1, R_2)) \quad r_{in} = 9.0305 \cdot 10^3$$

Approximate Solution 1 using the equation  $i_c = g_m \cdot (v_b - v_e)$

$$i_c = g_m \cdot (v_b - v_e)$$

Assume  $r_x := 0$  and  $r_0$  is infinity, i.e. an open circuit.

$$g_m := \frac{\alpha \cdot I_E}{V_T} \quad g_m = 0.1013 \quad r_{ib} := (1 + \beta) \cdot (r_e + R_P(R_E, R_3)) \quad r_{ib} = 1.0802 \cdot 10^4$$

$$v_b := v_s \cdot \frac{R_P(r_{ib}, R_P(R_1, R_2))}{R_S + R_P(r_{ib}, R_P(R_1, R_2))} \quad v_b = 0.6433 \quad r_\pi := (1 + \beta) \cdot r_e \quad r_\pi = 977.7264$$

$$r_{ib} := r_\pi + (1 + \beta) \cdot R_{te} \quad r_{ib} = 1.0802 \cdot 10^4$$

$$A_v := \frac{-R_P(R_1, R_2)}{R_S + R_P(R_1, R_2)} \cdot \frac{r_{ib}}{R_{tb} + r_{ib}} \cdot \frac{g_m \cdot R_{tc}}{1 + \frac{g_m \cdot R_{te}}{\alpha}} \quad A_v = -17.7277$$

$$r_{in} := R_P(r_{ib}, R_P(R_1, R_2)) \quad r_{in} = 9.0166 \cdot 10^3$$

$$r_{out} := R_C \quad r_{out} = 4.3 \cdot 10^3$$

Approximate Solution 2 using the equation  $i_c = \beta \cdot i_b$

Again, assume  $r_x := 0$  and  $r_0$  is infinity, i.e. an open circuit.

$$A_v := \frac{-R_P(R_1, R_2)}{R_S + R_P(R_1, R_2)} \cdot \frac{\beta \cdot R_{tc}}{R_{tb} + r_{ib}} \quad A_v = -17.7277$$

This is the same as in Approximate Solution 1 and is simpler.

$$r_{in} := R_P(r_{ib}, R_P(R_1, R_2)) \quad r_{in} = 9.0166 \cdot 10^3$$

$$r_{out} := R_C \quad r_{out} = 4.3 \cdot 10^3$$