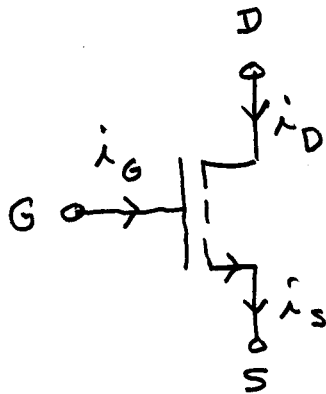



1-05/21/03

The MOSFET

Enhancement
Device



Depletion
Device

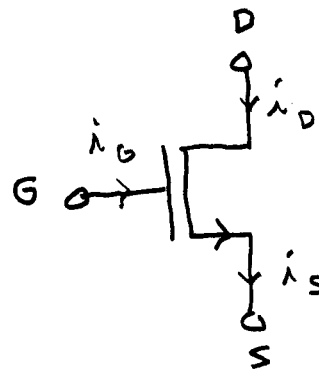

For either device, the drain current is given by

$$i_D = \frac{\mu C_{ox}}{2} \frac{W}{L} (1 + \lambda v_{DS}) (v_{GS} - v_{T0})^2$$

μ = majority carrier mobility

C_{ox} = gate oxide capacitance per unit area

W = channel width

L = channel length

2-05/21/03

λ = channel length modulation parameter (reciprocal of the Early voltage)

V_{T0} = threshold voltage

It is common to define k' as

$$k' = \mu C_{ox}$$

so that i_D can be written

$$i_D = \frac{k'}{2} \frac{W}{L} (1 + \lambda V_{DS}) (V_{GS} - V_{T0})^2$$

This equation assumes the active or saturation mode. For the device to be in this mode, we must have

$$V_{DS} > V_{GS} - V_{T0}$$

3 - 05 / 21 / 03

For the enhancement mode device $V_{T0} > 0$. For the depletion mode device, $V_{T0} < 0$.

To simplify the equation for i_D , let us define

$$K_0 = \frac{K'}{2} \frac{W}{L}$$

$$K = K_0 (1 + \lambda V_{DS})$$

$$\Rightarrow i_D = K (V_{GS} - V_{T0})^2$$


Because the gate is insulated, $i_G = 0$. Thus $i_S = i_D$.

The MOSFET Transfer Characteristics

The transfer characteristics are plots of i_D versus V_{GS} for $V_{DS} = \text{constant}$. Let us assume an enhancement mode device

4-05/21/03

for which $V_{T0} > 0$.

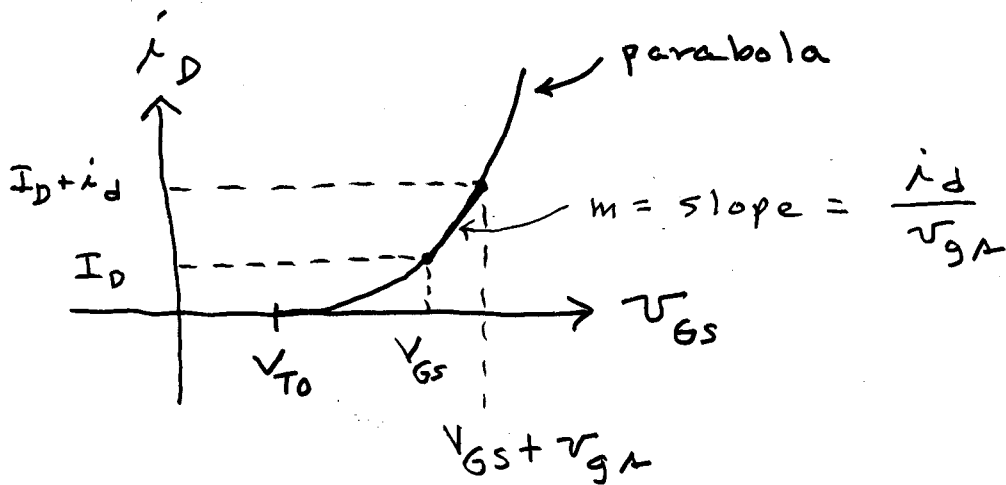

Draw a tangent line at the point (V_{GS}, I_D) . The slope of the line can be used to relate changes in i_D to changes in v_{GS} .

$$m = \frac{\partial I_D}{\partial V_{GS}} = 2K(V_{GS} - V_{T0})$$

$$= 2K \sqrt{\frac{I_D}{K}}$$

$$= 2\sqrt{KI_D}$$


$$\Rightarrow i_D = 2\sqrt{KI_D} v_{gs}$$

5 - 05/21/03

The MOSFET Output Characteristics

The output characteristics are plots of i_D versus v_{DS} for $v_{GS} = \text{constant}$.
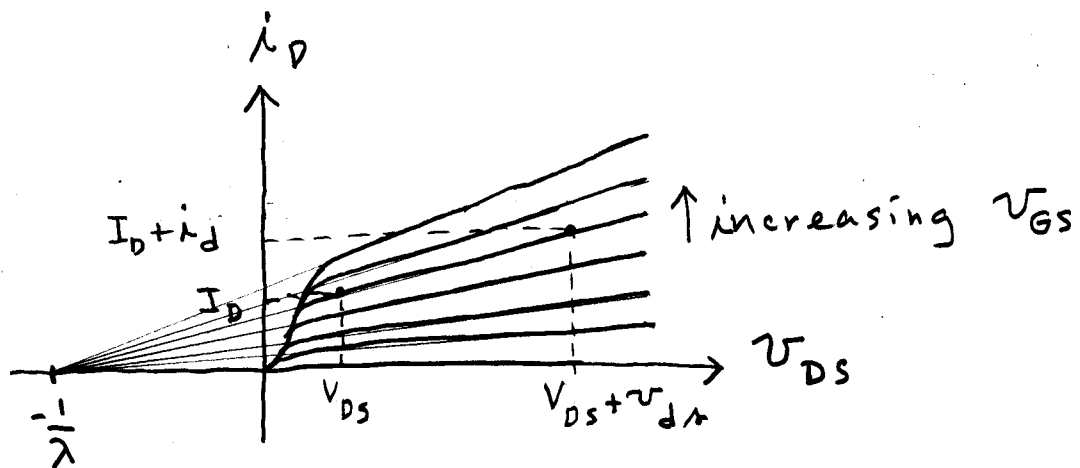
$$i_D = K_0 (1 + \lambda v_{DS}) (v_{GS} - V_{T0})^2$$



Draw a tangent line at the point (v_{DS}, I_D) . The slope of the line can be used to relate changes in i_D to changes in v_{DS} .

$$m = \frac{\partial I_D}{\partial v_{DS}} = K_0 \lambda (v_{GS} - V_{T0})^2$$

6-05/21/03

$$= \lambda \frac{I_D}{1 + \lambda V_{DS}} = \frac{I_D}{\frac{1}{\lambda} + V_{DS}}$$

$$\Rightarrow i_D = \frac{I_D}{\frac{1}{\lambda} + V_{DS}} v_{DA}$$

Thus, in general, we have

$$i_D = 2\sqrt{K I_D} v_{gA} + \frac{I_D}{\frac{1}{\lambda} + V_{DS}} v_{DA}$$

Let us define

$$g_m = 2\sqrt{K I_D} \quad r_o = \frac{\frac{1}{\lambda} + V_{DS}}{I_D}$$

$$\Rightarrow i_D = g_m v_{gA} + \frac{v_{DA}}{r_o}$$

Because the gate is insulated, it follows that

$$i_g = 0 \quad i_A = i_g + i_D = i_D$$


7-05/21/03

The Hybrid- π Model

The basic equations are

$$i_d = g_m v_{gs} + \frac{v_{ds}}{r_o} \quad i_g = 0$$

We can draw the model as follows:

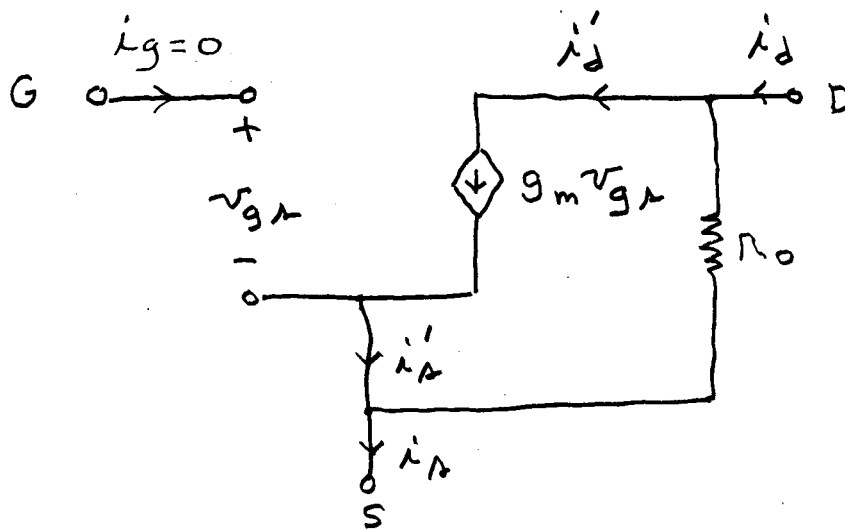

The T Model

The T model puts a resistor in series with the i_s branch which has the same voltage across it as v_{gs} in the hybrid- π model.

8-05/21/03

We can write

$$i'_A = i'_D = g_m v_{gA}$$


$$\Rightarrow v_{gA} = i'_A \frac{1}{g_m}$$

Let us define the resistance

$$r_A = \frac{1}{g_m}$$

$$\Rightarrow v_{gA} = i'_A r_A$$

Thus the T model is

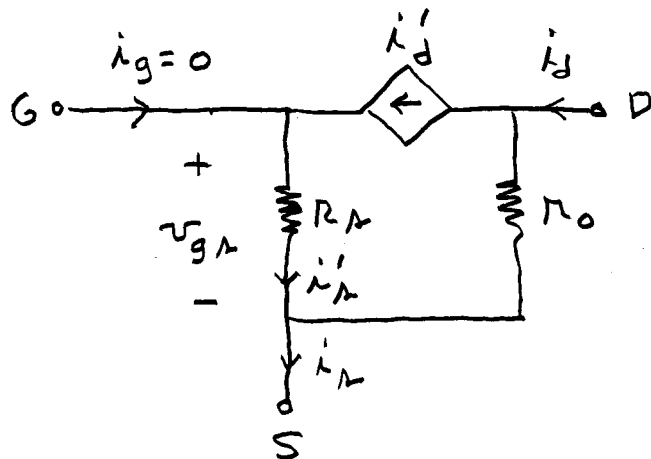

$$i'_D = i'_A = \frac{v_{gA}}{r_A} = g_m v_{gA}$$

Thus i'_D and i'_A are the same

9-05/21/03

as for the hybrid- π model. Also $i_g = i'_A - i'_D = 0$ which is the same as for the hybrid- π model.


BJT/MOSFET Comparison

	BJT	MOSFET
r_x	> 0	$= 0$
g_m	I_C/V_T	$2\sqrt{K I_D}$
r_{π}	V_T/I_B	∞
r_o	$\frac{V_A + V_{CE}}{I_C}$	$\frac{1/\lambda + V_{DS}}{I_D}$
β	I_C/I_B	∞
α	I_C/I_E	1
	$r_e = V_T/I_E$	$r_A = 1/g_m$

The BJT Bias Equation

Replace the dc circuits looking out of the collector, base, and emitter leads with Thévenin equivalents.

10-05/21/03

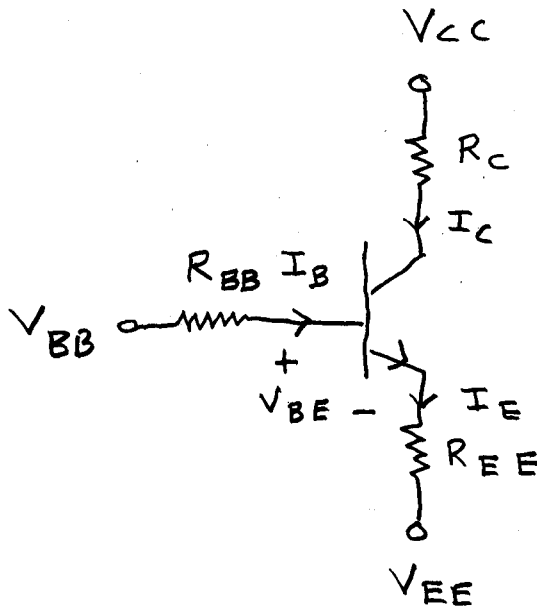

The loop equation between the V_{BB} and V_{EE} nodes is

$$V_{BB} - V_{EE} = I_B R_{BB} + V_{BE} + I_E R_{EE}$$

Suppose we desire I_C . We use

$$I_B = \frac{I_C}{\beta} \quad I_E = \frac{I_C}{\alpha}$$

$$\Rightarrow V_{BB} - V_{EE} = I_C \frac{R_{BB}}{\beta} + V_{BE} + I_C \frac{R_{EE}}{\alpha}$$


$$\Rightarrow I_C = \frac{V_{BB} - V_{EE} - V_{BE}}{\frac{R_{BB}}{\beta} + \frac{R_{EE}}{\alpha}}$$

11-05/21/03

In a similar way, we obtain
for I_E

$$I_E = \frac{V_{BB} - V_{EE} - V_{BE}}{\frac{R_{BB}}{1+\beta} + R_{EE}}$$

Example 1

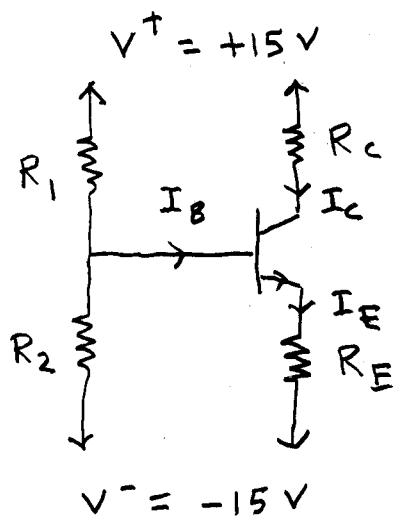

$$R_1 = 100 \text{ k}\Omega$$

$$R_2 = 120 \text{ k}\Omega$$

$$R_E = 5.6 \text{ k}\Omega$$

$$\beta = 99$$

$$\alpha = \frac{\beta}{1+\beta} = 0.99$$

$$V_{BE} = 0.65 \text{ V}$$


Solve for I_E

$$V_{BB} = V^+ \frac{R_2}{R_1 + R_2} + V^- \frac{R_1}{R_1 + R_2} = 1.3636 \text{ V}$$

$$R_{BB} = R_1 \parallel R_2 = 54.45 \text{ k}\Omega$$

12-05/21/03

The equivalent circuit is

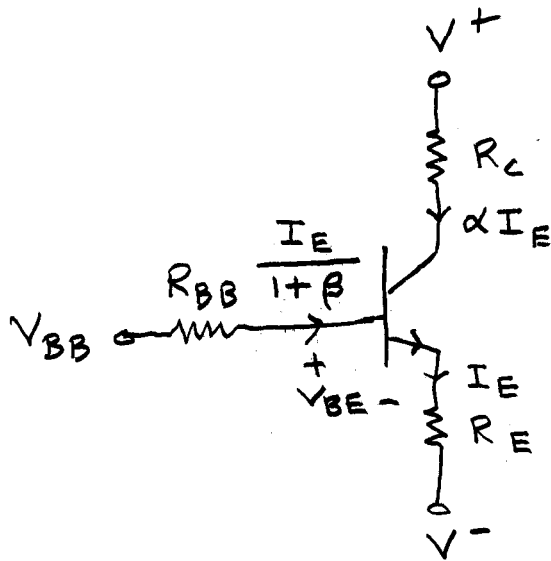

$$V_{BB} - V^- = \frac{I_E}{1+\beta} R_{BB} + V_{BE} + I_E R_E$$

$$\Rightarrow I_E = \frac{V_{BB} - V^- - V_{BE}}{\frac{R_{BB}}{1+\beta} + R_E} = 2.557 \text{ mA}$$

Our solution assumes the active mode. This requires $V_{CB} > 0$.

$$V_C = V^+ - \alpha I_E R_C = 4.1151 \text{ V}$$


$$V_B = V_E + V_{BE} = V^- + I_E R_E + V_{BE} = -0.0311 \text{ V}$$

13-05/21/03

$$\Rightarrow V_{CB} = V_C - V_B = 4.1461 \text{ V}$$

Because $V_{CB} > 0$, the BJT is in the active mode.

Example 2

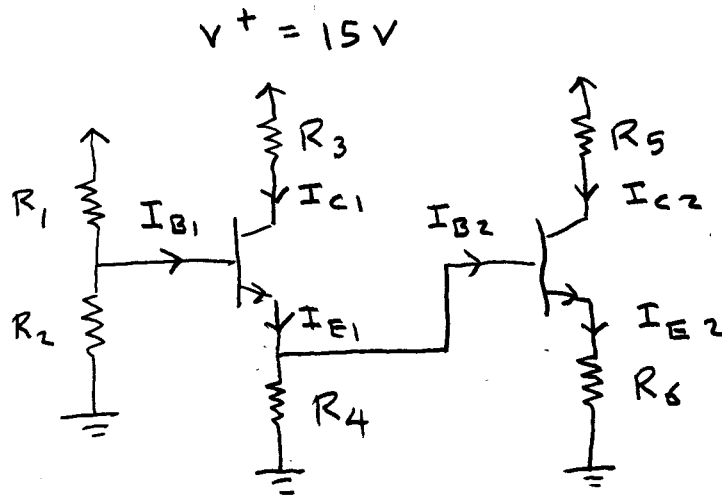

$$R_1 = 20 \text{ k}\Omega, R_2 = 10 \text{ k}\Omega, R_3 = R_4 = 3 \text{ k}\Omega$$

$$R_5 = R_6 = 2 \text{ k}\Omega, V_{BE1} = V_{BE2} = 0.65 \text{ V}$$

$$\beta_1 = \beta_2 = 100, \alpha_1 = \alpha_2 = \frac{100}{101}$$

$$V_{BB1} = V^+ \frac{R_2}{R_1 + R_2} \quad R_{BB1} = R_1 \parallel R_2$$

$$V_{EE1} = -I_{B2} R_4 = -\frac{I_{C2}}{\beta} R_4 \quad R_{EE1} = R_4$$

$$V_{BB2} = I_{E1} R_4 = \frac{I_{C1}}{\alpha} R_4 \quad R_{BB2} = R_4$$

14-05/21/03

Thus the two bias equations are

$$V + \frac{R_2}{R_1 + R_2} + \frac{I_{C2}}{\beta} R_4 = \frac{I_{C1}}{\beta} R_1 \parallel R_2 + V_{BE} + \frac{I_{C1}}{\alpha} R_4$$

$$\frac{I_{C1}}{\alpha} R_4 = \frac{I_{C2}}{\beta} R_4 + V_{BE} + \frac{I_{C2}}{\alpha} R_6$$

It is left as a homework exercise to solve these simultaneously to obtain

$$I_{C1} = 1.41 \text{ mA} \quad I_{C2} = 1.74 \text{ mA}$$

It is also left as an exercise to verify that $V_{CB} > 0$ for both transistors.