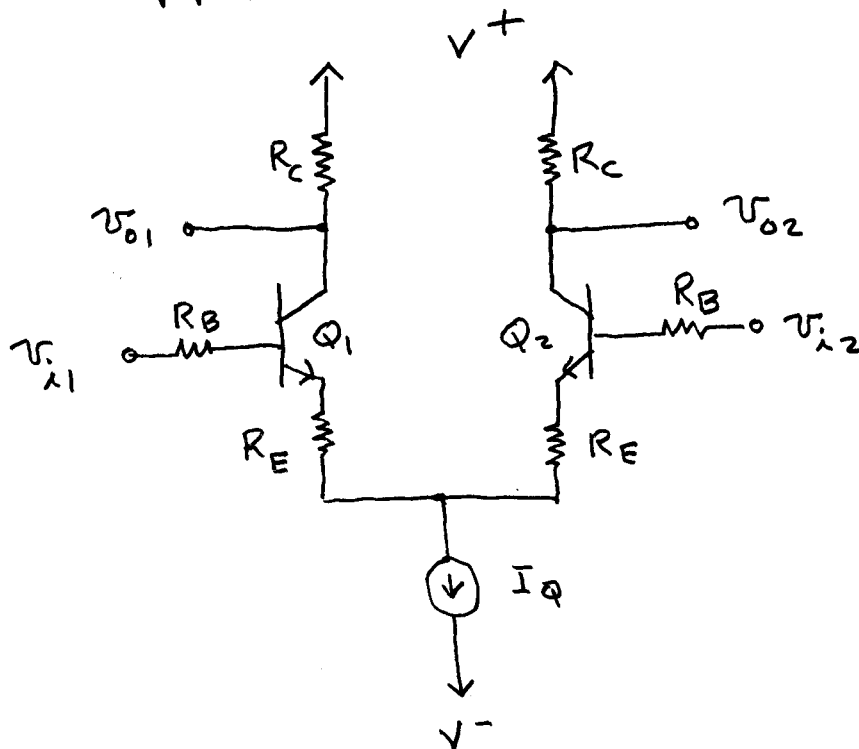


1 - 6/13/03

The BJT Diff Amp with Current Source
Tail Supply



DC Solution - set $v_{i1} = v_{i2} = 0$
Assume Q_1 and Q_2 are identical.

$$\Rightarrow I_{E1} = I_{E2} = \frac{I_Q}{2}$$


$$\begin{aligned} V_{CB} = V_C - V_B &= \left(V^+ - \alpha \frac{I_Q}{2} R_C \right) \\ &\quad - \left(- \frac{I_Q}{2(1+\beta)} R_B \right) \\ &= V^+ - \frac{I_Q}{2} \left(\alpha R_C - \frac{R_B}{1+\beta} \right) \end{aligned}$$

2-6/13/03

For the active mode $V_{CB} > 0$.

Small-Signal AC Solution

Set $v^+ = v^- = 0$ and $I_Q = 0$.

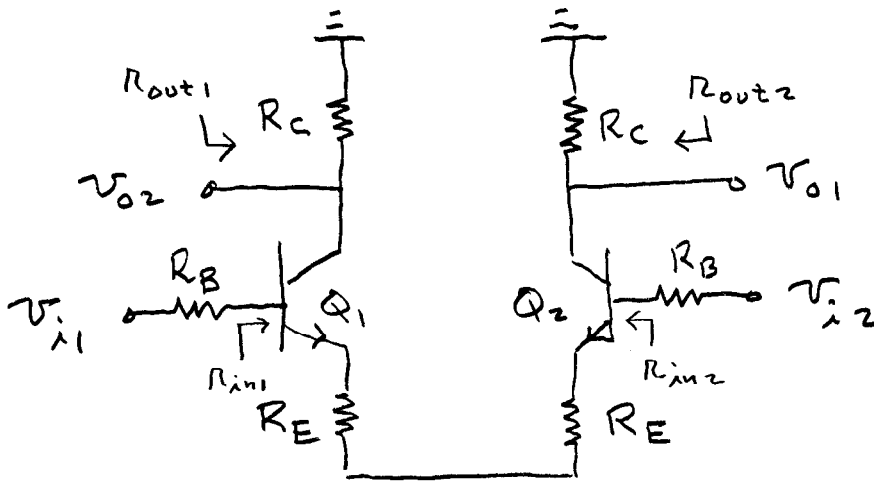

$$r_{e1} = r_{e2} = r_e = \frac{V_T}{I_E} = \frac{2V_T}{I_Q}$$

$$r'_{e1} = r'_{e2} = r'_e = \frac{R_B + r_x}{1 + \beta} + r_e$$


$$r_{ie1} = r_{ie2} = r_{ie} = r'_e \frac{r_o + R_c}{r'_e + r_o + \frac{R_c}{1 + \beta}}$$

$$R_{te1} = R_{te2} = R_{te} = 2R_E + r_{ie}$$

$$v_{e2(oc)} = v_{i2} \frac{r_o + \frac{R_c}{1 + \beta}}{r'_e + r_o + \frac{R_c}{1 + \beta}}$$

3 - 6 / 13 / 03

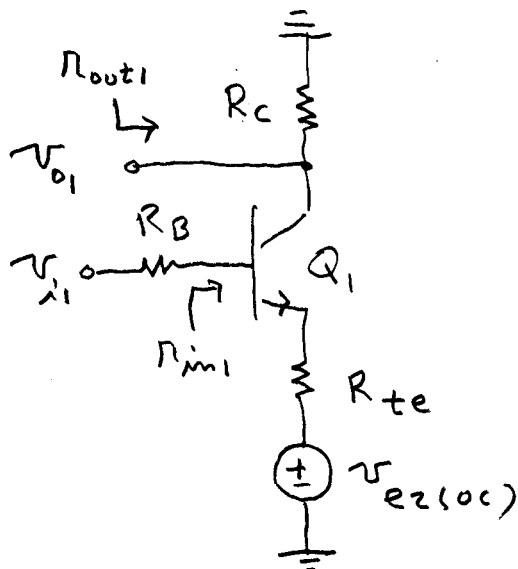
The circuit for v_{o1} , R_{out1} , and R_{in1} is



$$R_{in1} = R_{ib1}$$

$$= R_x + (1 + \beta)R_e + R_{te} \frac{(1 + \beta)R_o + R_c}{R_{te} + R_o + R_c}$$

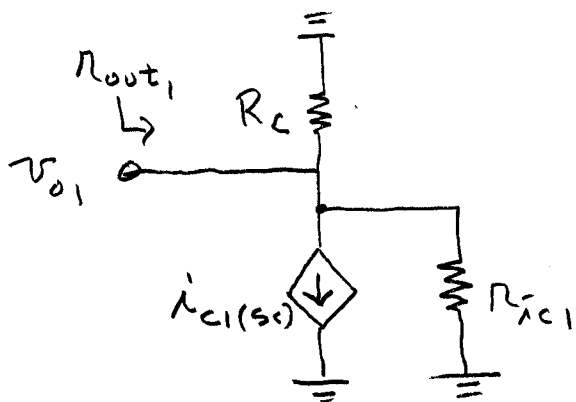Replace Q_1 with its Norton collector circuit



$$R_{ic1} = \frac{R_o + R_e' \parallel R_{te}}{1 - \frac{\alpha R_{te}}{R_e' + R_{te}}}$$

$$v_{o1} = -i_{c1}(sc) R_{ic1} \parallel R_{C1}$$

4 - 6/13/03

$$i_{c1}(s) = G_{mb1} v_{i1} - G_{me1} v_{e2}(oc)$$

$$G_{mb1} = G_{mb2} = G_{mb} = \frac{\alpha}{r_e' + R_{te} \parallel R_o} \frac{R_o - \frac{R_{te}}{\beta}}{R_o + R_{te}}$$

$$G_{me1} = G_{me2} = G_{me} = \frac{1}{R_{te} + R_e' \parallel R_o} \frac{\alpha R_o + R_e'}{R_o + R_e'}$$

$$\Rightarrow v_{o1} = [G_{mb1} v_{i1} - G_{me1} v_{e2}(oc)] \times (-R_{ic} \parallel R_c)$$

$$= \left[G_{mb1} v_{i1} - G_{me1} v_{i2} \frac{R_o + \frac{R_c}{1+\beta}}{R_e' + R_o + \frac{R_c}{1+\beta}} \right]$$

$$\times (-R_{ic} \parallel R_c)$$

$$R_{out1} = R_{ic1} \parallel R_c$$

For v_{o2} , R_{out2} , and R_{in2} , interchange the subscripts 1 and 2 in the above solutions.