
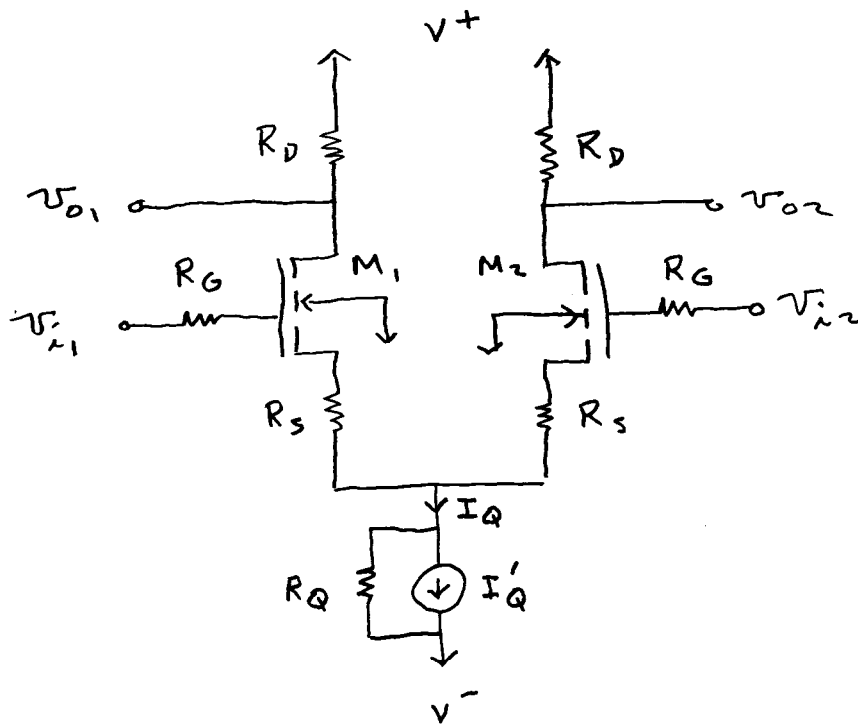


1-6/20/03

The MOSFET Diff Amp with Body Effect

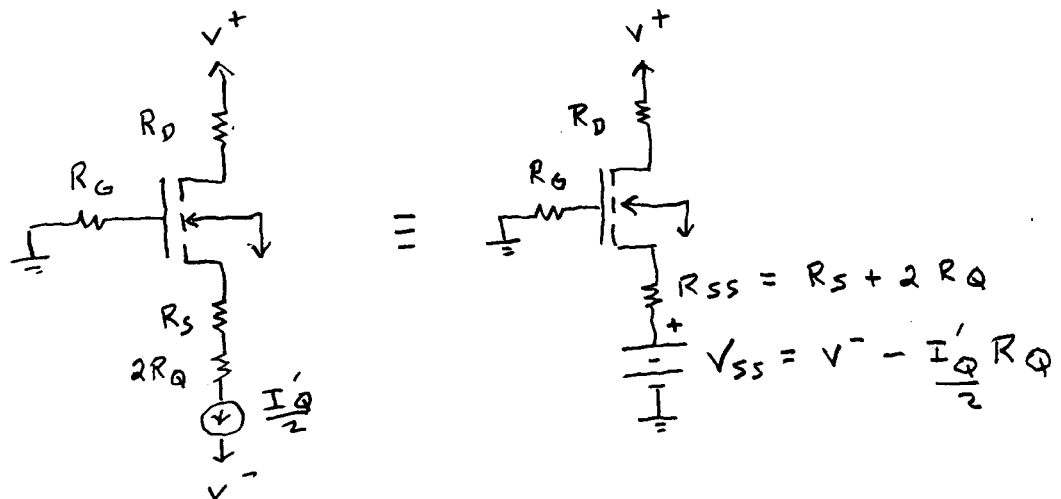

For the dc analysis, set $v_{i1} = v_{i2} = 0$ and split the source tail supply into two parallel sources - $I_Q/2$ in parallel with $2R_Q$. For identical devices, the equivalent circuit for either M_1 or M_2 is




2-6/20/03

From the MOSFET bias equation, we have

$$I_{D1} = I_{D2} = \frac{1}{4KR_{SS}} \left[\sqrt{1 + 4KV_1 R_{SS}} - 1 \right]^2$$


where $V_1 = V_{G6} - V_{SS} - V_{T0}$ and $V_{G6} = 0$

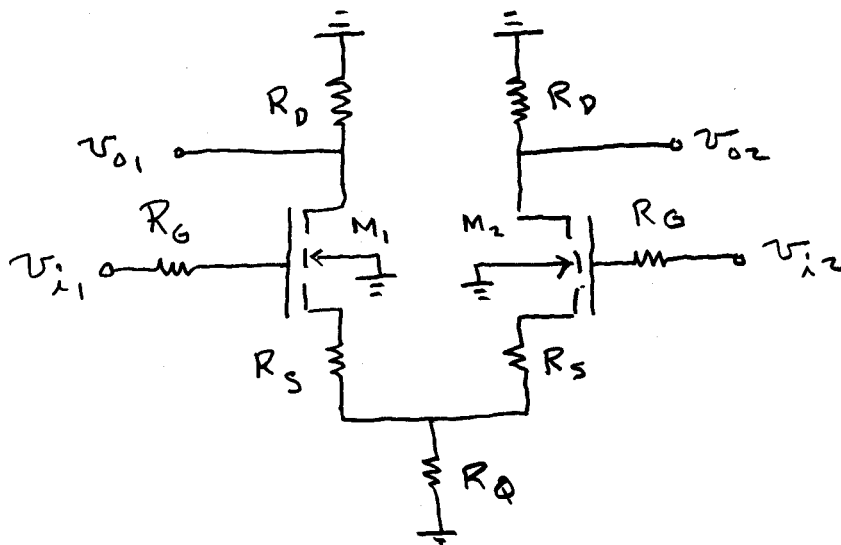The ac signal circuit is obtained by setting $v^+ = v^- = 0$ and $I'_Q = 0$.



To solve for v_{o1} , replace M_2 with its Thévenin source circuit. The circuit becomes

3 - 6/20/03

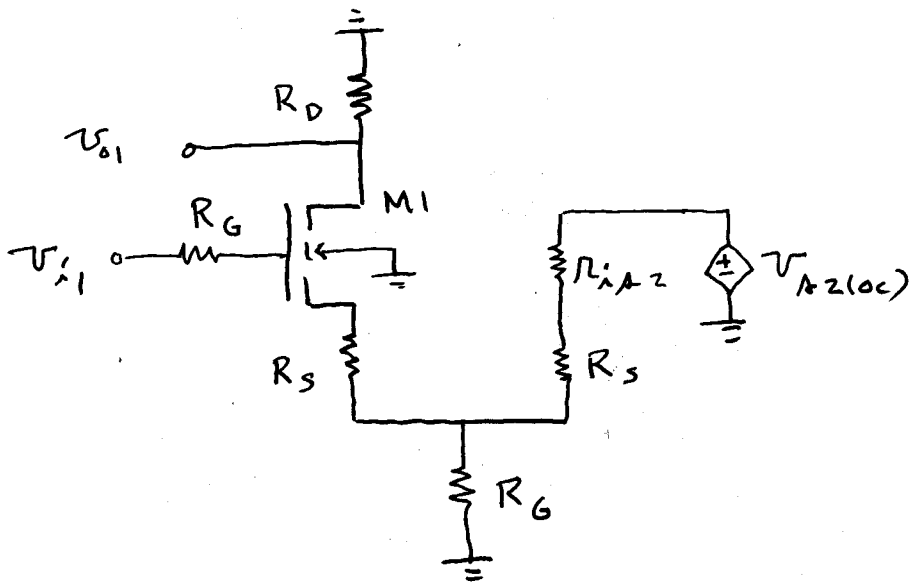

where


$$v_{A2(oc)} = \frac{v_{i2}}{1 + \chi_2} \frac{R_{o2}}{R'_{A2} + R_{o2}}$$

$$R'_{iA2} = R_{A2} \frac{R_{o2} + R_D}{R'_{A2} + R_{o2}}$$


$$R'_{A2} = R'_{A1} = \frac{R_A}{1 + \chi} = \frac{1}{g_m(1 + \chi)}$$

Next, replace the circuit looking out of the source of M_1 with a Thévenin equivalent circuit. The circuit becomes

4-6/20/03

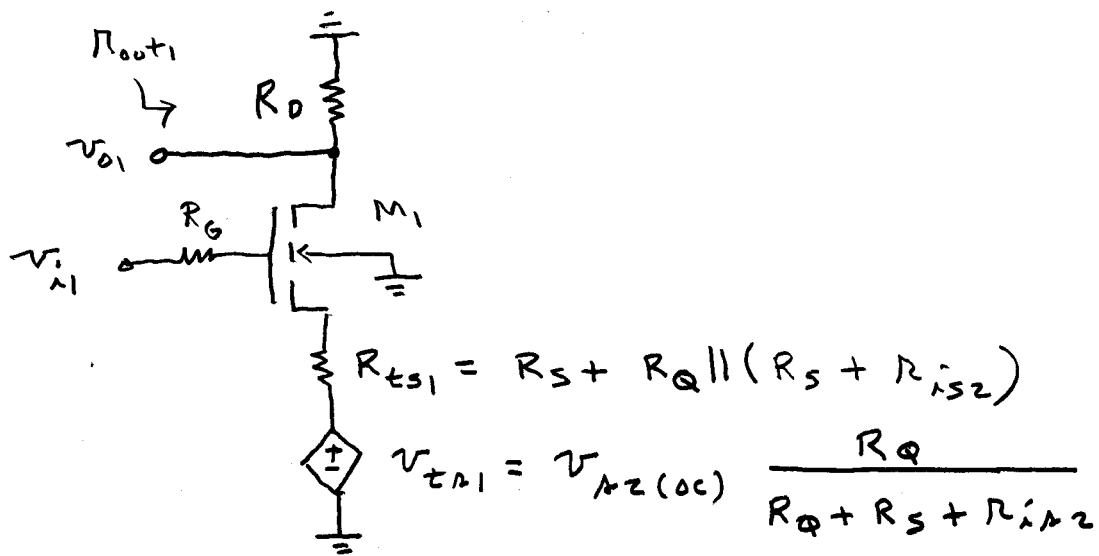

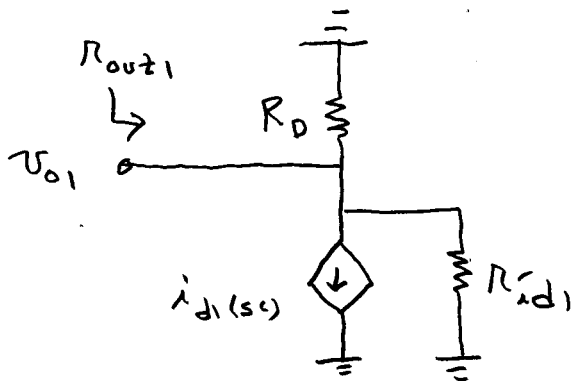To solve for v_{o1} and R_{out1} , replace M_1 with its Norton drain circuit. The circuit becomes



$$R_{out1} = R_{id1} \parallel R_D$$

$$v_{o1} = -i_{d1(sc)} R_{id1} \parallel R_D$$

where

5-6/20/03

$$R_{id1} = R_{o1} \left(1 + \frac{R_{ts1}}{R_{A1}'} \right) + R_{ts1}$$

$$i_{d1}(s) = G_{m1} v_{i1} - G_{m1} v_{ts1}$$

$$G_{m1} = \frac{1}{1+\chi_1} \frac{1}{R_{A1}' + R_{ts1} \parallel R_{o1}} \frac{R_{o1}}{R_{o1} + R_{ts1}}$$

$$G_{ms1} = \frac{1}{R_{ts1} + R_{A1}' \parallel R_o}$$

Combining terms, we obtain for v_{o1}

$$v_{o1} = - \left[G_{m1} v_{i1} - G_{m1} \frac{v_{i2}}{1+\chi_2} \frac{R_{o2}}{R_{A2}' + R_{o2}} \frac{R_o}{R_o + R_s + R_{iA2}} \right] \\ \times R_{id1} \parallel R_o$$

To obtain R_{out2} and v_{o2} , interchange the 1's and the 2's in all subscripts.

$$\text{But } G_{m2} \frac{1}{1+\chi_2} \frac{R_{o2}}{R_{A2}' + R_{o2}} = G_{m2}$$

Thus the solution for v_{o1} can be simplified to

6-6/20/03

$$v_{o1} = - \left[Gm_{g1} v_{i1} - Gm_{g2} v_{i2} \frac{R_Q}{R_Q + R_S + R_{iA2}} \right] \\ \times R_{id1} \parallel R_D$$

Thus for identical devices biased at the same voltages and currents, we can write

$$v_{o1} = - Gm_g \left[v_{i1} - v_{i2} \frac{R_Q}{R_Q + R_S + R_{iA2}} \right] R_{id} \parallel R_D$$

If R_Q is sufficiently large, it can be replaced with ∞ (open circuit) in the formulas. In this case

$$v_{o1} = -v_{o2} = - Gm_g [v_{i1} - v_{i2}] R_{id} \parallel R_D$$

In this case, the common-mode gain is zero and $CMRR = \infty$.

The above solution should be intuitively obvious because the

7-6/20/03

small signal ac drain current in M_2 must be the negative of the small signal ac drain current in M_1 .