

**EE4435 Homework**  
**Physical Characteristics of Op-Amps**

1. An op-amp has the low-frequency open-loop gain  $A_0 = 10^5$ . The op-amp is to be used in an inverting amplifier with a gain of  $-2000$ . (a) What is the required ratio  $R_F/R_1$ ? [2040.8]  
(b) For the value of  $R_F/R_1$ , how much larger is the input resistance than  $R_1$ ? [ $1.0204R_1$ ]
2. An op-amp has the low-frequency open-loop gain  $A_0 = 10^5$ . The op-amp is to be used in a non-inverting amplifier. The theoretical gain is calculated assuming that the op-amp is ideal. What is the highest theoretical gain that gives an error between the theoretical gain and the actual gain that is less than 5%? [5263.2]
3. At low frequencies, an op-amp has an open-loop gain  $A_0 = 10^5$  and an open-loop output resistance  $R_0 = 150 \Omega$ . The op-amp is to be used in a non-inverting amplifier having a voltage gain of 200. If the amplifier is designed with the assumption that the op-amp is ideal and the input resistance to the feedback network is to be  $100 \text{ k}\Omega$ , calculate the actual gain of the circuit and its output resistance. [199.60,  $0.29940 \Omega$ ]
4. At low frequencies, an op-amp has an open-loop gain  $A_0 = 10^5$  and an open-loop output resistance  $R_0 = 150 \Omega$ . The op-amp is to be used in an inverting amplifier having a voltage gain of  $-200$ . If the amplifier is designed with the assumption that the op-amp is ideal with an amplifier input resistance of  $1 \text{ k}\Omega$ , calculate the actual gain of the circuit and its output resistance. [ $-199.6$ ,  $0.301 \Omega$ ]
5. An op-amp has the gain-bandwidth product  $f_x = 1.5 \text{ MHz}$ . The op-amp is to be used in a non-inverting amplifier circuit. Calculate the highest gain that the amplifier can have if the half-power or  $-3 \text{ dB}$  bandwidth is to be  $30 \text{ kHz}$  or greater. [ $-50$ ]
6. Two non-inverting op-amp amplifiers are operated in cascade. Each amplifier has a gain of 20. If each op-amp has the gain-bandwidth product  $f_x = 1.5 \text{ MHz}$ , calculate the half-power or  $-3 \text{ dB}$  bandwidth of the cascade amplifier. [48.3 kHz]
7. An op-amp has the gain-bandwidth product  $f_x = 1.5 \text{ MHz}$ . Compare the bandwidths of an inverting and a non-inverting amplifier which use the op-amp if the dB values of the voltage gain magnitude  $A_{of}$  are 0 dB, 10 dB, 20 dB, and 30 dB. [Non-inverting: 1.5 MHz, 4.74 kHz, 150 kHz, 47.4 kHz, Inverting: 750 kHz, 360 kHz, 136 kHz, 46 kHz]
8. An op-amp has a dc gain  $A_0 = 10^5$  and a gain bandwidth product  $f_x = 1.5 \text{ MHz}$ . The op-amp is used in an inverting amplifier with the element values  $R_1 = 1.5 \text{ k}\Omega$  and  $R_F = 75 \text{ k}\Omega$ . Calculate the dc gain of the amplifier, the upper cutoff frequency, and the value of the elements in the equivalent circuit for the input impedance. [ $-49.98$ , 29.4 kHz,  $R_2 = 0.75 \Omega$ ,  $L = 7.96 \text{ mH}$ ]
9. The op-amp in the preceding problem has an open-loop output resistance  $R_0 = 150 \Omega$ . Calculate the value of the elements in the equivalent circuit for the output impedance. [ $R_2 = 150 \Omega$ ,  $L = 811 \mu\text{H}$ ]
10. An op-amp has the saturation voltages  $V_{SAT}^+ = V^+ - 3 \text{ V}$  and  $V_{SAT}^- = V^- + 3 \text{ V}$ , where  $V^+ = 15 \text{ V}$  and  $V^- = -15 \text{ V}$ . The current limited output current is  $I_M = 30 \text{ mA}$ . (a) Determine the lowest load resistance that can be driven to full output without current limiting. (b) Determine the peak output voltage for a load resistance of  $75 \Omega$ . (c) The op-amp is used

to realize a non-inverting amplifier with a gain of 5. The input waveform is a square wave with a peak value of 1 V. Sketch the plot of the output voltage waveform for a capacitive load of value  $C_L = 1 \mu\text{F}$ . Assume that the op-amp does not slew. [400  $\Omega$ , 2.25 V, slopes are  $\pm 3 \times 10^4 \text{ V/s}$ ]

11. The op-amp in the preceding problem has a slew rate of  $0.75 \text{ V}/\mu\text{s}$ . (a) Calculate the full-power bandwidth of the op-amp. (b) Calculate the peak value of the largest amplitude sine-wave that the op-amp can put out at frequency of 30 kHz if it is not to slew. (c) Calculate the largest peak-to-peak signal that the op-amp can put out at 30 kHz. Hint, assume that the amplitude of the input signal is increased until the output voltage waveform is fully converted into a triangle wave. [9.95 kHz, 6.25 V]
12. A non-inverting amplifier with feedback resistors  $R_F$  and  $R_1$  has a resistor  $R_2$  in series with its non-inverting input. The op-amp has the input bias current  $I_B$ . Solve for the dc component of the output voltage due to  $I_B$ . Assume that  $A_0 \rightarrow \infty$ ,  $I_{OS} = 0$ , and  $V_{OS} = 0$ .  $[(1 + R_F/R_1) I_B (R_2 - R_1 || R_F)]$
13. A non-inverting op-amp with feedback resistors  $R_F = 100 \text{ k}\Omega$  and  $R_1 = 1 \text{ k}\Omega$  has a dc offset voltage of 1 V at its output when  $v_I = 0$ . (a) If the input offset current and input bias current can be neglected, calculate the input offset voltage  $V_{OS}$ . (b) If the input offset voltage and input bias current can be neglected, calculate the input offset current  $I_{OS}$ . (c) If the input offset voltage and input offset current can be neglected, calculate the input bias current  $I_B$ . [9.9 mV, 20  $\mu\text{A}$ , 10  $\mu\text{A}$ ]
14. A non-inverting amplifier has a resistor  $R_1$  in series with the + input and feedback resistors  $R_2$  and  $R_F$ . A series resistor  $R_3$  and capacitor  $C$  are connected between the + and - inputs. Show that the effective open-loop transfer function is given by

$$A'(s) = A(s) \frac{1 + R_3Cs}{1 + (R_1 + R_2 || R_F + R_3)Cs}$$

Thus the  $R_3 - C$  network adds a pole-zero pair to the transfer function. Using a Bode plot, show how this can improve the stability of an amplifier when  $A(s)$  has more than one pole below the unity-gain frequency.