

ECE4435 Homework
Physical Characteristics of Op-Amps

1. An op-amp has the low-frequency open-loop gain $A_0 = 10^5$. The op-amp is to be used in an inverting amplifier with a gain of -2000 . (a) What is the required ratio R_F/R_1 ? [2040.8]
(b) For the value of R_F/R_1 , how much larger is the input resistance than R_1 ? [$1.0204R_1$]
2. An op-amp has the low-frequency open-loop gain $A_0 = 10^5$. The op-amp is to be used in a non-inverting amplifier. The theoretical gain is calculated assuming that the op-amp is ideal. What is the highest theoretical gain that gives an error between the theoretical gain and the actual gain that is less than 5%? [5263.2]
3. At low frequencies, an op-amp has an open-loop gain $A_0 = 10^5$ and an open-loop output resistance $R_0 = 150 \Omega$. The op-amp is to be used in a non-inverting amplifier having a voltage gain of 200. If the amplifier is designed with the assumption that the op-amp is ideal and the input resistance to the feedback network is to be $100 \text{ k}\Omega$, calculate the actual gain of the circuit and its output resistance. [199.60, 0.29940Ω]
4. At low frequencies, an op-amp has an open-loop gain $A_0 = 10^5$ and an open-loop output resistance $R_0 = 150 \Omega$. The op-amp is to be used in an inverting amplifier having a voltage gain of -200 . If the amplifier is designed with the assumption that the op-amp is ideal with an amplifier input resistance of $1 \text{ k}\Omega$, calculate the actual gain of the circuit and its output resistance. [-199.6 , 0.301Ω]
5. An op-amp has the gain-bandwidth product $f_x = 1.5 \text{ MHz}$. The op-amp is to be used in a non-inverting amplifier circuit. Calculate the highest gain that the amplifier can have if the half-power or -3 dB bandwidth is to be 30 kHz or greater. [-50]
6. Two non-inverting op-amp amplifiers are operated in cascade. Each amplifier has a gain of 20. If each op-amp has the gain-bandwidth product $f_x = 1.5 \text{ MHz}$, calculate the half-power or -3 dB bandwidth of the cascade amplifier. [48.3 kHz]
7. An op-amp has the gain-bandwidth product $f_x = 1.5 \text{ MHz}$. Compare the bandwidths of an inverting and a non-inverting amplifier which use the op-amp if the dB values of the voltage gain magnitude A_{of} are 0 dB, 10 dB, 20 dB, and 30 dB. [Non-inverting: 1.5 MHz, 4.74 kHz, 150 kHz, 47.4 kHz, Inverting: 750 kHz, 360 kHz, 136 kHz, 46 kHz]
8. An op-amp has a dc gain $A_0 = 10^5$ and a gain bandwidth product $f_x = 1.5 \text{ MHz}$. The op-amp is used in an inverting amplifier with the element values $R_1 = 1.5 \text{ k}\Omega$ and $R_F = 75 \text{ k}\Omega$. Calculate the dc gain of the amplifier, the upper cutoff frequency, and the value of the elements in the equivalent circuit for the input impedance. [-49.98 , 29.4 kHz, $R_2 = 0.75 \Omega$, $L = 7.96 \text{ mH}$]
9. The op-amp in the preceding problem has an open-loop output resistance $R_0 = 150 \Omega$. Calculate the value of the elements in the equivalent circuit for the output impedance. [$R_2 = 150 \Omega$, $L = 811 \mu\text{H}$]
10. An op-amp has the saturation voltages $V_{SAT}^+ = V^+ - 3 \text{ V}$ and $V_{SAT}^- = V^- + 3 \text{ V}$, where $V^+ = 15 \text{ V}$ and $V^- = -15 \text{ V}$. The current limited output current is $I_M = 30 \text{ mA}$. (a) Determine the lowest load resistance that can be driven to full output without current limiting. (b) Determine the peak output voltage for a load resistance of 75Ω . (c) The op-amp is used

to realize a non-inverting amplifier with a gain of 5. The input waveform is a square wave with a peak value of 1 V. Sketch the plot of the output voltage waveform for a capacitive load of value $C_L = 1 \mu\text{F}$. Assume that the op-amp does not slew. [400 Ω , 2.25 V, slopes are $\pm 3 \times 10^4 \text{ V/s}$]

11. The op-amp in the preceding problem has a slew rate of $0.75 \text{ V}/\mu\text{s}$. (a) Calculate the full-power bandwidth of the op-amp. (b) Calculate the peak value of the largest amplitude sine-wave that the op-amp can put out at frequency of 30 kHz if it is not to slew. (c) Calculate the largest peak-to-peak signal that the op-amp can put out at 30 kHz. Hint, assume that the amplitude of the input signal is increased until the output voltage waveform is fully converted into a triangle wave. [9.95 kHz, 6.25 V]
12. A non-inverting amplifier with feedback resistors R_F and R_1 has a resistor R_2 in series with its non-inverting input. The op-amp has the input bias current I_B . Solve for the dc component of the output voltage due to I_B . Assume that $A_0 \rightarrow \infty$, $I_{OS} = 0$, and $V_{OS} = 0$. $[(1 + R_F/R_1) I_B (R_2 - R_1 || R_F)]$
13. A non-inverting op-amp with feedback resistors $R_F = 100 \text{ k}\Omega$ and $R_1 = 1 \text{ k}\Omega$ has a dc offset voltage of 1 V at its output when $v_I = 0$. (a) If the input offset current and input bias current can be neglected, calculate the input offset voltage V_{OS} . (b) If the input offset voltage and input bias current can be neglected, calculate the input offset current I_{OS} . (c) If the input offset voltage and input offset current can be neglected, calculate the input bias current I_B . (d) The op-amp has the low-frequency open-loop gain $A_0 = 10^5$. When either power supply voltage is changed by 1 V, the dc offset at the op amp output changes by 0.5 V. Calculate the power supply rejection ratio in $\mu\text{V/V}$. [9.9 mV, 20 μA , 10 μA , 5 $\mu\text{V/V}$]
14. A non-inverting amplifier has a resistor R_1 in series with the + input and feedback resistors R_2 and R_F . A series resistor R_3 and capacitor C are connected between the + and - inputs. Show that the effective open-loop transfer function is given by

$$A'(s) = A(s) \frac{1 + R_3 C s}{1 + (R_1 + R_2 || R_F + R_3) C s}$$

Thus the $R_3 - C$ network adds a pole-zero pair to the transfer function. Using a Bode plot, show how this can improve the stability of an amplifier when $A(s)$ has more than one pole below the unity-gain frequency.

15. An op-amp has the low-frequency open-loop differential gain $A_0 = 10^5$. The op amp is used as a non-inverting amplifier with the feedback ratio $v_F/v_O = 0.0001$. The gain with feedback is found to be $v_O/v_I = 9100$. Calculate the common-mode rejection ratio ρ . (955 or 59.6 dB)