

# **Design Project**

ECE4445 – Audio Engineering

November 27<sup>th</sup>, 2006

**Franklin Falcon**

901-95-6137

[ffalcon@gatech.edu](mailto:ffalcon@gatech.edu)

**Juan O'Connell**

570-575-8161

[gtg131v@mail.gatech.edu](mailto:gtg131v@mail.gatech.edu)

In this design project, various simulations were performed. The simulations are:

1. Loudspeaker mounted on infinite baffle.
2. Loudspeaker mounted inside a closed box.
3. Loudspeaker with matching network mounted inside a closed box.
4. Loudspeaker with matching network and 2<sup>nd</sup> order crossover network mounted inside a closed box.
5. Loudspeaker with matching network and 3<sup>rd</sup> order crossover network mounted inside a closed box.
6. Loudspeaker mounted inside a vented box.

All the simulations were performed using PSPICE. The SPICE circuits and netlists are attached at the end of the report.

Zoff := READPRN("off.txt")

Zon := READPRN("on.txt")

Zoff =

	0	1	2
0	9.994	8.258	40.046
1	10.244	8.39	40.636
2	10.517	8.555	40.839
3	10.792	8.704	41.537
4	11.067	8.876	41.815
5	11.34	9.034	42.706
6	11.64	9.225	43.056
7	11.939	9.436	42.956
8	12.239	9.61	44.423
9	12.538	9.815	45.014
10	12.873	10.048	45.625
11	13.222	10.31	45.932
12	13.546	10.558	46.356
13	13.895	10.827	46.886
14	14.245	11.117	47.236
15	14.619	11.432	47.697

Zon =

	0	1	2
0	9.994	6.021	10.063
1	10.244	6.03	10.058
2	10.518	6.039	10.25
3	10.792	6.049	10.568
4	11.067	6.058	10.728
5	11.341	6.066	11.26
6	11.641	6.077	11.345
7	11.94	6.088	11.499
8	12.239	6.097	11.906
9	12.538	6.108	12.123
10	12.873	6.12	12.43
11	13.222	6.135	12.743
12	13.546	6.147	13.018
13	13.896	6.16	13.357
14	14.245	6.174	13.608
15	14.619	6.191	13.935

$R_E := 5.33$  DC resistance

$V_T := 1.56$  Test box volume

$N := 300$  Number of data points minus 1       $Z_p(x,y) := \frac{x \cdot y}{x + y}$  Parallel combinaton

From the Zoff array:

$$f_s := 30.482 \quad R_{ES} := 43.614 - R_E \quad R_{ES} = 38.284 \quad R_1 := \sqrt{R_E \cdot (R_E + R_{ES})}$$

$$R_1 = 15.247 \quad f_1 := 18.36 \quad f_2 := 50.582 \quad \sqrt{f_1 \cdot f_2} = 30.474$$

$$Q_{MS} := \frac{f_s}{f_2 - f_1} \cdot \sqrt{\frac{R_E + R_{ES}}{R_E}} \quad Q_{MS} = 2.706 \quad Q_{ES} := \frac{R_E}{R_{ES}} \cdot Q_{MS} \quad Q_{ES} = 0.377$$

$$Q_{TS} := \frac{R_E}{R_E + R_{ES}} \cdot Q_{MS} \quad Q_{TS} = 0.331$$

$$n_e := \frac{2}{\pi} \cdot \arg\left(\text{Zoff}_{250,1} \cdot \cos\left(\text{Zoff}_{250,2} \cdot \frac{\pi}{180}\right) - R_E + j \cdot \text{Zoff}_{250,1} \cdot \sin\left(\text{Zoff}_{250,2} \cdot \frac{\pi}{180}\right)\right) \quad n_e = 0.65$$

$$L_e := \frac{\sqrt{\left(\text{Zoff}_{250,1} \cdot \cos\left(\text{Zoff}_{250,2} \cdot \frac{\pi}{180}\right) - R_E\right)^2 + \left(\text{Zoff}_{250,1} \cdot \sin\left(\text{Zoff}_{250,2} \cdot \frac{\pi}{180}\right)\right)^2}}{\left(2 \cdot \pi \cdot \text{Zoff}_{250,0}\right)^{n_e}} \quad L_e = 0.03$$

$$n := 0..N \quad f_n := 10 \cdot \left(\frac{20000}{10}\right)^{\frac{n}{N}} \quad \text{Frequency range variable for calculating Zvc(f)}$$

$L_E := 13 \cdot 10^{-3}$  "Tweaked" value of parallel lossless inductor in Allen Robinson's model

$$\text{Zvc(f)} := R_E + Z_p \left[ j \cdot 2 \cdot \pi \cdot f \cdot L_E \cdot L_e \cdot (j \cdot 2 \cdot \pi \cdot f)^{n_e} \right] + R_{ES} \cdot \frac{\frac{1}{Q_{MS}} \cdot \left(\frac{j \cdot f}{f_S}\right)}{1 - \left(\frac{f}{f_S}\right)^2 + \frac{1}{Q_{MS}} \cdot \left(\frac{j \cdot f}{f_S}\right)}$$

From the Zon array:



$$f_{CT} := 75.889 \quad R_{ECT} := 34.353 - R_E \quad R_{ECT} = 29.023 \quad R_1 := \sqrt{R_E \cdot (R_E + R_{ECT})}$$

$$R_1 = 13.531 \quad f_{1T} := 55.988 \quad f_{2T} := 95.33 \quad \sqrt{f_{1T} \cdot f_{2T}} = 73.057$$

$$Q_{MCT} := \frac{f_{CT}}{f_{2T} - f_{1T}} \cdot \sqrt{\frac{R_E + R_{ECT}}{R_E}} \quad Q_{MCT} = 4.897$$

$$Q_{ECT} := \frac{R_E}{R_{ECT}} \cdot Q_{MCT} \quad Q_{ECT} = 0.899 \quad Q_{TCT} := \frac{R_E}{R_E + R_{ECT}} \cdot Q_{MCT} \quad Q_{TCT} = 0.76$$
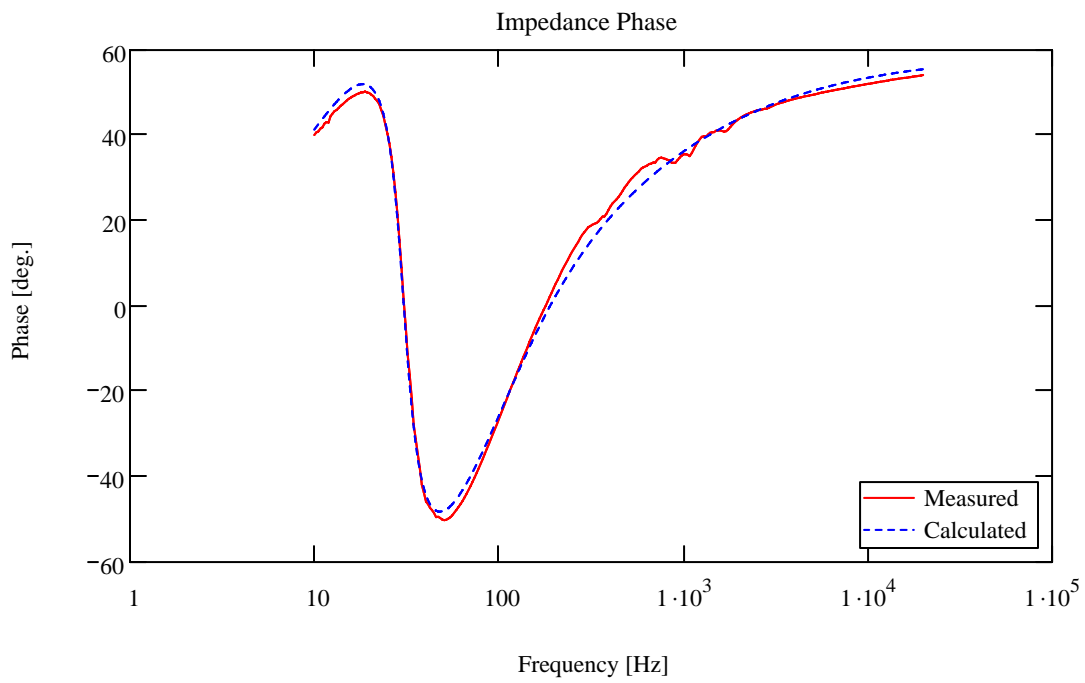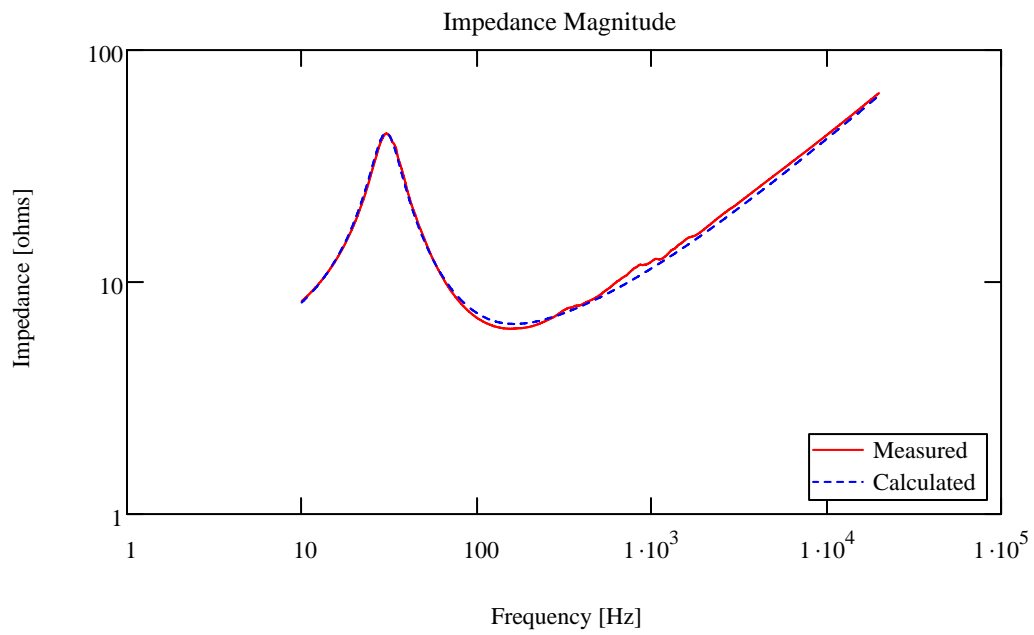
$$V_{AS} := V_T \cdot \left( \frac{f_{CT}}{f_S} \cdot \frac{Q_{ECT}}{Q_{ES}} - 1 \right) \quad V_{AS} = 7.711$$



### Infinite Baffle:

In this section, parameters are calculated to construct the electrical circuits which simulate the speaker mounted on an infinite baffle. From these electrical circuits, it is possible to obtain the input impedance, the sound pressure level produced by the loudspeaker, and the diaphragm peak displacement. The equations used for the calculations are shown below. Also, the graphics show the parameters measured from the SPICE simulation.

$$Q_{MS} = 2.706 \quad Q_{ES} = 0.377 \quad Q_{TS} = 0.331$$

$$\rho_o := 1.18 \quad c := 345 \quad a := 0.12 \quad V_{AS} := 0.218 \quad \text{---> in m}^3$$

$$f_S = 30.482 \quad V_{AS} = 0.218 \quad S_D := \pi a^2 \quad S_D = 0.045$$

$$C_{MS} := \frac{V_{AS}}{\rho_o \cdot c^2 \cdot S_D^2} \quad C_{MS} = 7.584 \times 10^{-4}$$

$$M_{MS} := \frac{1}{(2\pi \cdot f_S)^2 \cdot C_{MS}} \quad M_{MS} = 0.036$$

$$R_{MS} := \frac{1}{Q_{MS}} \cdot \sqrt{\frac{M_{MS}}{C_{MS}}} \quad R_{MS} = 2.544$$

$$Bl := \sqrt{\frac{R_E}{Q_{ES}}} \cdot \sqrt{\frac{M_{MS}}{C_{MS}}} \quad Bl = 9.869$$

$$M_{MD} := M_{MS} - 2 \cdot \frac{8 \cdot \rho_o}{3\pi^2 \cdot (a)} \cdot S_D^2 \quad M_{MD} = 0.025$$


$$M_{A1} := \frac{8 \cdot \rho_o}{3 \cdot \pi^2 \cdot (a)} \quad M_{A1} = 2.657$$

$$R_{A2} := \frac{\rho_o \cdot c}{\pi \cdot a^2} \quad R_{A2} = 8.999 \times 10^3$$


$$R_{A1} := \frac{128 \cdot \rho_o \cdot c}{9 \cdot \pi^3 \cdot a^2} - R_{A2} \quad R_{A1} = 3.969 \times 10^3$$

$$C_{A1} := \frac{5.94 \cdot a^3}{\rho_o \cdot c^2} \quad C_{A1} = 7.308 \times 10^{-8}$$

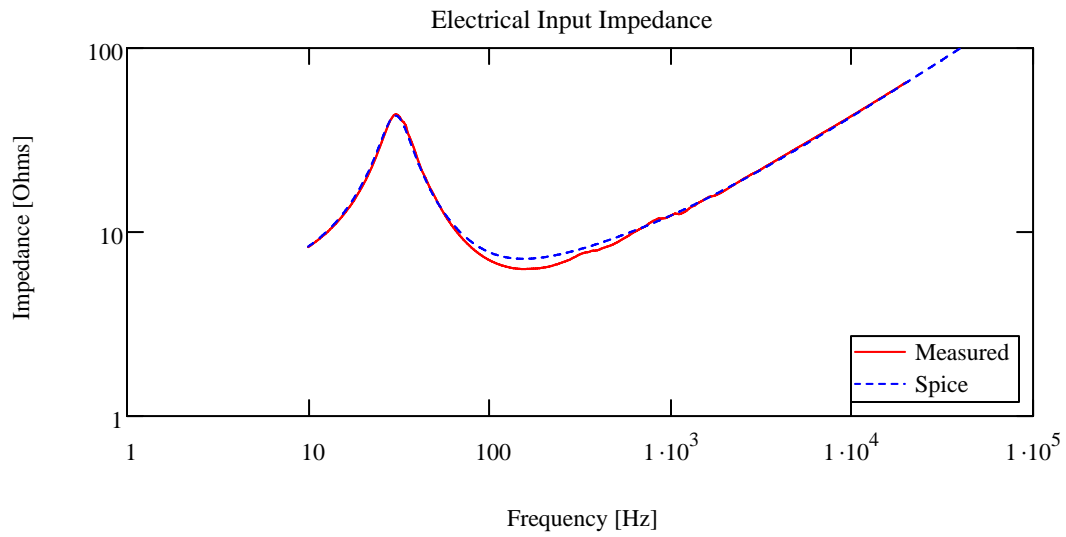
```
SpcIBZin := READPRN("SpiceIBZin.txt")
```


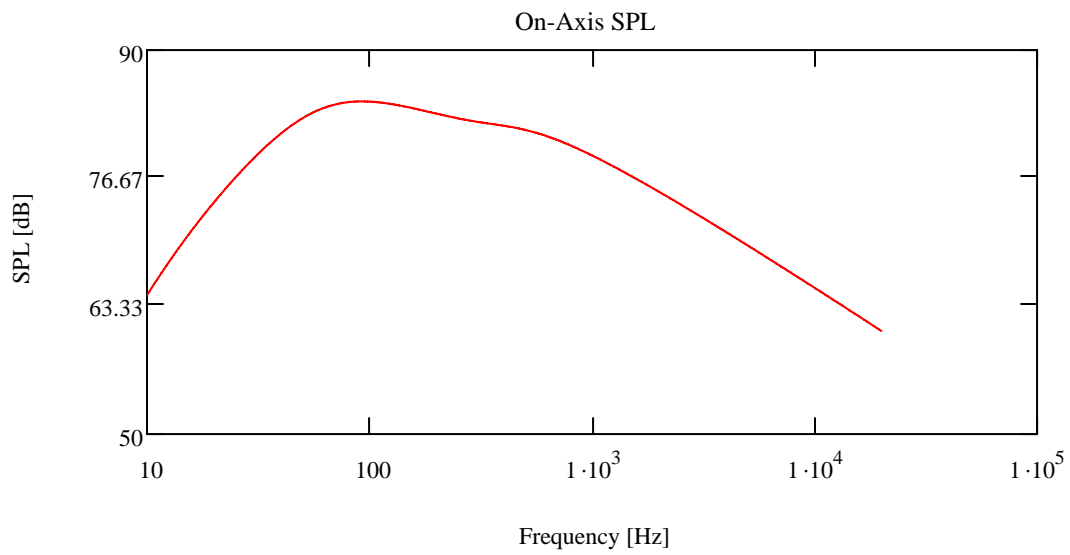
```
SpcIBSPL := READPRN("SpiceIBSPL.txt")
```


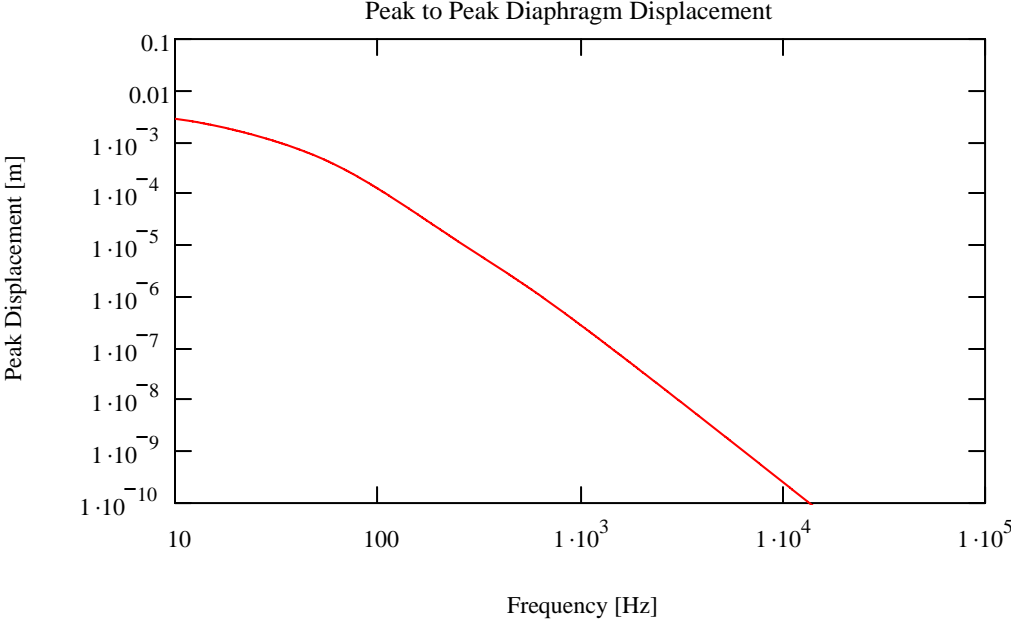
```
SpcIBXpp := READPRN("SpiceIBXpp.txt")
```





### Closed Box:

In this section, parameters are calculated to build the circuits that model the loudspeaker mounted inside a closed box. The first three graphs show the results of the SPICE measurements. A matching network was designed with the purpose of making the input impedance behave like if it was only the voice coil resistor  $R_E$ , the graph shown under "Matching Network Design" shows the electrical input impedance before and after adding the matching network. Also, 2nd and 3rd order crossover networks were designed with the purpose of only allowing low frequencies to reach the woofer. The measured sound pressure levels without crossover network, with a 2nd order network, and with a 3rd order network, are shown in the graph under "Crossover Network Design".

$$\alpha := \left( \frac{Q_{ECT}}{Q_{ES}} \right)^2 - 1 \quad \alpha = 4.698$$

$$V_{AB} := \frac{V_{AS}}{\alpha} \quad V_{AB} = 0.046$$

$$C_{AB} := \frac{V_{AB}}{\rho_o \cdot c^2} \quad C_{AB} = 3.304 \times 10^{-7}$$

$$R_{AB} := \left( \sqrt{1 + \alpha} \cdot \frac{Q_{MS}}{Q_{MCT}} \right) \cdot \frac{R_{MS}}{S_D^2} \quad R_{AB} = 1.64 \times 10^3$$

$$M_{MC} := \left( \frac{Bl^2 \cdot Q_{ECT}}{\pi \cdot a^2 \cdot c \cdot R_E} \right)^2 \cdot \frac{V_{AS}}{\rho_o \cdot (1 + \alpha)} \quad M_{MC} = 0.036$$

$$R_{MS} := \frac{1}{Q_{MS}} \cdot \sqrt{\frac{M_{MC}}{C_{MS}}} \quad R_{MS} = 2.544$$




$$M_{AB} := \frac{M_{MC} - M_{MD}}{\pi^2 \cdot a^4} - M_{A1} \quad M_{AB} = 2.657$$

$$R_{AL} := \frac{1}{2\pi \cdot (1) \cdot C_{AB}} \quad R_{AL} = 4.818 \times 10^6$$

SpCBZin := READPRN("SpiceCBZin.txt")

SpCBSPL := READPRN("SpiceCBSPL.txt")

SpCBXpp := READPRN("SpiceCBXpp.txt")

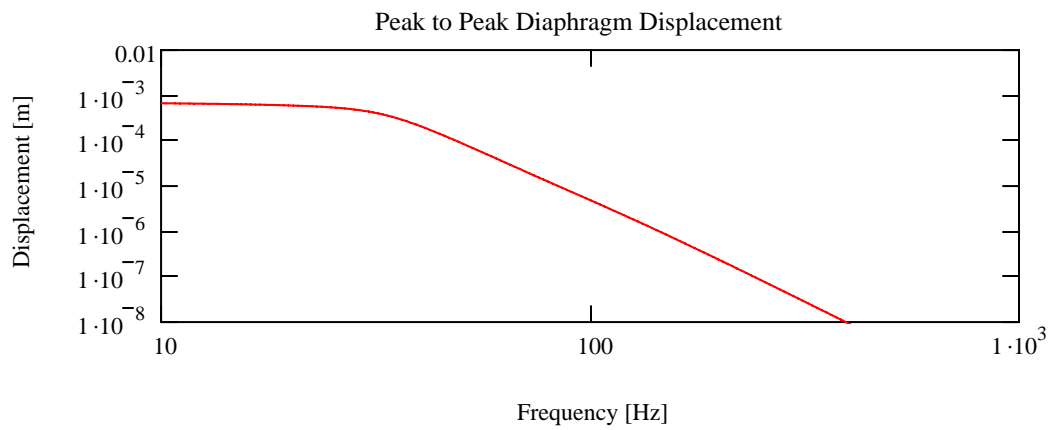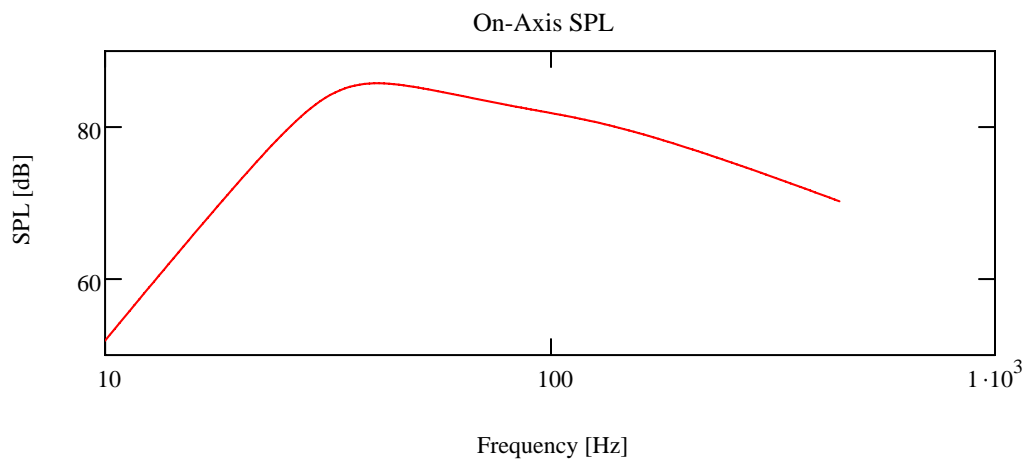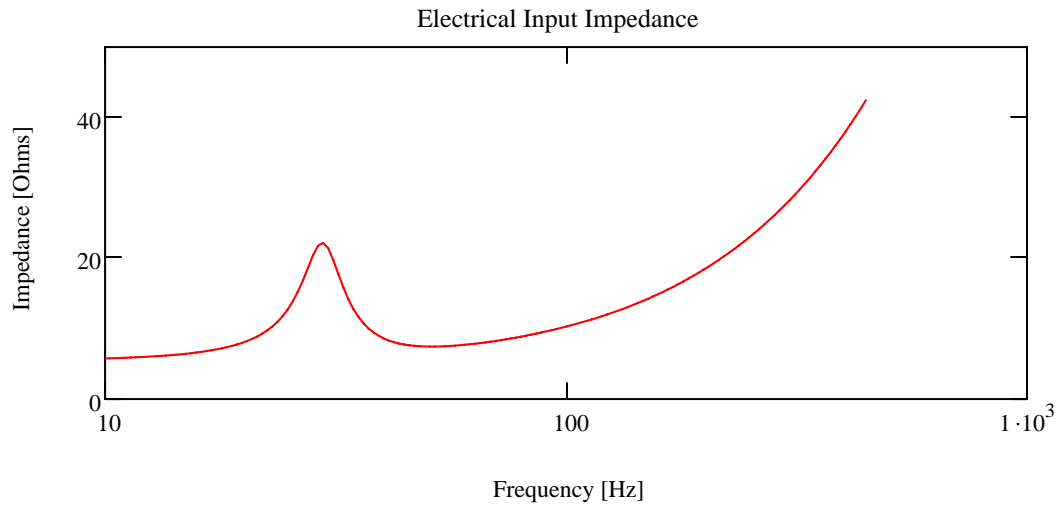

### Matching Network Design:

$$f_c := f_s \cdot \sqrt{1 + \alpha} \quad f_c = 72.764 \quad f_{1mn} := 2000 \quad f_{2mn} := 20 \cdot 10^3 \quad L_e = 0.03 \quad n_e = 0.65$$

$$R_E = 5.33 \quad Q_{MCT} = 4.897 \quad Q_{ECT} = 0.899 \quad Q_{EC} := Q_{ES} \cdot \sqrt{1 + \alpha}$$

$$R_{1,mn} := R_E \quad C_{1,mn} := \frac{L_e}{(2\pi)^{(1-n_e)} \cdot R_E^2 \cdot \left[ f_{1mn}^{n_e} \cdot f_{2mn}^{(2+n_e)} \right]^{\frac{1-n_e}{2(1+n_e)}}}$$


$$C_{2,mn} := \frac{L_e}{(2\pi)^{1-n_e} \cdot R_E^2 \cdot \left[ f_{1mn}^{(2+n_e)} \cdot f_{2mn}^{n_e} \right]^{\frac{1-n_e}{2(1+n_e)}}} - C_{1,mn} \quad R_{2,mn} := \frac{1}{2\pi f_{1mn} \cdot \left( \frac{1}{1+n_e} \right) \cdot f_{2mn} \cdot \left( \frac{n_e}{1+n_e} \right) \cdot C_{2,mn}}$$

$$R_{3,mn} := R_E \cdot \left( 1 + \frac{Q_{ECT}}{Q_{MCT}} \right) \quad L_{1,mn} := \frac{R_E \cdot Q_{ECT}}{2\pi f_c} \quad C_{3,mn} := \frac{1}{2\pi f_c \cdot R_E \cdot Q_{ECT}}$$

$$R_{1,mn} = 5.33 \quad C_{1,mn} = 2.054 \times 10^{-5} \quad C_{2,mn} = 1.293 \times 10^{-5} \quad R_{2,mn} = 2.484$$

$$R_{3,mn} = 6.309 \quad L_{1,mn} = 0.01 \quad C_{3,mn} = 4.563 \times 10^{-4}$$

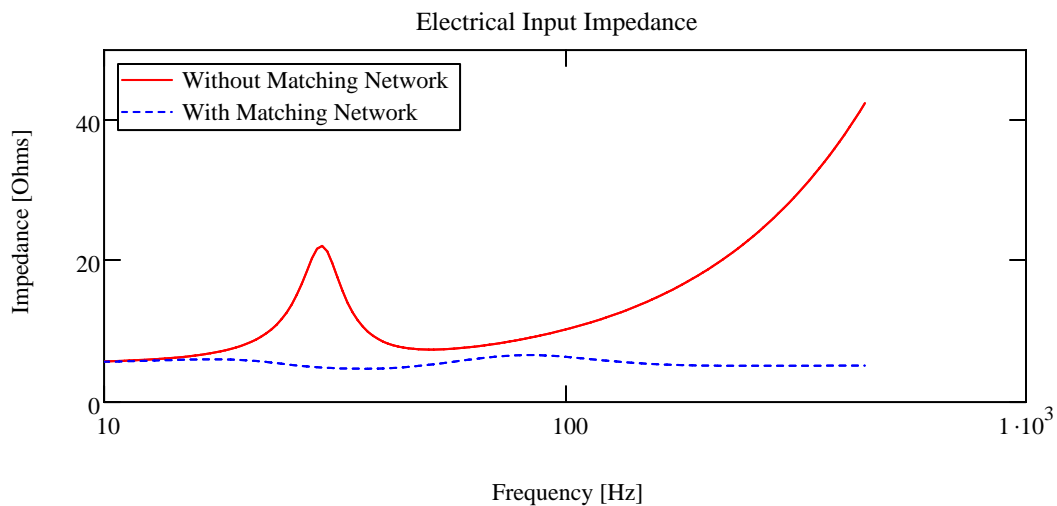SpCBwMNZin := READPRN("SpiceCBwMNZin.txt")



### Crossover Network Design:

#### . 2nd Order Network:

Assuming  $Q_w := 0.5$   $f_w := 800$   $R_E = 5.33$

$$L_w := \frac{R_E}{2\pi f_w \cdot Q_w} \quad C_w := \frac{Q_w}{2\pi f_w \cdot R_E} \quad L_w = 2.121 \times 10^{-3} \quad C_w = 1.866 \times 10^{-5}$$

#### . 3rd Order Network:


$f_c = 72.764$   $f_w = 800$

$$L_2 := \frac{R_E}{4\pi f_w} \quad L_1 := 3L_2 \quad C_3 := \frac{2}{3\pi f_w \cdot R_E}$$

$$L_1 = 1.591 \times 10^{-3} \quad L_2 = 5.302 \times 10^{-4} \quad C_3 = 4.977 \times 10^{-5}$$

`SpcCBw2COSPL := READPRN("SpiceCBwMN2COSPL.txt")`
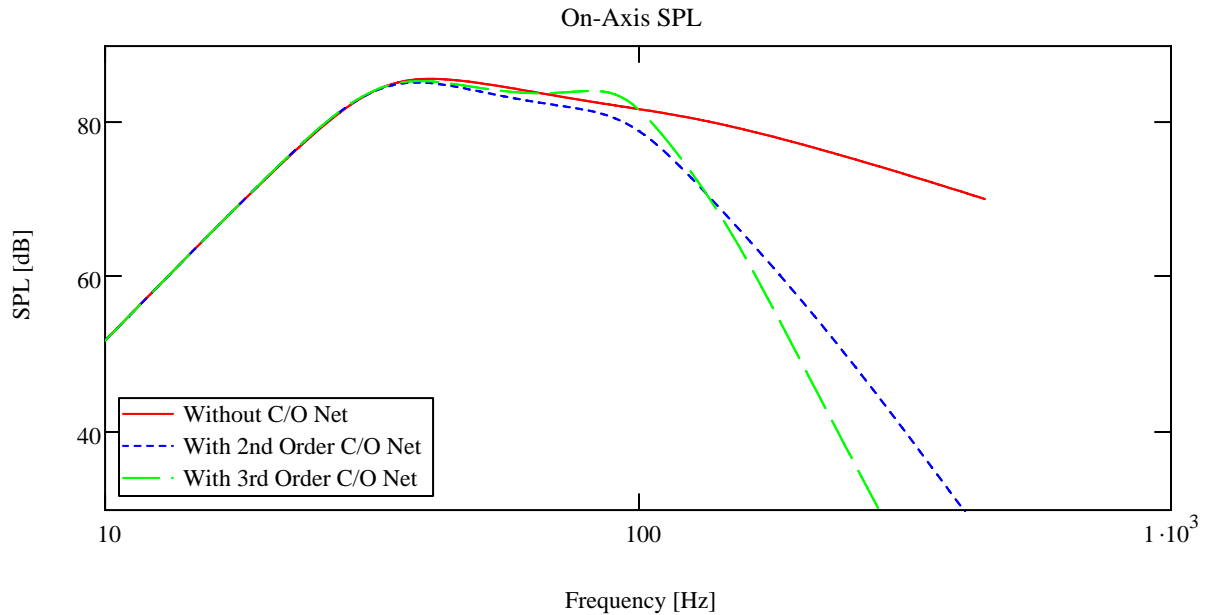
`SpcCBw3COSPL := READPRN("SpiceCBwMN3COSPL.txt")`



### Vented Box:

In this section, parameters are calculated to build the circuits that will simulate the behavior of the loudspeaker mounted inside a vented box. The electrical input impedance was measured, along with the sound pressure level and the peak displacement. The graph labeled "On-Axis SPL" shows the sound pressure levels produced by the diaphragm and the air in the vent, along with the total SPL. The plot labeled "Peak-to-Peak Displacement" shows the displacement of the diaphragm as well as the displacement of the air in the port.

$$d_w := 0.305 \quad \text{--> 12 in = woofer frame diameter}$$

$$a_w := 0.12 \quad \text{--> 12 cm = piston radius}$$

$$a_p := 0.04 \quad \text{--> 4 cm = port radius}$$

woofer-port spacing assumed to be 1.6 times the woofer frame radius, then:

$$d_1 := 0.8d_w \quad d_1 = 0.244$$

$$S_w := \pi a_w^2 \quad S_w = 0.045$$

$$B := 0.65 \quad \text{. --> Assumed Value (p.114)}$$

$$M_{AB} := \frac{B \cdot \rho_o}{\pi \cdot a_w} \quad M_{AB} = 2.035 \quad \text{Old Mab was 2.657}$$

$$C_{AB} = 3.304 \times 10^{-7}$$

$$Q_{TS} = 0.331 \quad Q_L := 7$$

With assumed  $Q_L=7$  and Alignment Chart on p.138:

$$h := 1.1998 \quad f_B := h \cdot f_S \quad f_B = 36.572$$

$$R_{AL} := \frac{Q_L}{2\pi f_B \cdot C_{AB}} \quad R_{AL} = 9.221 \times 10^4$$

$$M_{A1P} := \frac{8\rho_o}{3\pi \cdot a_p^2} \quad M_{A1P} = 7.971$$

$$M_{AP} := \frac{1}{(2\pi f_B)^2 \cdot C_{AB}} - M_{A1P} \quad M_{AP} = 49.355$$

$$R_{A2P} := \frac{\rho_o \cdot c}{\pi a_p^2} \quad R_{A2P} = 8.099 \times 10^4$$

$$R_{A1P} := \frac{128 \rho_o \cdot c}{9 \pi^3 \cdot a_p^2} - R_{A2P} \quad R_{A1P} = 3.572 \times 10^4$$

$$C_{A1P} := \frac{5.94 a_p^3}{\rho_o \cdot c^2} \quad C_{A1P} = 2.707 \times 10^{-9}$$

$$k_p := \frac{3 \pi a_p}{16 d_1} \quad k_p = 0.097$$

$$S_p := \pi a_p^2 \quad S_p = 5.027 \times 10^{-3}$$

$$M_{A1W} := \frac{8 \rho_o}{3 \pi^2 \cdot a_w} \quad M_{A1W} = 2.657$$

$$R_{A2W} := \frac{\rho_o \cdot c}{\pi a_w^2} \quad R_{A2W} = 8.999 \times 10^3$$

$$R_{A1W} := \frac{128 \rho_o \cdot c}{9 \pi^3 \cdot a_w^2} - R_{A2W} \quad R_{A1W} = 3.969 \times 10^3$$




$$C_{A1W} := \frac{5.94 a_w^3}{\rho_o \cdot c^2} \quad C_{A1W} = 7.308 \times 10^{-8}$$

$$k_w := \frac{3 \pi a_w}{16 d_1} \quad k_w = 0.29$$

SpcVBZin := READPRN("SpiceVBZin.txt")      SpcVBSPLv := READPRN("SpiceVBSPLv.txt")

SpcVBSPLw := READPRN("SpiceVBSPLw.txt")      SpcVBSPL := READPRN("SpiceVBSPL.txt")

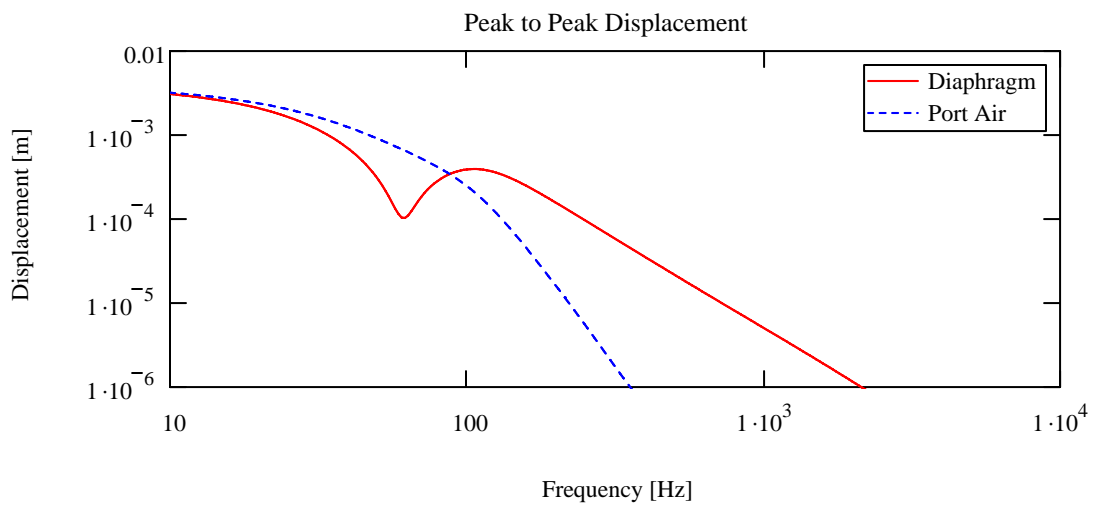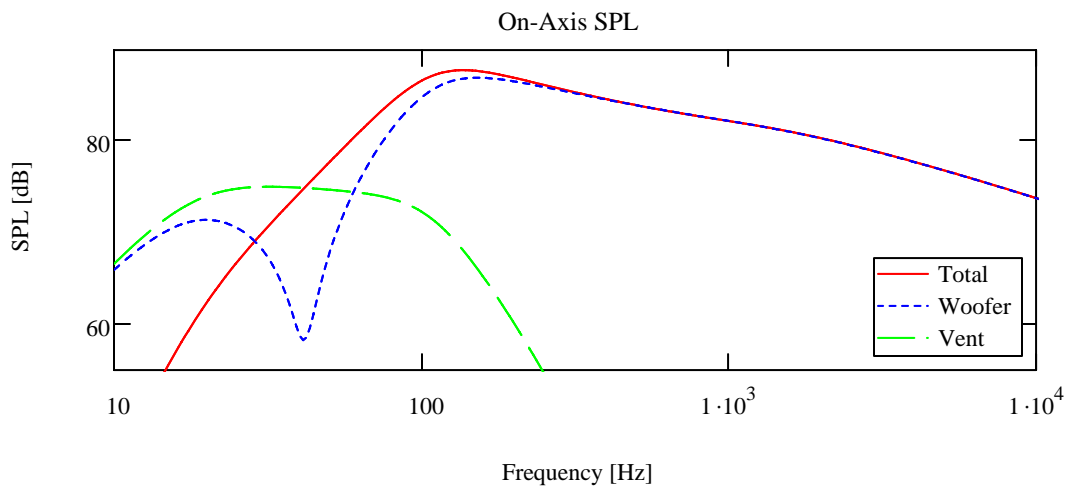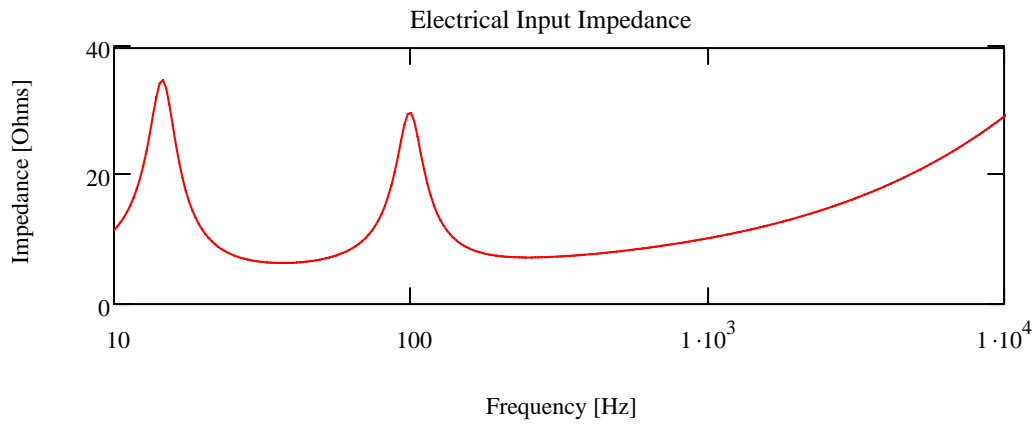SpcVBXppD := READPRN("SpiceVBXppD.txt")      SpcVBXppP := READPRN("SpiceVBXppP.txt")



## Summary and Conclusions

This report shows the result of simulating the behavior of a loudspeaker under different operating conditions. In the case of the closed box simulation, a matching network was placed in parallel with the voice coil. The purpose of this network is to cause the voice coil impedance to behave as if it were purely resistive, i.e. to cancel the peak at the resonant frequency as well as the high frequency rise due to the voice coil inductance. Furthermore, 2<sup>nd</sup> and 3<sup>rd</sup> order crossover networks were placed at the input of the voice coil circuit, i.e. before the matching network. The purpose of these networks is to allow only low frequencies to reach the woofer. The plots of the sound pressure level when using the crossover networks show how the slope of the magnitude Bode plot changes from -20 dB per decade (without C/O network) to -40 dB per decade (with 2<sup>nd</sup> order network) and -60 dB per decade (with a 3<sup>rd</sup> order crossover network).


In the case of the vented box, it is important to notice that the sound pressure level that we hear is the result of adding the SPL produced by the diaphragm and the SPL produced by the air in the port. In the plot showing the SPL of the vented box system, it is easy to notice that at some frequencies, the SPL produced by the air in the vent is considerably larger than the SPL produced by the diaphragm.




# **Appendix**

## SPICE Circuits and Netlists


## Infinite Baffle Circuits

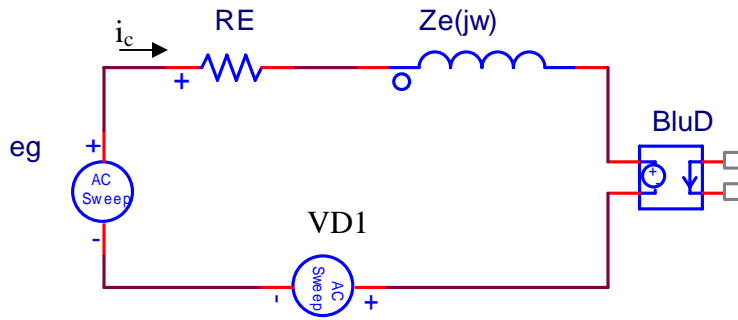

Electrical

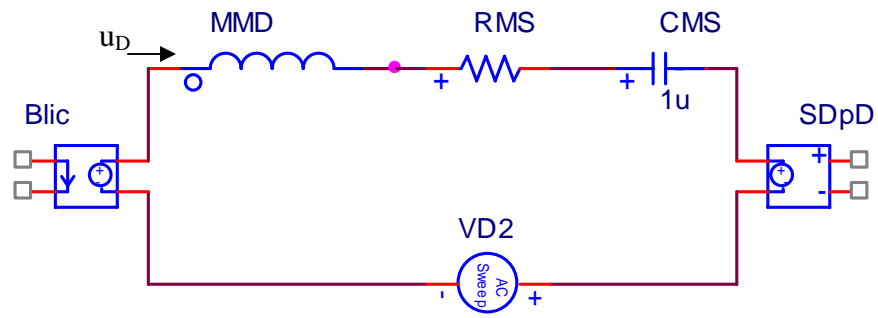


Mechanical

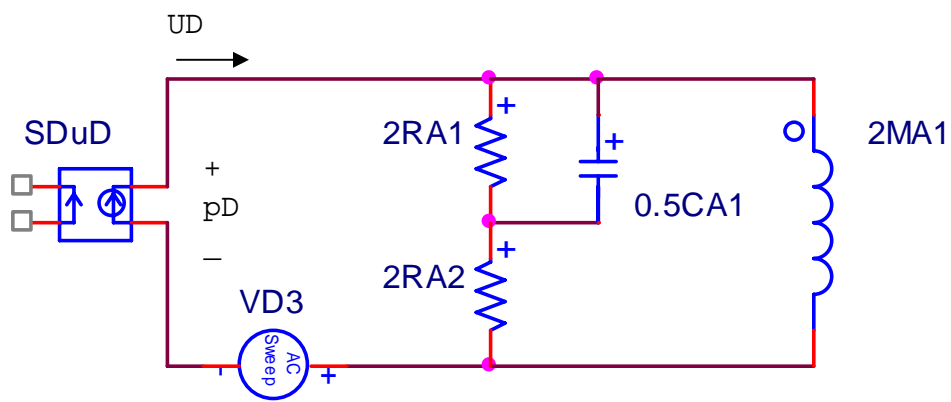


Acoustical


## Closed Box Circuits

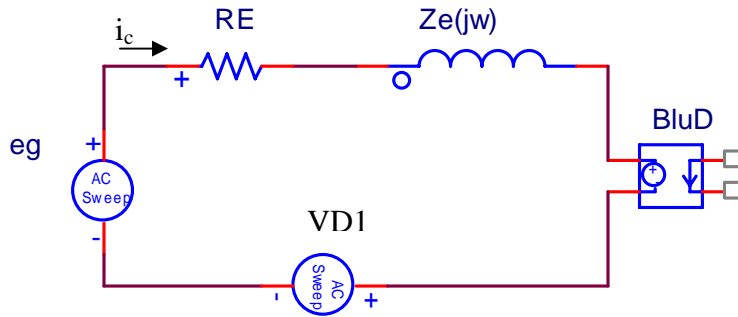


Electrical

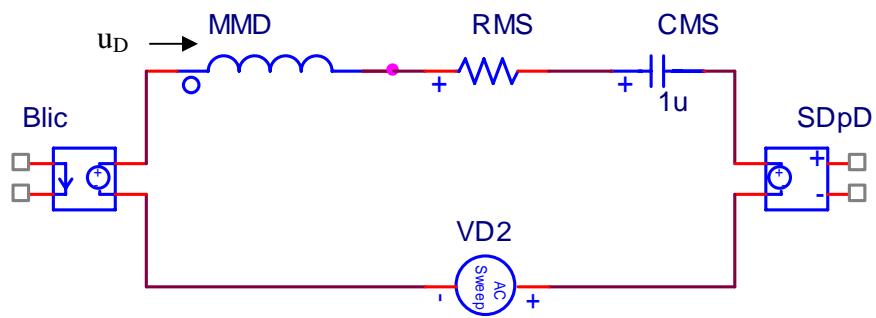


Mechanical

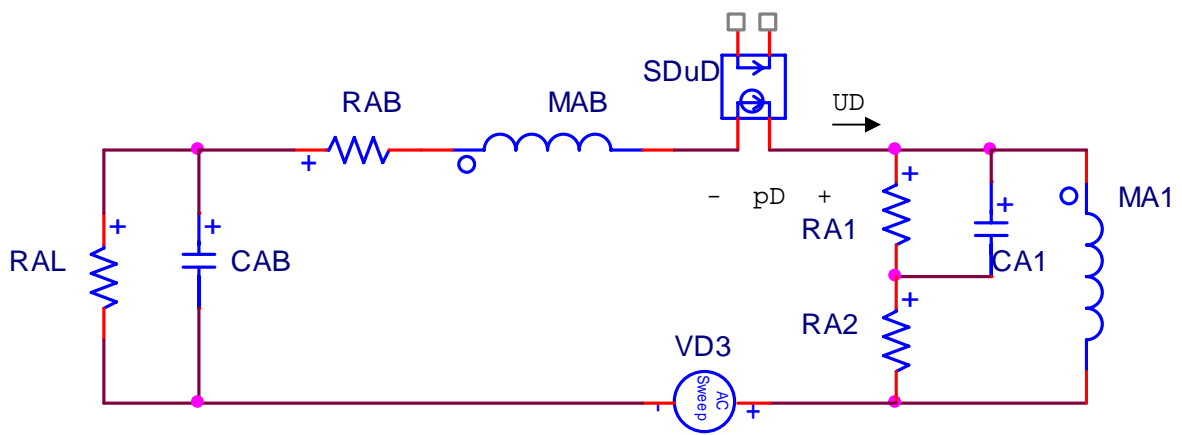


Acoustical

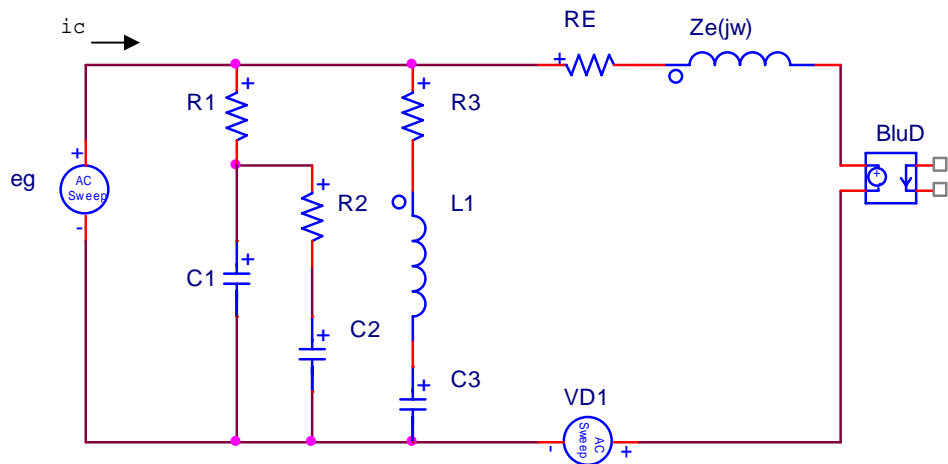

Electrical With Matching Network

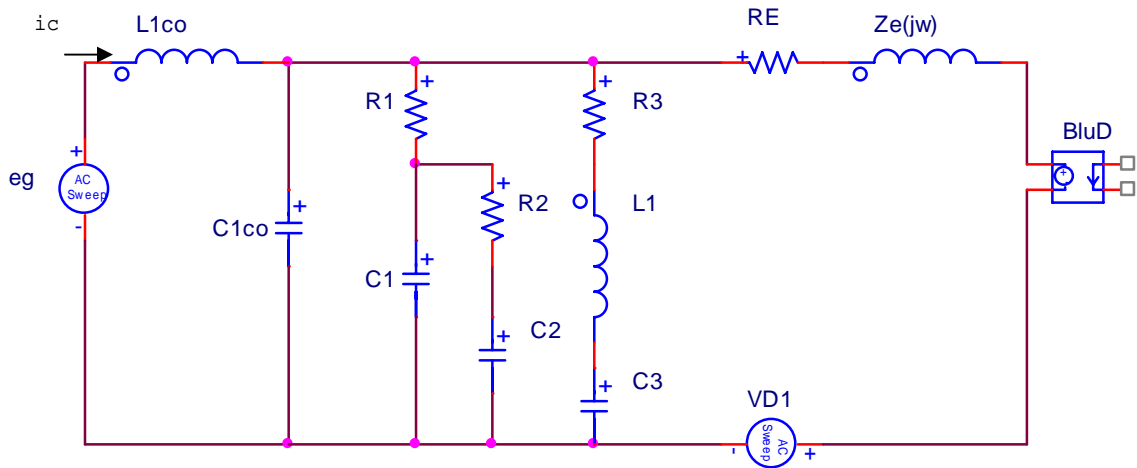


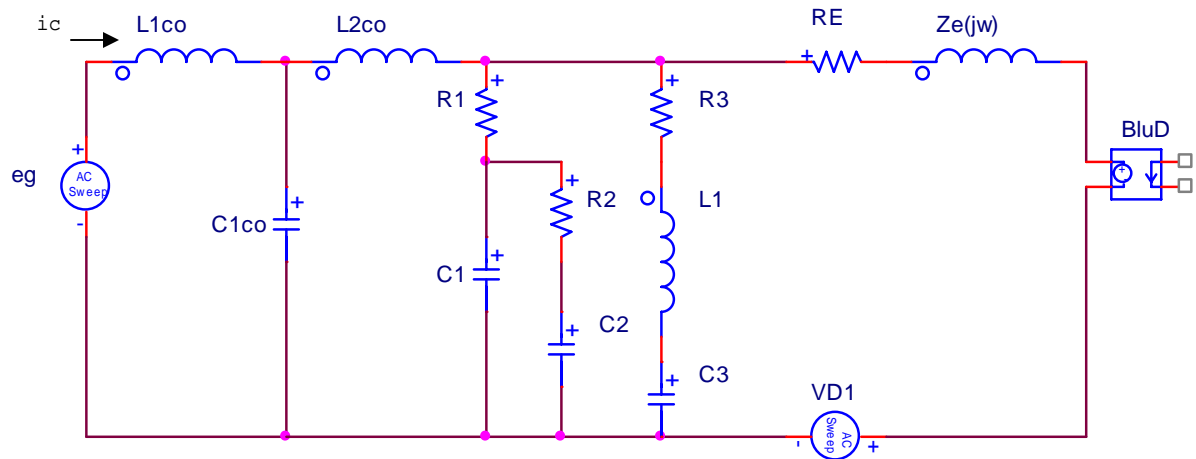Electrical With Matching Network and 2nd Order Crossover Network




Electrical With Matching Network and 3rd Order Crossover Network


## Vented Box Circuits

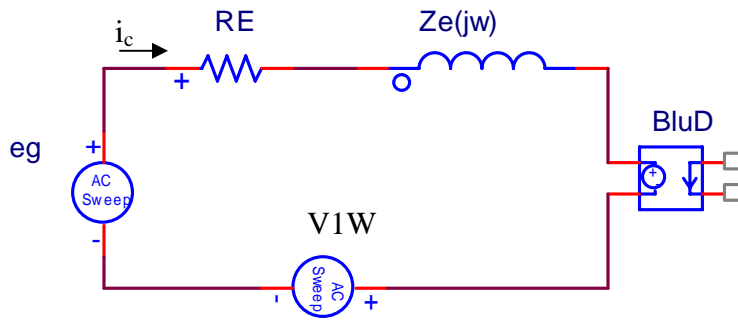

Electrical

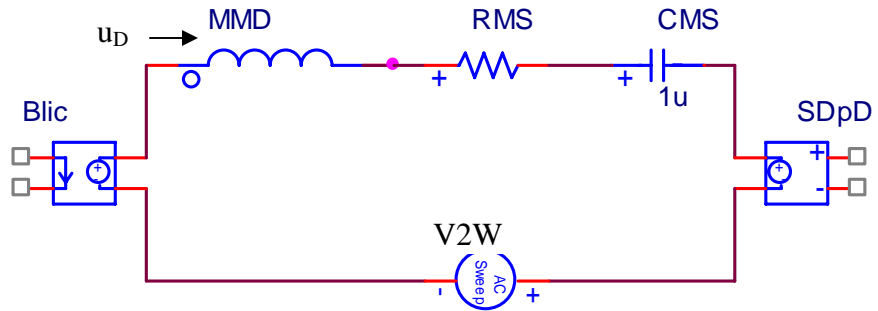

Mechanical

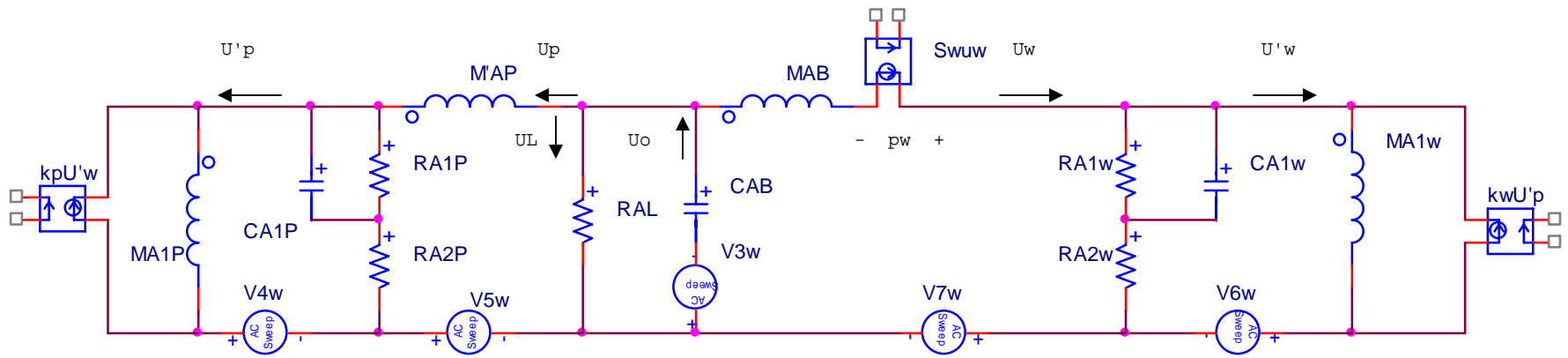

Acoustical

```

*-----
*Infinite Baffle
*-----
*INFINITE BAFFLE NETLIST
*DISPLAY VM(1)/IM(VD1) FOR INPUT IMPEDANCE
*DISPLAY 20*LOG10(VM(13)) FOR ON-AXIS PRESSURE
*DISPLAY VM(14) FOR DIAPHRAGM DISPLACEMENT

*ELECTRICAL CIRCUIT
VEG 1 0 AC 1V
RE 1 2 5.33
*LOSSY VOICE-COIL INDUCTANCE
GZE 2 3 LAPLACE {V(2,3)} = {1/(0.03*PWR(S,0.65))}
HBLUD 3 4 VD2 9.869
VD1 4 0 AC 0V

*MECHANICAL CIRCUIT
LMMD 5 6 0.025
RMS 6 7 2.544
CMS 7 8 7.584E-4
HBLIC 5 0 VD1 9.869
ESDPD 8 9 10 0 0.045
VD2 9 0 AC 0V

*ACOUSTICAL CIRCUIT
LMA1 10 12 5.314
RA1 10 11 7.938E3
RA2 11 12 17.998E3
CA1 10 11 3.654E-8
VD3 12 0 AC 0V
FSDUD 0 10 VD2 0.045

*ON-AXIS PRESSURE SOURCE
EPD 13 0 LAPLACE {I(VD3)} = {9390*S}
*DIAPHRAGM DISPLACEMENT SOURCE
EXD 14 0 LAPLACE {I(VD3)} = {1/S}

.AC DEC 77 10 100K
.PROBE
.END

```

```

*-----
*CLOSED-BOX
*-----
*DISPLAY VM(1)/IM(VD1) FOR INPUT IMPEDANCE
*DISPLAY 20*LOG10(16) FOR ON-AXIS PRESSURE
*DISPLAY VM(17) FOR DIAPHRAGM DISPLACEMENT

*ELECTRICAL CIRCUIT
VEG 1 0 AC 1V
RE 1 2 5.33
*LOSSY VOICE-COIL INDUCTANCE
GZE 2 3 LAPLACE {V(2,3)}={1/(0.03*PWR(S,0.65))}
HBLUD 3 4 VD2 9.869
VD1 4 0 AC 0

*MECHANICAL CIRCUIT
HBLI 5 0 VD1 9.869
LMMD 5 6 0.025
RMS 6 7 2.544
CMS 7 8 7.584E-4

```



ESDPD 8 9 10 13 0.045  
VD2 9 0 AC 0

\*ACOUSTICAL CIRCUIT  
FSDUD 13 10 VD2 0.045  
LMA1 10 12 2.657  
RA1 10 11 3.969E3  
RA2 11 12 9E3  
CA1 10 11 7.308E-8  
VD3 12 0 AC 0  
LMAB 13 14 2.657  
RAB 14 15 1.64E3  
CAB 15 0 3.304E-7  
RAL 15 0 4.818E6

\*ON-AXIS PRESSURE DISPLAYS IN PROBE WITH 20\*LOG10(VM(16))  
EXP 16 0 LAPLACE {I(VD3)} = {59E3\*S}  
\*DIAPHRAGM DIAPLACEMENT DISPLAYS IN PROBE WITH VM(17)  
EXD 17 0 LAPLACE {I(VD2)}={1/S}  
.AC DEC 50 10 10K  
.PROBE  
.END

\*-----  
\*CLOSED-BOX WITH MATCHING NETWORK  
\*-----  
\*DISPLAY VM(1)/IM(VD1) FOR INPUT IMPEDANCE  
\*DISPLAY 20\*LOG10(16) FOR ON-AXIS PRESSURE  
\*DISPLAY VM(17) FOR DIAPHRAGM DIAPLACEMENT

\*ELECTRICAL CIRCUIT  
VEG 1 0 AC 1V  
RE 1 2 5.33  
\*LOSSY VOICE-COIL INDUCTANCE  
GZE 2 3 LAPLACE {V(2,3)}={1/(0.03\*PWR(S,0.65))}  
HBLUD 3 4 VD2 9.869  
VD1 4 0 AC 0  
\*-----

\*Matching Network  
RR1 1 18 5.33  
CC1 18 0 2.054E-5  
RR2 18 19 2.484  
CC2 19 0 1.293E-5  
RR3 1 20 6.309  
LL1 20 21 0.01  
CC3 21 0 4.563E-4  
\*-----

\*MECHANICAL CIRCUIT  
HBLI 5 0 VD1 9.869  
LMMD 5 6 0.025  
RMS 6 7 2.544  
CMS 7 8 7.584E-4  
ESDPD 8 9 10 13 0.045  
VD2 9 0 AC 0

\*ACOUSTICAL CIRCUIT  
FSDUD 13 10 VD2 0.045  
LMA1 10 12 2.657  
RA1 10 11 3.969E3  
RA2 11 12 9E3  
CA1 10 11 7.308E-8

AllNets.txt

VD3 12 0 AC 0  
LMAB 13 14 2.657  
RAB 14 15 1.64E3  
CAB 15 0 3.304E-7  
RAL 15 0 4.818E6

\*ON-AXIS PRESSURE DISPLAYS IN PROBE WITH 20\*LOG10(VM(16))  
EXP 16 0 LAPLACE {I(VD3)} = {59E3\*S}  
\*DIAPHRAGM DISPLACEMENT DISPLAYS IN PROBE WITH VM(17)  
EXD 17 0 LAPLACE {I(VD2)}={1/S}  
. AC DEC 50 10 10K  
. PROBE  
. END

\*-----  
\*CLOSED-BOX WITH MATCHING NETWORK AND 2ND ORDER C/O NETWORK  
\*-----  
\*DISPLAY VM(1)/IM(VD1) FOR INPUT IMPEDANCE  
\*DISPLAY 20\*LOG10(16) FOR ON-AXIS PRESSURE  
\*DISPLAY VM(17) FOR DIAPHRAGM DISPLACEMENT

\*ELECTRICAL CIRCUIT  
VEG 1 0 AC 1V

\*-----  
\*2nd Order C/O Network  
LLw 1 2 2.121E-3  
CCw 2 0 1.866E-5

\*-----  
\*Matching Network  
RR1 2 3 5.33  
CC1 3 0 2.054E-5  
RR2 3 4 2.484  
CC2 4 0 1.293E-5  
RR3 2 18 6.309  
LL1 18 19 0.01  
CC3 19 0 4.563E-4

\*-----  
RE 2 20 5.33  
\*LOSSY VOICE-COIL INDUCTANCE  
GZE 20 21 LAPLACE {V(20,21)}={1/(0.03\*PWR(S,0.65))}  
HBLUD 21 22 VD2 9.869  
VD1 22 0 AC 0

\*-----  
\*MECHANICAL CIRCUIT  
HBLI 5 0 VD1 9.869  
LMMD 5 6 0.025  
RMS 6 7 2.544  
CMS 7 8 7.584E-4  
ESDPD 8 9 10 13 0.045  
VD2 9 0 AC 0

\*ACOUSTICAL CIRCUIT  
FSDUD 13 10 VD2 0.045  
LMA1 10 12 2.657  
RA1 10 11 3.969E3  
RA2 11 12 9E3  
CA1 10 11 7.308E-8  
VD3 12 0 AC 0  
LMAB 13 14 2.657  
RAB 14 15 1.64E3  
CAB 15 0 3.304E-7

RAL 15 0 4.818E6

\*ON-AXIS PRESSURE DISPLAYS IN PROBE WITH 20\*LOG10(VM(16))  
 EXP 16 0 LAPLACE {I(VD3)} = {59E3\*S}  
 \*DIAPHRAGM DISPLACEMENT DISPLAYS IN PROBE WITH VM(17)  
 EXD 17 0 LAPLACE {I(VD2)}={1/S}  
 . AC DEC 50 10 10K  
 . PROBE  
 . END

\*-----  
 \*CLOSED-BOX WITH MATCHING NETWORK AND 3RD ORDER C/O NETWORK  
 \*-----

\*DISPLAY VM(1)/IM(VD1) FOR INPUT IMPEDANCE  
 \*DISPLAY 20\*LOG10(16) FOR ON-AXIS PRESSURE  
 \*DISPLAY VM(17) FOR DIAPHRAGM DISPLACEMENT

\*ELECTRICAL CIRCUIT  
 VEG 1 0 AC 1V

\*-----  
 \*3rd Order C/O Network

LLco1 1 2 1.591E-3  
 CCco 2 0 4.977E-5  
 LLco2 2 3 5.302E-4

\*-----  
 \*Matching Network

RR1 3 4 5.33  
 CC1 4 0 2.054E-5  
 RR2 4 18 2.484  
 CC2 18 0 1.293E-5  
 RR3 3 19 6.309  
 LL1 19 20 0.01  
 CC3 20 0 4.563E-4

\*-----  
 RE 3 21 5.33  
 \*LOSSY VOICE-COIL INDUCTANCE  
 GZE 21 22 LAPLACE {V(21, 22)}={1/(0.03\*PWR(S, 0.65))}  
 HBLUD 22 23 VD2 9.869  
 VD1 23 0 AC 0

\*-----

\*MECHANICAL CIRCUIT  
 HBLI 5 0 VD1 9.869  
 LMMD 5 6 0.025  
 RMS 6 7 2.544  
 CMS 7 8 7.584E-4  
 ESDPD 8 9 10 13 0.045  
 VD2 9 0 AC 0

\*ACOUSTICAL CIRCUIT  
 FSDUD 13 10 VD2 0.045  
 LMA1 10 12 2.657  
 RA1 10 11 3.969E3  
 RA2 11 12 9E3  
 CA1 10 11 7.308E-8  
 VD3 12 0 AC 0  
 LMAB 13 14 2.657  
 RAB 14 15 1.64E3  
 CAB 15 0 3.304E-7  
 RAL 15 0 4.818E6

```
*ON-AXIS PRESSURE DISPLAYS IN PROBE WITH 20*LOG10(VM(16))
EXP 16 0 LAPLACE {I(VD3)} = {59E3*S}
*DIAPHRAGM DI SPLACEMENT DISPLAYS IN PROBE WITH VM(17)
EXD 17 0 LAPLACE {I(VD2)}={1/S}
.AC DEC 50 10 10K
.PROBE
.END
```

```
*-----
*VENTED-BOX
*-----
```

```
*DI SPLAY VM(1)/IM(VD1) FOR INPUT IMPEDANCE
*DI SPLAY VM(21) FOR DIAPHRAGM DI SPLACEMENT
*DI SPLAY VM(22) FOR PORT DI SPLACEMENT
*DI SPLAY 20*LOG10(VM(23)) FOR ON-AXIS PRESSURE
*DI SPLAY 20*LOG10(VM(24)) FOR DIAPHRAGM PRESSURE
*DI SPLAY 20*LOG10(VM(25)) FOR PORT PRESSURE
```

```
*ELECTRICAL CIRCUIT
```

```
VEG 1 0 AC 1V
REW 1 2 5.33
*LOSSY VOICE-COIL INDUCTANCE
GRA 2 3 LAPLACE {V(2,3)}={1/(0.03*PWR(S,0.65))}
HBLUW 3 4 V2W 9.869
V1W 4 0 AC OV
```

```
*Mechanical Ckt
```

```
HBLIW 5 0 V1W 9.869
LMMDW 5 6 0.025
RMSW 6 7 2.544
CMSW 7 8 7.584E-4
ESDPW 8 9 17 10 0.045
V2W 9 0 AC OV
```

```
*Acoustical CKT
```

```
FSDUW 10 17 V2W 0.045
LMABW 10 11 2.035
CABW 11 12 3.304E-7
V3W 0 12 AC 0
RALW 11 0 9.221E4
LMAP 11 13 49.355
FKP 15 13 V6W 0.097
LMA1P 13 15 7.971
RA1P 13 14 3.572E4
CA1P 13 14 2.707E-9
RA2P 14 16 8.099E4
V4W 15 16 AC OV
V5W 16 0 AC OV
FKWUP 19 17 V4W 0.29
LMA1W 17 19 2.657
RA1W 17 18 3.969E3
CA1W 17 18 7.308E-8
RA2W 18 20 9E3
V6W 19 20 AC OV
V7W 20 0 AC OV
```

```
*DIAPHRAGM DI SPLACEMENT SOURCE
EXD 21 0 LAPLACE {I(V2W)}={1/S}
```

AllNets.txt

```
*PORT DI S PLACEMENT SOURCE
EXP 22 0 LAPLACE {I (V5W)}={1/(5.027E-3*S)}
*ON-AXIS PRESSURE SOURCE
EPSUM 23 0 LAPLACE {I (V3W)}={9390*S}
*DIAPHRAGM PRESSURE SOURCE
EPD 24 0 LAPLACE {I (V7W)}={9390*S}
*VENT PRESSURE SOURCE
EPV 25 0 LAPLACE {I (V5W)}={9390*S}
.AC DEC 100 10 10K
.PROBE
.END
```