

ECE 3040 Microelectronic Circuits Quiz 3


June 2, 2004

Professor Leach

Name _____

Instructions. Print your name in the space above. The quiz is closed-book and closed-notes. The quiz consists of 2 problems. **Honor Code Statement:** *I have neither given nor received help on this quiz.*
 Initials _____

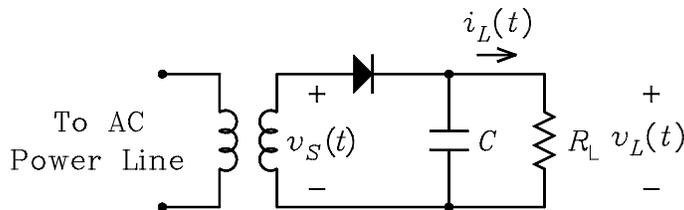1. (a) What are the two diode reverse breakdown mechanisms called? *Answer:* Zener and avalanche.
 (b) Draw the symbol for a Zener diode. (See the notes or book)
 (c) What are the two charge storage mechanisms in a diode called? Which dominates for a forward biased diode and is it determined by a voltage or a current? Which dominates for a reverse biased diode and is it determined by a voltage or a current? *Answer:* Junction (or depletion) charge and diffusion charge. The diffusion charge dominates in a forward biased diode and is determined by the current. The junction (or depletion) charge dominates in a reverse biased diode and is determined by the voltage.
 (d) Describe the construction of a Schottky barrier diode and draw its symbol. *Answer:* It is a metal (aluminum) to semiconductor (n-type) junction. See notes or book for diagram.
2. A half-wave rectifier circuit is shown. It is given that $v_S(t)$ is a 60 Hz sinusoidal voltage with an rms value of 24 V. When the diode is forward biased, its voltage drop is $V_{D0} = 0.6$ V. The circuit values are $R_L = 200 \Omega$ and $C = 1000 \mu\text{F}$.



- (a) Calculate the peak load voltage. *Answer:* $v_{L(\text{peak})} = 24\sqrt{2} - 0.6 = 33.34$ V
- (b) Calculate the maximum reverse bias voltage across the diode. *Answer:* $33.341 - (-24\sqrt{2}) = 67.282$ V
- (c) The percent ripple is given by $\% \text{ ripple} = [1 - \exp(-T/R_L C)] \times 100\%$. When the diode is off, what is the lowest value that the load voltage can “droop” to before the diode conducts again? *Answer:*

$$\% \text{ ripple} = \left[1 - \exp\left(\frac{-1}{60 \times 200 \times 1000 \times 10^{-6}}\right) \right] \times 100\% = 7.996\%$$

$$v_{AC} = 33.341 \times \frac{7.996}{100} = 2.666 \text{ V}$$

$$v_{\text{droop}} = 33.341 - 2.666 = 30.675 \text{ V}$$