

# ECE 3050 Analog Electronics Quiz 1

August 26, 2009


Professor Leach      Last Name: \_\_\_\_\_ First Name: \_\_\_\_\_

**Instructions. Print** your name in the spaces above. Place a box around any answer. **Honor Code Statement:**

*I have neither given nor received help on this quiz.* Initials \_\_\_\_\_

1 of 2. For  $v_s = 5\text{ V}$ ,  $R_1 = 11\text{ k}\Omega$ ,  $R_2 = 1.1\text{ k}\Omega$ , and  $g_m = 1/20$ :

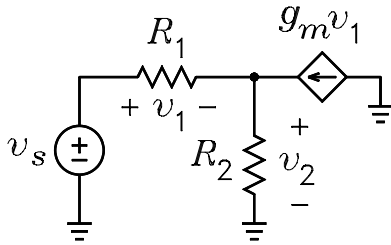- (a) Use superposition, voltage division, current division, and Ohm's Law to solve for  $v_1$ .  
 (b) Use the values of  $v_s$  and  $v_1$  to solve for  $v_2$ .



$$R_1 := 11000 \quad R_2 := 1100 \quad v_s := 5 \quad g_m := \frac{1}{20}$$

$$v_1 = v_s \cdot \frac{R_1}{R_1 + R_2} - g_m \cdot v_1 \cdot R_2$$

$$v_1 := v_s \cdot \frac{R_1}{1 + g_m \cdot R_2 \cdot (R_1 + R_2)} \quad v_1 = 0.089$$

$$v_2 := v_s - v_1 \quad v_2 = 4.911$$

2 of 2. (a) With the aid of a graph, illustrate how the value of the diode small-signal resistance is defined. [It is the reciprocal of the slope of the  $i_D$  versus  $v_D$  graph.]

(b) Draw and label the hybrid- $\pi$  model of the BJT.