

ECE 3050 Analog Electronics Quiz 6


September 30, 2009

Professor Leach

Name _____

Instructions. Print your name in the space above. Place a box around your answers. Points will be subtracted if you do not express each numerical answer as a decimal number and if you do not put a box around answers. **Honor Code Statement:** *I have neither given nor received help on this quiz.* Initials _____

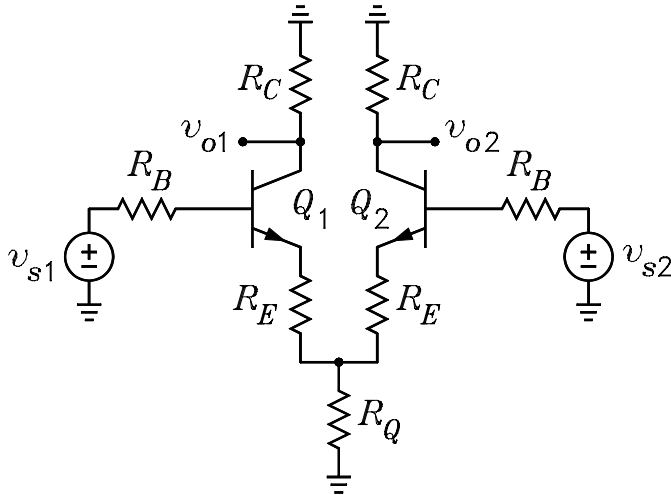1. The figure shows the ac signal circuit for a differential amplifier. For each BJT, it is given that $\alpha = 0.99$, $\beta = 99$, $r_x = 0$, $g_m = 49.5 \text{ mS}$, $r_\pi = 2 \text{ k}\Omega$, $r_e = 20 \Omega$, $r_o = \infty$, $R_B = 1 \text{ k}\Omega$, $R_E = 70 \Omega$, $R_Q = 50 \text{ k}\Omega$, and $R_C = 12 \text{ k}\Omega$.
 - (a) Replace v_{s1} and v_{s2} with differential inputs. Solve for the differential gain $A_{v(d)} = v_{o1}/v_{id}$.
 - (b) Replace v_{s1} and v_{s2} with common-mode inputs. Solve for the common-mode gain $A_{v(cm)} = v_{o1}/v_{icm}$.
 - (c) What is the common-mode rejection ratio?



Solutions on next page.

$$\alpha := 0.99 \quad \beta := 99 \quad g_m := 49.5 \cdot 10^{-3} \quad r_\pi := 2000 \quad r_e := 20 \quad R_B := 1000$$

$$R_E := 70 \quad R_Q := 50000 \quad R_C := 12000 \quad r'_e := \frac{R_B}{1 + \beta} + r_e \quad r'_e = 30$$

You were expected to use the small-signal models to arrive at the following answers:

$$(a) \quad v_{i1} = \frac{v_{id}}{2} \quad v_{i2} = \frac{-v_{id}}{2} \quad v_{o1} = -i'_{c1} \cdot R_C = -\alpha \cdot i'_{e1} \cdot R_C = -\alpha \cdot \frac{v_{id}}{r'_e + R_E} \cdot R_C$$

$$A_{vd} = \frac{v_{o1}}{v_{id}} \quad A_{vd} := \frac{\frac{-\alpha \cdot R_C}{2}}{r'_e + R_E} \quad A_{vd} = -59.4$$

$$(b) \quad v_{i1} = v_{icm} \quad v_{i2} = v_{icm} \quad v_{o1} = -i'_{c1} \cdot R_C = -\alpha \cdot i'_{e1} \cdot R_C = -\alpha \cdot \frac{v_{icm}}{r'_e + R_E + 2 \cdot R_Q} \cdot R_C$$

$$A_{vcm} = \frac{v_{o1}}{v_{icm}} \quad A_{vcm} := \frac{-\alpha \cdot R_C}{r'_e + R_E + 2 \cdot R_Q} \quad A_{vcm} = -0.119$$

$$(c) \quad CMRR := \left| \frac{A_{vd}}{A_{vcm}} \right| \quad CMRR = 500.5$$

$$CMRR_{dB} := 20 \cdot \log(CMRR) \quad CMRR_{dB} = 53.988$$