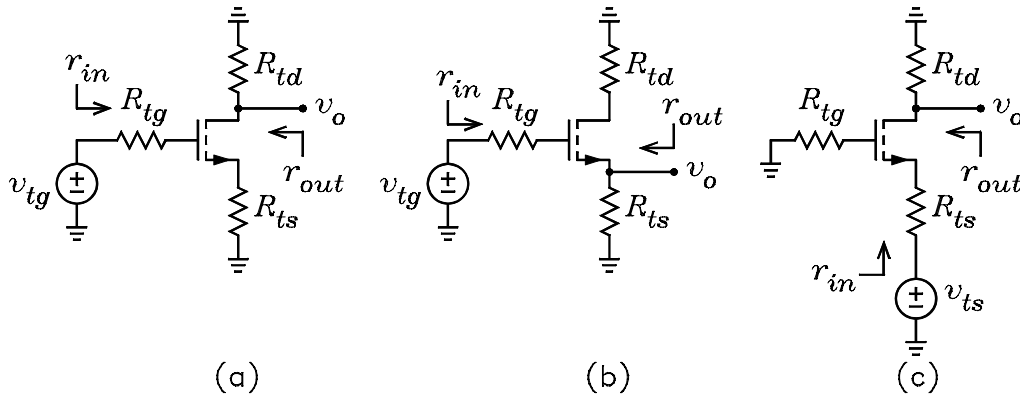


## ECE3050 Homework Set 10

The figures show a common-source amplifier, a common-drain amplifier, and a common-gate amplifier. For each circuit, it is given that  $R_{tg} = 1\text{ k}\Omega$ ,  $R_{ts} = 100\ \Omega$ , and  $R_{td} = 10\text{ k}\Omega$ . The transistors have the parameters  $I_D = 1.5\text{ mA}$ ,  $V_{DS} = 10\text{ V}$ ,  $K = 0.005\text{ A/V}^2$ , and  $\lambda = 0\text{ V}^{-1}$ .



1. For each transistor, show that  $g_m = 1/182.6\text{ S}$ ,  $r_s = 182.6\ \Omega$ , and  $r_0 = \infty\text{ k}\Omega$ .
2. For the common-source amplifier of Figure (a):

(a) Replace the MOSFET with the T model or simplified T model and show that

$$v_o = -i'_d R_{td} = -10^4 i'_d$$

$$i'_d = i'_s = \frac{v_{tg}}{r_s + R_{ts}} = \frac{v_{tg}}{282.6}$$

$$\frac{v_o}{v_{tg}} = \frac{-R_{td}}{r_s + R_{ts}} = -35.4$$

(b) Replace the MOSFET with the  $\pi$  model and show that

$$v_o = -i'_d R_{td} = -10^4 i'_d$$

$$i'_d = \frac{v_{tg}}{\frac{1}{g_m} + R_{ts}} = \frac{v_{tg}}{282.6}$$

$$\frac{v_o}{v_{tg}} = \frac{-R_{td}}{\frac{1}{g_m} + R_{ts}} = -35.4$$

3. For the common-drain amplifier of Figure (b):

(a) Use the T model or simplified T model to show that

$$\frac{v_o}{v_{tg}} = \frac{R_{ts}}{r_s + R_{ts}} = 0.354$$

$$r_{out} = R_{ts} \parallel r_s = 64.61\ \Omega$$

(b) Use the  $\pi$  model to show that

$$\frac{v_o}{v_{tg}} = \frac{R_{ts}}{\frac{1}{g_m} + R_{ts}} = 0.354$$

$$r_{out} = R_{ts} \parallel \frac{1}{g_m} = 64.61 \Omega$$

4. For the common-gate amplifier of Figure (c)

(a) Use the T model or simplified T model to show that

$$\frac{v_o}{v_{ts}} = \frac{-1}{r_s + R_{ts}} \times (-R_{td}) = \frac{R_{td}}{r_s + R_{ts}} = 35.4$$

$$r_{out} = R_{td} = 10 \text{ k}\Omega$$

(b) Use the  $\pi$  model to show that

$$\frac{v_o}{v_{ts}} = \frac{-1}{\frac{1}{g_m} + R_{ts}} \times (-R_{td}) = \frac{R_{td}}{\frac{1}{g_m} + R_{ts}} = 35.4$$

$$r_{out} = R_{td} = 10 \text{ k}\Omega$$

5. What are the new answers to problems 4 through 6 if the body lead connects to ac ground and  $\chi = 0.3$ ? Answers: For problem 2,  $v_o/v_{tg} = -32.0$  and  $r_{out} = 10 \text{ k}\Omega$ . For problem 3,  $v_o/v_{tg} = 0.32$  and  $r_{out} = 58.4 \Omega$ . For problem 4,  $v_o/v_{ts} = 32$  and  $r_{out} = 10 \text{ k}\Omega$ .