


ECE3050 – Assignment 17

1. The figures show inverting amplifier circuits.


(a) For the circuit of Fig. (a), specify R_1 , R_F , and R_O for a voltage gain of -50 , an input resistance of $2\text{ k}\Omega$, and an output resistance of $1\text{ k}\Omega$. If the op amp clips at a peak output voltage of 12 V , specify the maximum peak input voltage if the op amp is not to be driven into clipping. Answers: $R_1 = 2\text{ k}\Omega$, $R_F = 100\text{ k}\Omega$, $R_O = 1\text{ k}\Omega$, and $|v_{I(peak)}| = 0.24\text{ V}$.

(b) Fig. (b) shows the circuit of Fig. (a) with a load resistor connected to the output. Calculate the new voltage gain if $R_L = 1\text{ k}\Omega$. What is the maximum peak output voltage if the op amp is not to clip? Answers: $v_O/v_I = -25$ and $|v_{O(peak)}| = 6\text{ V}$.


(c) Repeat part (b) if the circuit is modified as shown in Fig. (c). Answers: $v_O/v_I = -50$ and $|v_{O(peak)}| = 5.97\text{ V}$. Hint, use voltage division to solve for $|v_{O(peak)}|$ in terms of $|v'_{O(peak)}|$.

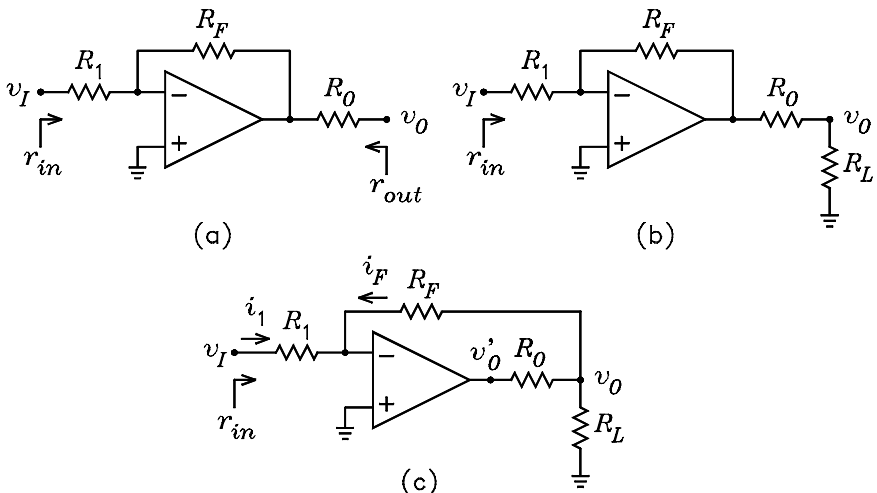

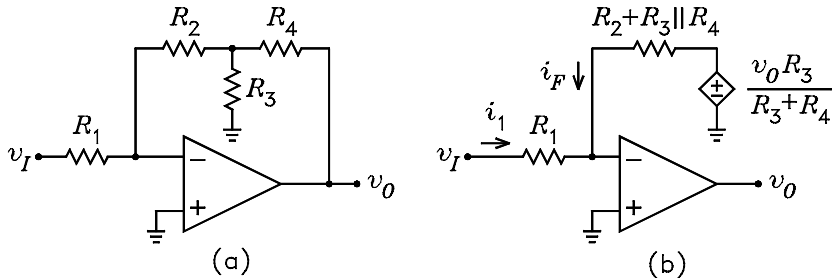
2. Fig. (a) shows an inverting amplifier with a T feedback network. Fig. (b) shows the amplifier with a Thévenin equivalent made looking into the feedback network from the input. The amplifier is to be designed for an input resistance of $1\text{ k}\Omega$ and a voltage gain of -1000 . If $R_2 = R_4$ and $R_3 = 100\ \Omega$, specify the value of R_2 and R_4 . Answers: $R_1 = 1\text{ k}\Omega$ and $R_2 = R_4 = 9.9005\text{ k}\Omega$.



3. Show that the same expression for the voltage gain of the circuit in figure (a) of problem 2 is obtained if Norton equivalent circuits are made looking out of the negative input through R_1 and R_2 and the sum of the two Norton currents is set to zero. Hint: First show that the Norton current looking into R_2 is $[v_O / (R_4 + R_2 || R_3)] \times R_3 / (R_2 + R_3)$.
4. The figure shows a current to voltage converter. The circuit is to be designed to convert an input current of $-50 \mu\text{A}$ into an output voltage of $+4 \text{V}$.

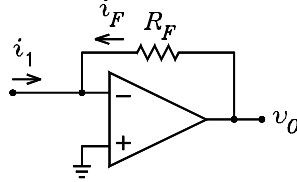


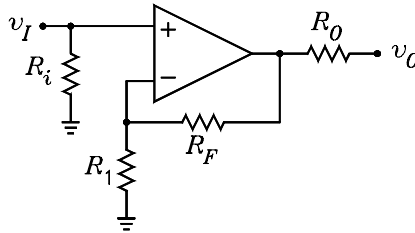- (a) Calculate the required value of R_F . Answer: $R_F = 80 \text{ k}\Omega$.
 - (b) If the op amp clips at a peak output voltage of 12V , calculate the maximum peak input current. Answer: $i_{1(\text{peak})} = 150 \mu\text{A}$.
 - (c) The circuit is driven from an amplifier which can be modeled by a voltage-controlled voltage source with an open-circuit voltage gain of 10 and an output resistance of $2 \text{ k}\Omega$. Calculate the overall voltage gain of the two circuits in combination. Answer: $v_O/v_I = -400$.
5. The figure shows a non-inverting amplifier. The circuit is to be designed for an input resistance of $10 \text{ k}\Omega$, and output resistance of 100Ω , and an open-circuit voltage gain of 20. When the peak output voltage is 10V , the current through R_F and R_1 is to be 0.2 mA . Specify the resistors in the circuit. Answers: $R_i = 10 \text{ k}\Omega$, $R_O = 100 \Omega$, $R_1 = 2.5 \text{ k}\Omega$, and $R_F = 47.5 \text{ k}\Omega$.




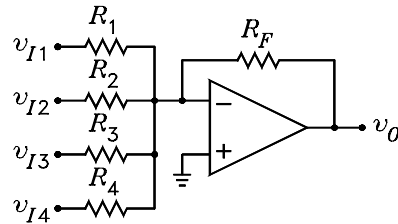6. For the inverting amplifier circuit of Fig. (c) in Problem 1, let the open-loop gain of the op amp be denoted by A . In this case, the open-circuit output voltage is given by $v_O = A(v_+ - v_-)$.
 - (a) Solve for v_O as a function of v_I , R_1 , R_F , and A
 - (b) If $A \rightarrow \infty$, what is v_O given by?
7. Repeat Problem 5 for the non-inverting amplifier of Problem 4.
8. The figure shows a 4 input inverting summer. The circuit is to be designed for an output voltage given by $v_O = -(2v_{I1} + 4v_{I2} + 6v_{I3} + 8v_{I4})$. When the peak output


voltage is 10 V, the current through R_F is to be 0.5 mA. Specify the resistors in the circuit. Answers: $R_F = 20 \text{ k}\Omega$, $R_1 = 10 \text{ k}\Omega$, $R_2 = 5 \text{ k}\Omega$, $R_3 = 3.33 \text{ k}\Omega$, and $R_4 = 2.5 \text{ k}\Omega$.



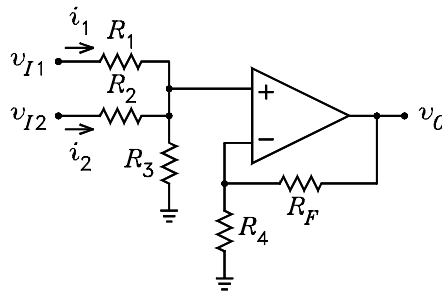9. The figure shows a non-inverting summer. The gain v_O/v_+ is specified to be 50. If $R_3 = R_4 = 1 \text{ k}\Omega$, specify R_1 , R_2 , and R_F for an output voltage given by $v_O = 5v_{I1} + 2v_{I2}$. Answers: $R_F = 49 \text{ k}\Omega$, $R_1 = 8.6 \text{ k}\Omega$, and $R_2 = 21.5 \text{ k}\Omega$.



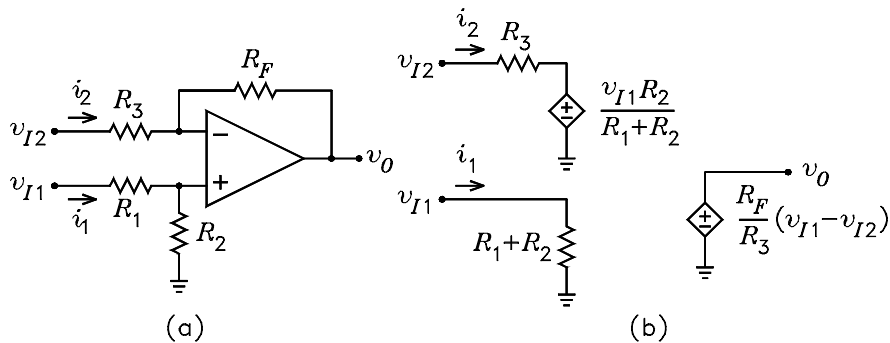
10. Fig. (a) shows a differential amplifier. Fig. (b) shows the equivalent circuit for the special case $R_1 = R_3$ and $R_2 = R_F$. It is desired to design the circuit so that $v_O = 10(v_{I1} - v_{I2})$. In addition, the input resistance seen between the two input nodes is to be $10 \text{ k}\Omega$.




- (a) Specify the resistors in the circuit. Answers: $R_1 = R_3 = 5 \text{ k}\Omega$, $R_2 = R_F = 50 \text{ k}\Omega$.
 (b) For $v_{I2} = 0$, solve for the resistance seen looking into the v_{I1} input. Answer: $55 \text{ k}\Omega$.
 (c) For $v_{I1} = 0$, solve for the resistance seen looking into the v_{I2} input. Answer: $5 \text{ k}\Omega$.

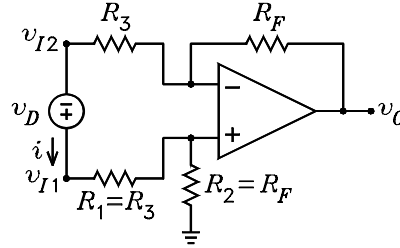11. The figure shows a differential amplifier with a source connected between its two inputs.

The circuit elements values are the same as those found in problem 10. Solve for the voltage gain v_O/v_D , v_{I1} , v_{I2} , the voltage at each op amp input, and the common-mode input voltage v_{ICM} . Answers: $v_O/v_D = 10$, $v_{I1} = 5.5v_D$, $v_{I2} = 4.5v_D$, $v_+ = v_- = 5v_D$, $v_{ICM} = v_O/2 = 5v_D$.



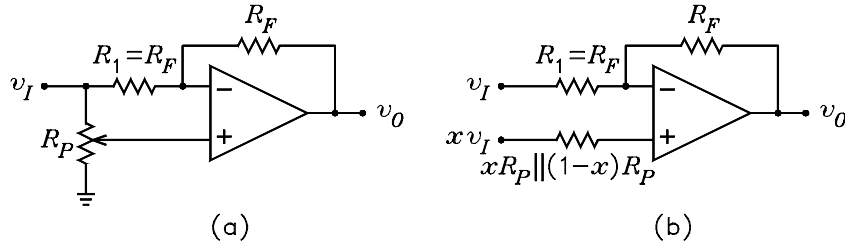12. Fig. (a) shows a switch hitter circuit. Fig. (b) shows the equivalent circuit which can be used to calculate v_O . It is given that $R_1 = R_F = 10\text{ k}\Omega$, $R_P = 100\text{ k}\Omega$, the resistance below the potentiometer wiper is xR_P , and the resistance above the wiper is $(1-x)R_P$, where $0 \leq x \leq 1$. Note that $xR_P + (1-x)R_P = R_P$.




(a) Prove that the Thévenin equivalent circuit seen looking out of the v_+ input is the one shown in Fig. (b). What is the maximum source resistance of this Thévenin circuit? Answer: $25\text{ k}\Omega$.


(b) Solve for v_O . Answer: $v_O = (2x - 1)v_I$.

(c) The v_I node of the switch hitter is connected to the v_{I1} input of the inverting summer in problem 8. The v_O node is connected to the v_{I2} input of the inverting summer. The other inputs to the inverting summer are connected to ground. Solve for v_O of the inverting summer. Answer: $v_O = (2 - 8x)v_I$.

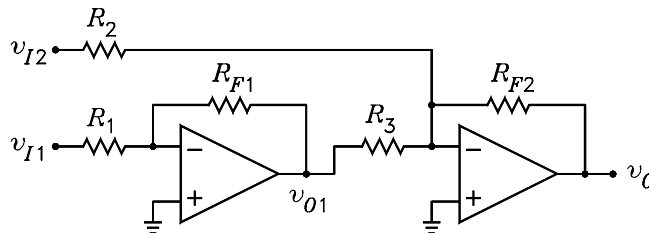
13. The figure shows a two op amp diff amp. Design the circuit for an output voltage given by $v_O = 50(v_{I1} - v_{I2})$. The input resistance to each input is to be $5\text{ k}\Omega$. Answers: $R_1 = R_2 = R_{F1} = R_3 = 5\text{ k}\Omega$, $R_{F2} = 250\text{ k}\Omega$.



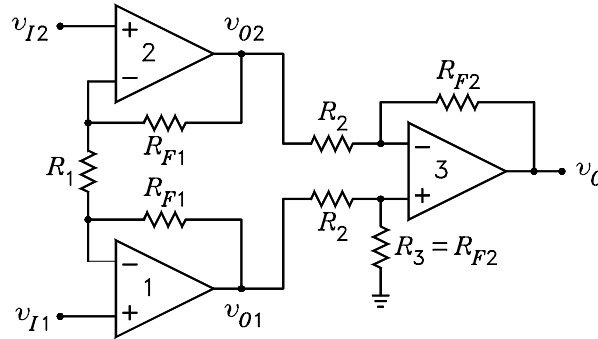
14. The figure shows a three op amp instrumentation amplifier. (a) Design the circuit such that $v_{O1} - v_{O2} = 10(v_{I1} - v_{I2})$ and $v_O = 10(v_{O1} - v_{O2})$. Answers: $1 + 2R_{F1}/R_1 = 10$, choose $R_1 = 2 \text{ k}\Omega$ and $R_{F1} = 9 \text{ k}\Omega$, $R_{F2}/R_2 = 10$, choose $R_{F2} = 10 \text{ k}\Omega$, and $R_2 = 1 \text{ k}\Omega$. (b) For $v_{I1} = 0.03 \text{ V}$ and $v_{I2} = 0.01 \text{ V}$, calculate v_{O1} , v_{O2} , and v_O . Answers: $v_{O1} = 0.12 \text{ V}$, $v_{O2} = -0.08 \text{ V}$, and $v_O = 2 \text{ V}$.



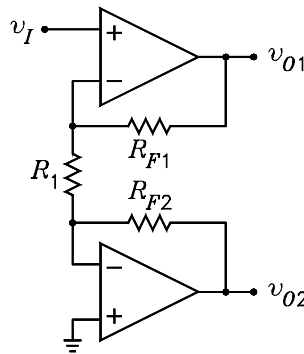
15. The figure shows a balanced output amplifier. Design the circuit so that $v_{O1} = -v_{O2} = 6v_I$. When $v_{O1} = \pm 12 \text{ V}$ and $v_{O2} = \mp 12 \text{ V}$, the current through R_{F1} and R_{F2} is not to exceed 1 mA . Answers: for 1 mA , $R_1 = 2 \text{ k}\Omega$, $R_{F1} = 10 \text{ k}\Omega$, and $R_{F2} = 12 \text{ k}\Omega$.



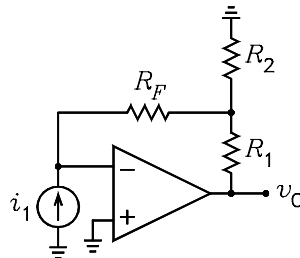16. For the circuit shown, show that the Thévenin equivalent circuit seen looking into R_F from the v_- node consists of the voltage $v_O R_2 / (R_1 + R_2)$ in series with the resistance $R_F + R_1 \parallel R_2$. Use superposition to show that $v_- = i_1 (R_F + R_1 \parallel R_2) + v_O R_2 / (R_1 + R_2)$. Set $v_- = 0$ to show that $v_O = -i_1 [R_1 + R_F (1 + R_1/R_2)]$.



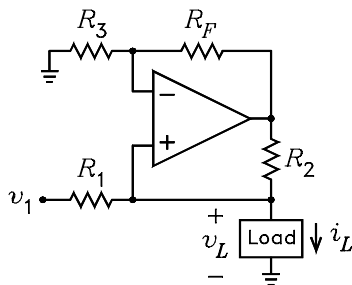17. For the circuit shown, let v_O be the op amp output voltage.



- (a) With the load open circuited, i.e. $i_L = 0$, use superposition of v_1 and v_O to show that $v_{L(oc)} = (v_1 R_2 + v_O R_1) / (R_1 + R_2)$. Show that $v_O = v_{L(oc)} (1 + R_F/R_3)$.
 (a) Solve the equations from the previous part to show that

$$v_{L(oc)} = v_1 \frac{\frac{R_2}{R_1 + R_2}}{1 - \frac{R_1}{R_1 + R_2} \left(1 + \frac{R_F}{R_3}\right)}$$


- (b) With the load short circuited, i.e. $v_L = 0$, show that $i_{L(sc)} = v_1/R_1$.
 (c) The load sees a source resistance given by $v_{L(oc)}/i_{L(sc)}$. Show that this is infinite if

$$\frac{R_3}{R_3 + R_F} = \frac{R_1}{R_1 + R_2}$$


- (d) When the above equation holds, show that the load current is given by $i_L = v_1/R_1$ and that this is independent of v_L . Hint, solve for the Norton equivalent circuit seen by the load.

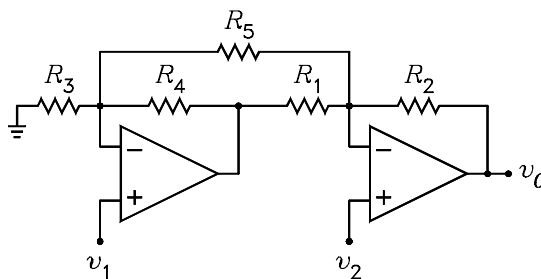18. For the circuit shown, use superposition of v_1 and v_2 to show that v_O is given by


$$v_O = -v_1 \left[\left(1 + \frac{R_4}{R_3 \parallel R_5}\right) \frac{R_2}{R_1} + \frac{R_2}{R_5} \right] + v_2 \left(1 + \frac{R_2}{R_1 \parallel R_5} + \frac{R_4}{R_5} \frac{R_2}{R_1}\right)$$



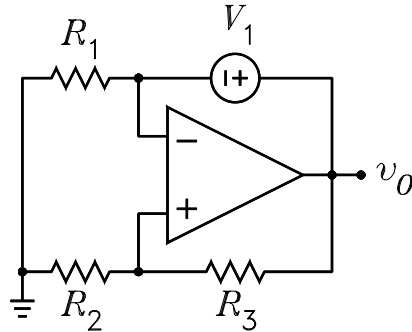
19. For $R_1 = 10\text{ k}\Omega$, $R_2 = 30\text{ k}\Omega$, $R_3 = 20\text{ k}\Omega$, and $V_1 = 4\text{ V}$, show that $v_O = 10\text{ V}$. Hint: The answer is independent of R_1 .



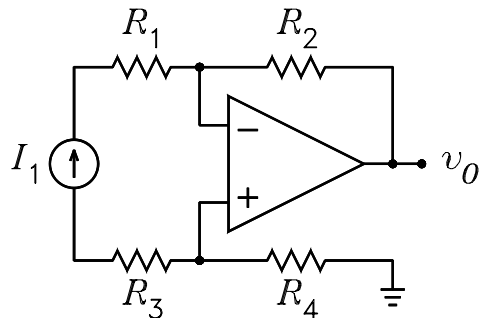
20. For $I_1 = 1\text{ mA}$, $R_1 = 3\text{ k}\Omega$, $R_2 = 4\text{ k}\Omega$, $R_3 = 2\text{ k}\Omega$, and $R_4 = 1\text{ k}\Omega$, show that $v_O = -5\text{ V}$. Hint: The answer is independent of R_1 and R_2 .



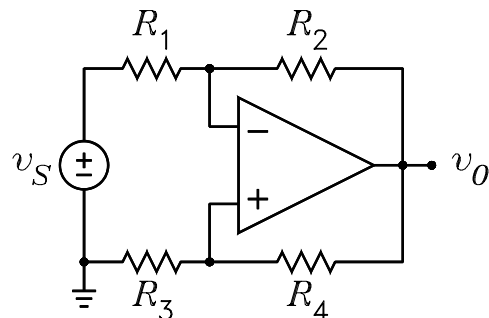21. For $R_1 = 50\text{ k}\Omega$, $R_2 = 20\text{ k}\Omega$, $R_3 = 10\text{ k}\Omega$, and $R_4 = 40\text{ }\Omega$, show that $v_O/v_S = 5/9$.




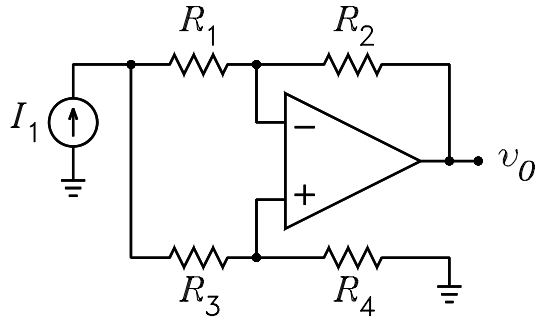22. For $I_1 = 1\text{ mA}$, $R_1 = 3\text{ k}\Omega$, $R_2 = 4\text{ k}\Omega$, $R_3 = 2\text{ k}\Omega$, and $R_4 = 1\text{ k}\Omega$, show that $v_O = -1\text{ V}$. Hint: Use superposition of I_1 and v_O to solve for the voltage at the two op-amp inputs. Set the voltages equal to each other to solve for v_O .



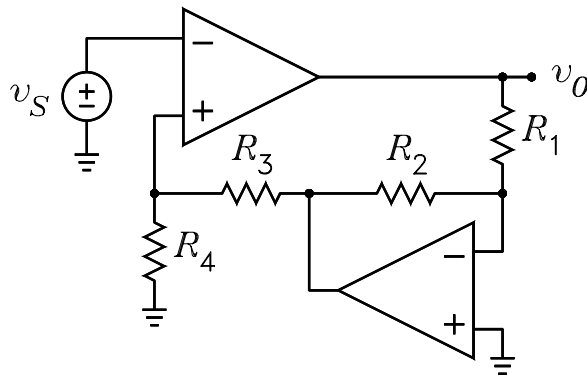23. Show that

$$\frac{v_O}{v_S} = -\frac{R_1}{R_2} \left(1 + \frac{R_3}{R_4} \right)$$



24. The figure shows a Schmitt trigger. It is given that $V_{SAT} = 12\text{ V}$ and $R_F = 10\text{ k}\Omega$. Solve for V_{REF} and R_1 for $V_A = -4\text{ V}$ and $V_B = +2\text{ V}$. Answers: $R_1 = 3.33\text{ k}\Omega$, $V_{REF} = -1.33\text{ V}$.

