

BJT Single Stage Amplifier Circuits

ECE 3050 – Analog Electronics

The Common-Emitter Amplifier

The common-emitter amplifier is used to obtain a high voltage gain and a high input resistance. The circuit in Fig. 1(a) shows the ac signal circuit. The input source is represented by a Thévenin equivalent connected to the base. The output is taken from the collector. We assume that the dc bias solution is known and that the BJT is biased in its active mode. The small-signal parameters r_e , r'_e , and r_0 are given by

$$r_e = \frac{V_T}{I_E} \quad r'_e = \frac{R_{tb} + r_x}{1 + \beta} + r_e \quad r_0 = \frac{V_A + V_{CE}}{I_C}$$

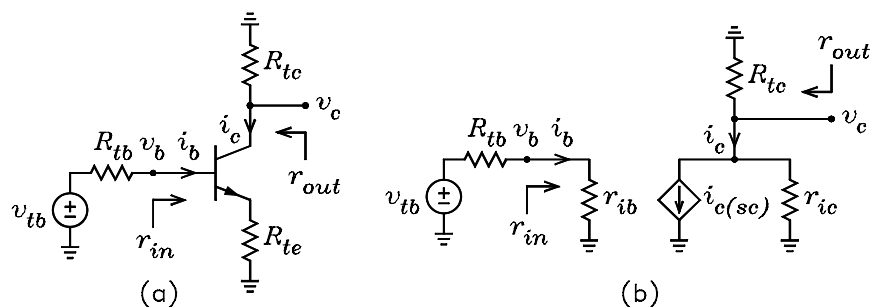


Figure 1: (a) Ac signal circuit of the common-emitter amplifier. (b) Equivalent input and output circuits.

The circuit in Fig. 1(b) shows the equivalent input and output circuits. The collector output voltage is given by

$$v_c = -i_{c(sc)}(r_{ic} \parallel R_{tc}) = -G_{mb}v_{tb}(r_{ic} \parallel R_{tc})$$

It follows that the voltage gain from v_{tb} to v_c is given by

$$A_v = \frac{v_c}{v_{tb}} = -G_{mb}(r_{ic} \parallel R_{tc})$$

where

$$G_{mb} = \frac{\alpha}{r'_e + R_{te} \parallel r_0} \frac{r_0 - R_{te}/\beta}{r_0 + R_{te}}$$

$$r_{ic} = \frac{r_0 + r'_e \parallel R_{te}}{1 - \alpha R_{te}/(r'_e + R_{te})}$$

Note that the voltage gain is negative. This means that the CE amplifier is an inverting amplifier.

The output resistance seen looking into the v_c node is

$$r_{out} = r_{ic} \parallel R_{tc}$$

The input resistance seen looking into the v_b node is

$$r_{ib} = r_x + (1 + \beta) r_e + R_{te} \frac{(1 + \beta) r_0 + R_{tc}}{r_0 + R_{te} + R_{tc}}$$

When the r_0 approximations are used, G_{mb} and r_{ib} are replaced with

$$G_{mb} \simeq \frac{\alpha}{r'_e + R_{te}}$$

$$r_{ib} \simeq r_x + (1 + \beta) (r_e + R_{te})$$

Example 1 Fig. 2 shows the circuit diagrams of NPN and PNP single-stage CE amplifiers. For each circuit, it is given that $R_S = 5 \text{ k}\Omega$, $R_1 = 120 \text{ k}\Omega$, $R_2 = 100 \text{ k}\Omega$, $R_C = 4.3 \text{ k}\Omega$, $R_E = 5.6 \text{ k}\Omega$, $R_3 = 100 \Omega$, $R_L = 20 \text{ k}\Omega$, $V^+ = 15 \text{ V}$, $V^- = -15 \text{ V}$, $V_{BE} = 0.65 \text{ V}$, $\beta = 99$, $\alpha = 0.99$, $r_x = 20 \Omega$, $V_A = 100 \text{ V}$ and $V_T = 0.025 \text{ V}$. Solve for the gain $A_v = v_o/v_s$, the input resistance r_{in} , and the output resistance r_{out} . The capacitors can be assumed to be ac short circuits at the operating frequency.

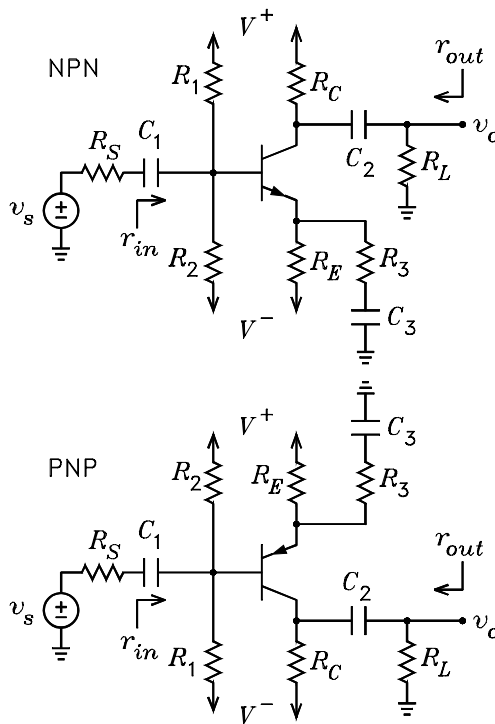


Figure 2: Single-stage CE amplifiers.

Solution. For the dc bias solution, replace all capacitors with open circuits. For the NPN circuit, the Thévenin voltage and resistance seen looking out of the base are

$$V_{BB} = \frac{V^+ R_2 + V^- R_1}{R_1 + R_2} = -1.364 \text{ V} \quad R_{BB} = R_1 || R_2 = 54.55 \text{ k}\Omega$$

The Thévenin voltage and resistance seen looking out of the emitter are $V_{EE} = V^-$ and $R_{EE} = R_E$. The bias equation for I_E is

$$I_E = \frac{V_{BB} - V_{EE} - V_{BE}}{R_{BB}/(1 + \beta) + R_{EE}} = 2.113 \text{ mA}$$

To test for the active mode, we calculate the collector-base voltage

$$V_{CB} = V_C - V_B = (V^+ - \alpha I_E R_C) - \left(V_{BB} - \frac{I_E}{1 + \beta} R_{BB} \right) = 8.521 \text{ V}$$

Because this is positive, the BJT is biased in its active mode.

For the small-signal ac analysis, we need r_0 and r_e . To calculate r_0 , we first calculate the collector-emitter voltage

$$V_{CE} = V_{CB} + V_{BE} = 9.171 \text{ V}$$

It follows that r_0 and r_e have the values

$$r_0 = \frac{V_A + V_{CE}}{\alpha I_E} = 52.18 \text{ k}\Omega \quad r_e = \frac{V_T}{I_E} = 11.83 \text{ }\Omega$$

For the small-signal analysis, V^+ and V^- are zeroed and the three capacitors are replaced with ac short circuits. The Thévenin voltage and resistance seen looking out of the base are given by

$$v_{tb} = v_s \frac{R_1 \| R_2}{R_S + R_1 \| R_2} = 0.916 v_s \quad R_{tb} = R_S \| R_1 \| R_2 = 4.58 \text{ k}\Omega$$

The Thévenin resistances seen looking out of the emitter and the collector are

$$R_{te} = R_E \| R_3 = 98.25 \text{ }\Omega \quad R_{tc} = R_C \| R_L = 3.539 \text{ k}\Omega$$

Next, we calculate r'_e , G_{mb} , r_{ic} , and r_{ib} .

$$r'_e = \frac{R_{tb} + r_x}{1 + \beta} + r_e = 57.83 \text{ }\Omega$$

$$G_{mb} = \frac{\alpha}{r'_e + R_{te} \| r_0} \frac{r_0 - R_{te}/\beta}{r_0 + R_{te}} = \frac{1}{157.8} \text{ S}$$

$$r_{ic} = \frac{r_0 + r'_e \| R_{te}}{1 - \alpha R_{te}/(r'_e + R_{te})} = 138.6 \text{ k}\Omega$$

$$r_{ib} = r_x + (1 + \beta) r_e + R_{te} \frac{(1 + \beta) r_0 + R_{tc}}{r_0 + R_{te} + R_{tc}} = 10.39 \text{ k}\Omega$$

The output voltage is given by

$$v_o = -G_{mb} (r_{ic} \| R_{tc}) v_{tb} = -G_{mb} (r_{ic} \| R_{tc}) \times 0.916 v_s = -20.04 v_s$$

Thus the voltage gain is $A_v = -20.04$. The input and output resistances are given by

$$r_{in} = R_1 \| R_2 \| r_{ib} = 8.73 \text{ k}\Omega \quad r_{out} = R_{tc} = 3.539 \text{ k}\Omega$$

The solutions for the PNP amplifier are the same as for the NPN circuit.

Example 2 If the r_0 approximations are used, calculate the new voltage gain and input resistance for the CE amplifiers.

Solution. Only G_{mb} and r_{ib} change. The approximate values are given by

$$G_{mb} \simeq G_m = \frac{\alpha}{r'_e + R_{te}} = 157.7 \text{ S} \quad r_{ib} \simeq r_x + (1 + \beta)(r_e + R_{te}) = 11.03 \text{ k}\Omega$$

The new voltage gain and input resistance are given by

$$A_v = -G_m (r_{ic} \parallel R_{tc}) \times 0.916 = -20.05 \quad r_{in} = R_1 \parallel R_2 \parallel r_{ib} = 9.173 \text{ k}\Omega$$

Note that there is very little change in the value of A_v .

The Common-Base Amplifier

The common-base amplifier is used to obtain a high voltage gain and a low input resistance. The circuit in Fig. 3(a) shows the ac signal circuit. The input source is represented by a Thévenin equivalent connected to the emitter. The output is taken from the collector. We assume that the dc bias solution is known and that the BJT is biased in its active mode. The small-signal parameters r_e , r'_e , and r_0 are given by

$$r_e = \frac{V_T}{I_E} \quad r'_e = \frac{R_{tb} + r_x}{1 + \beta} + r_e \quad r_0 = \frac{V_A + V_{CE}}{I_C}$$

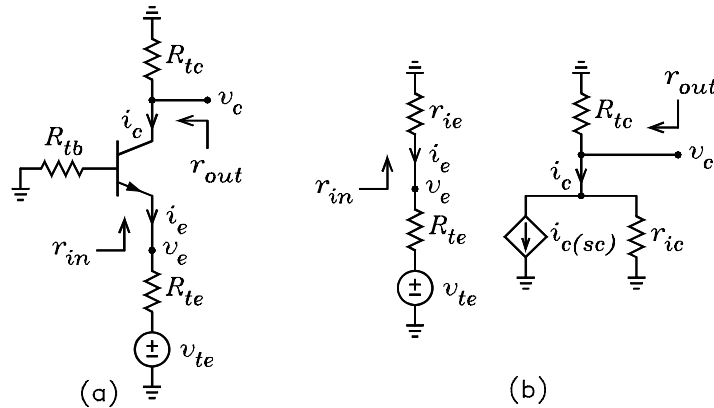


Figure 3: (a) Ac signal circuit of the common-base amplifier. (b) Equivalent input and output circuits.

The circuit in Fig. 1(b) shows the equivalent input and output circuits. The collector output voltage is given by

$$v_c = -i_{c(sc)} (r_{ic} \parallel R_{tc}) = G_{me} v_{te} (r_{ic} \parallel R_{tc})$$

It follows that the voltage gain is given by

$$A_v = \frac{v_c}{v_{te}} = G_{me} (r_{ic} \parallel R_{tc})$$

where

$$G_{me} = \frac{1}{R_{te} + r'_e \parallel r_0} \frac{\alpha r_0 + r'_e}{r_0 + r'_e}$$

$$r_{ic} = \frac{r_0 + r'_e \parallel R_{te}}{1 - \alpha R_{te} / (r'_e + R_{te})}$$

Note that the voltage gain is positive. This means that the CB amplifier is a non-inverting amplifier.

The output resistance seen looking into the v_c node is

$$r_{out} = r_{ic} \parallel R_{tc}$$

The input resistance seen looking into the v_e node is

$$r_{ie} = r'_e \frac{r_0 + R_{tc}}{r'_e + r_0 + R_{tc} / (1 + \beta)}$$

When the r_0 approximations are used, G_{me} and r_{ie} are replaced with

$$G_{me} \simeq G_m = \frac{\alpha}{r'_e + R_{te}}$$

$$r_{ie} \simeq r'_e$$

Example 3 Fig. 4 shows the circuit diagrams of NPN and PNP single-stage CB amplifiers. For each circuit, it is given that $R_S = 100 \Omega$, $R_1 = 120 \text{ k}\Omega$, $R_2 = 100 \text{ k}\Omega$, $R_C = 4.3 \text{ k}\Omega$, $R_E = 5.6 \text{ k}\Omega$, $R_3 = 100 \Omega$, $R_L = 20 \text{ k}\Omega$, $V^+ = 15 \text{ V}$, $V^- = -15 \text{ V}$, $V_{BE} = 0.65 \text{ V}$, $\beta = 99$, $\alpha = 0.99$, $r_x = 20 \Omega$, $V_A = 100 \text{ V}$ and $V_T = 0.025 \text{ V}$. Solve for the gain $A_v = v_o/v_s$, the input resistance r_{in} , and the output resistance r_{out} . The capacitors can be assumed to be ac short circuits at the operating frequency.

Solution. Because the dc bias circuits are the same as for the common-emitter amplifiers, the bias currents and voltages are the same. In addition, r_e and r_0 are the same.

For the small-signal analysis, V^+ and V^- are zeroed and the three capacitors are replaced with ac short circuits. The Thévenin voltage and resistance seen looking out of the emitter are given by

$$v_{te} = v_s \frac{R_E}{R_S + R_E} = 0.9825 v_s \quad R_{te} = R_S \parallel R_E = 98.25 \Omega$$

The Thévenin resistances seen looking out of the base and the collector are

$$R_{tb} = 0 \quad R_{tc} = R_C \parallel R \parallel L = 3.539 \text{ k}\Omega$$

Next, we calculate r'_e , G_{me} , r_{ic} , and r_{ie} .

$$r'_e = \frac{R_{tb} + r_x}{1 + \beta} + r_e = 12.03 \Omega$$

$$G_{me} = \frac{1}{R_{te} + r'_e \parallel r_0} \frac{\alpha r_0 + r'_e}{r_0 + r'_e} = \frac{1}{111.4} \text{ S}$$

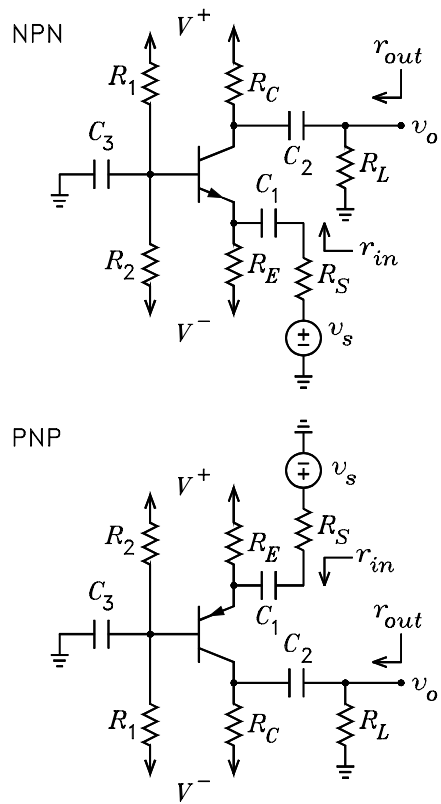


Figure 4: Single-stage common-base amplifiers.

$$r_{ic} = \frac{r_0 + r'_e \parallel R_{te}}{1 - \alpha R_{te} / (r'_e + R_{te})} = 442.3 \text{ k}\Omega$$

$$r_{ie} = r'_e \frac{r_0 + R_{tc}}{r'_e + r_0 + R_{tc} / (1 + \beta)} = 12.83 \Omega$$

The output voltage is given by

$$v_o = G_{me} (r_{ic} \parallel R_{tc}) v_{te} = G_{me} (r_{ic} \parallel R_{tc}) \times 0.9825 v_s = 30.97 v_s$$

Thus the voltage gain is $A_v = 30.97$. The input and output resistances are given by

$$r_{in} = R_1 \parallel R_2 \parallel r_{ib} = 12.81 \Omega \quad r_{out} = R_{tc} = 4.259 \text{ k}\Omega$$

The solutions for the PNP amplifier are the same as for the NPN circuit.

Example 4 *If the r_0 approximations are used, calculate the new voltage gain and input resistance for the CB amplifiers.*

Solution. Only G_{me} and r_{ie} change. The approximate values are given by

$$G_{me} \simeq G_m = \frac{\alpha}{r'_e + R_{te}} = \frac{1}{111.4} \text{ S} \quad r_{ie} \simeq r'_e = 12.03 \text{ k}\Omega$$

The new voltage gain and input resistance are given by

$$A_v = G_m (r_{ic} \parallel R_{tc}) \times 0.9825 = 30.97 \quad r_{in} = R_E \parallel r_{ie} = 12 \Omega$$

To 4 significant places, there is no change in the value of A_v .

The Common-Collector Amplifier

The common-collector amplifier is used to obtain a voltage gain that is approximately unity and a high input resistance. The circuit in Fig. 5(a) shows the ac signal circuit. The input source is represented by a Thévenin equivalent connected to the base. The output is taken from the emitter. We assume that the dc bias solution is known and that the BJT is biased in its active mode. The small-signal parameters r_e , r'_e , and r_0 are given by

$$r_e = \frac{V_T}{I_E} \quad r'_e = \frac{R_{tb} + r_x}{1 + \beta} + r_e \quad r_0 = \frac{V_A + V_{CE}}{I_C}$$

The circuit in Fig. 1(b) shows the equivalent input and output circuits. The emitter output voltage is given by

$$v_e = v_{e(oc)} \frac{R_{te}}{r_{ie} + R_{te}}$$

where

$$v_{e(oc)} = v_{tb} \frac{r_0 + R_{tc} / (1 + \beta)}{r'_e + r_0 + R_{tc} / (1 + \beta)}$$

It follows that the voltage gain from v_{tb} to v_e is given by

$$A_v = \frac{v_e}{v_{tb}} = \frac{R_{te}}{r_{ie} + R_{te}} \frac{r_0 + R_{tc} / (1 + \beta)}{r'_e + r_0 + R_{tc} / (1 + \beta)}$$

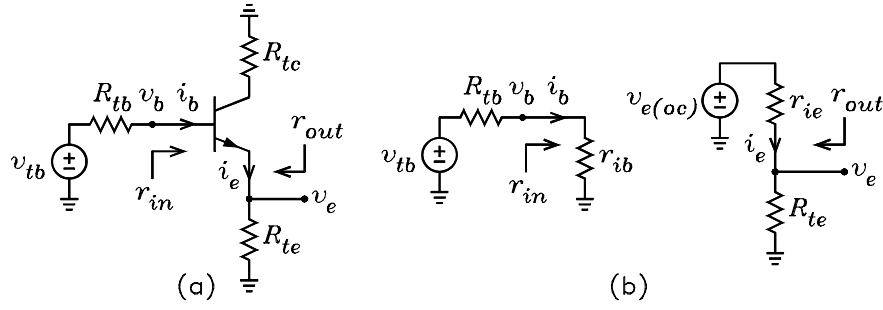


Figure 5: (a) Ac signal circuit of the common-collector amplifier. (b) Equivalent input and output circuits.

where

$$r_{ie} = r'_e \frac{r_0 + R_{tc}}{r'_e + r_0 + R_{tc}/(1 + \beta)}$$

Note that the voltage gain is positive. This means that the CC amplifier is a non-inverting amplifier.

The output resistance seen looking into the v_e node is

$$r_{out} = r_{ie} \parallel R_{te}$$

The input resistance seen looking into the v_b node is

$$r_{ib} = r_x + (1 + \beta) r_e + R_{te} \frac{(1 + \beta) r_0 + R_{tc}}{r_0 + R_{te} + R_{tc}}$$

When the r_0 approximations are used, $v_{e(oc)}$, r_{ie} , and r_{ib} are replaced with

$$v_{e(oc)} \simeq v_{tb}$$

$$r_{ie} \simeq r'_e$$

$$r_{ib} \simeq r_x + (1 + \beta) (r_e + R_{te})$$

Example 5 Fig. 6 shows the circuit diagrams of NPN and PNP single-stage CC amplifiers. For each circuit, it is given that $R_S = 5 \text{ k}\Omega$, $R_1 = 120 \text{ k}\Omega$, $R_2 = 100 \text{ k}\Omega$, $R_E = 5.6 \text{ k}\Omega$, $R_3 = 100 \Omega$, $R_L = 20 \text{ k}\Omega$, $V^+ = 15 \text{ V}$, $V^- = -15 \text{ V}$, $V_{BE} = 0.65 \text{ V}$, $\beta = 99$, $\alpha = 0.99$, $r_x = 20 \Omega$, $V_A = 100 \text{ V}$ and $V_T = 0.025 \text{ V}$. Solve for the gain $A_v = v_o/v_s$, the input resistance r_{in} , and the output resistance r_{out} . The capacitors can be assumed to be ac short circuits at the operating frequency.

Solution. Because the dc bias circuits are the same as for the common-emitter amplifiers, the bias currents and voltages are the same. In addition, r_e is the same. Because V_{CE} is different, a new value of r_0 must be calculated. The collector-to-emitter voltage is given by

$$V_{CE} = V_C - V_E = V^+ - \left(V_{BB} - \frac{I_E}{1 + \beta} R_{BB} - V_{BE} \right) = 17.01 \text{ V}$$

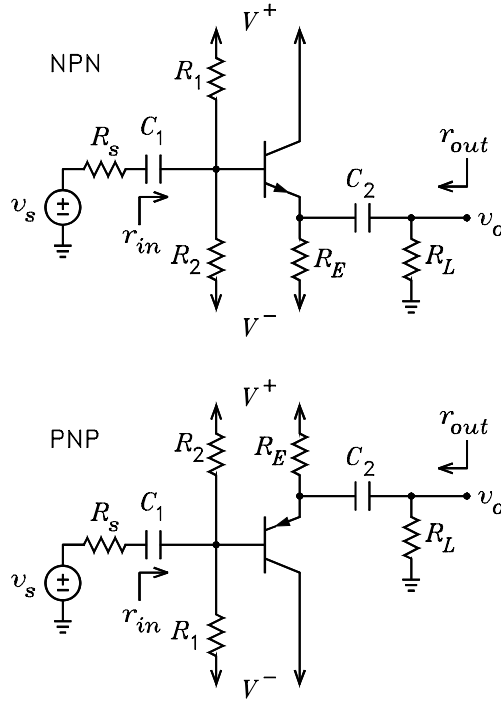


Figure 6: Single-stage common-collector amplifiers.

Thus r_0 has the value

$$r_0 = \frac{V_A + V_{CE}}{\alpha I_E} = 55.93 \text{ k}\Omega$$

For the small-signal analysis, V^+ and V^- are zeroed and the three capacitors are replaced with ac short circuits. The Thévenin voltage and resistance seen looking out of the base are given by

$$v_{tb} = v_s \frac{R_1 \parallel R_2}{R_S + R_1 \parallel R_2} = 0.916 v_s \quad R_{tb} = R_S \parallel R_1 \parallel R_2 = 4.58 \text{ k}\Omega$$

The Thévenin resistances seen looking out of the emitter and the collector are

$$R_{te} = R_E \parallel R_3 = 4.375 \text{ k}\Omega \quad R_{tc} = 0$$

Next, we calculate r'_e , $v_{e(oc)}$, r_{ie} , and r_{ib} .

$$r'_e = \frac{R_{tb} + r_x}{1 + \beta} + r_e = 57.83 \text{ }\Omega$$

$$v_{e(oc)} = v_{tb} \frac{r_0 + R_{tc} / (1 + \beta)}{r'_e + r_0 + R_{tc} / (1 + \beta)} = 0.999 v_{tb}$$

$$r_{ie} = r'_e \frac{r_0 + R_{tc}}{r'_e + r_0 + R_{tc} / (1 + \beta)} = 57.77 \text{ }\Omega$$

$$r_{ib} = r_x + (1 + \beta) r_e + R_{te} \frac{(1 + \beta) r_0 + R_{tc}}{r_0 + R_{te} + R_{tc}} = 407 \text{ k}\Omega$$

The output voltage is given by

$$v_o = v_{e(oc)} \frac{R_{te}}{r_{ie} + R_{te}} = \frac{R_{te}}{r_{ie} + R_{te}} \times 0.999 \times 0.916v_s = 0.903v_s$$

Thus the voltage gain is $A_v = 0.903$. The input and output resistances are given by

$$r_{in} = R_1 \parallel R_2 \parallel r_{ib} = 48.1 \text{ k}\Omega \quad r_{out} = r_{ie} \parallel R_E \parallel R_L = 57.02 \text{ }\Omega$$

The solutions for the PNP amplifier are the same as for the NPN circuit.

Example 6 *If the r_0 approximations are used, calculate the new voltage gain and input resistance for the CB amplifiers.*

Solution. In this case, $v_{e(oc)}$, r_{ie} , and r_{ib} change. The approximate values are given by

$$v_{e(oc)} \simeq v_{tb} = 0.916v_s \quad r_{ie} \simeq r'_e = 57.83 \text{ }\Omega$$

$$r_{ib} \simeq r_x + (1 + \beta)(r_e + R_{te}) = 438.7 \text{ k}\Omega$$

The new voltage gain, output resistance, and input resistance are given by

$$A_v = \frac{R_{te}}{r_{ie} + R_{te}} \times 0.916 = 0.904 \quad r_{out} = r_{ie} \parallel R_E \parallel R_L = 57.08 \text{ }\Omega$$

$$r_{in} = R_E \parallel r_{ie} = 48.51 \text{ k}\Omega$$

These answers are close to those for the exact solution.