

ECE 3050 Analog Electronics Quiz 2


January 23, 2009

Professor Leach Last Name: _____ First Name: _____

Instructions. Print your name in the spaces above. Place a box around any answer. **Honor Code Statement:**

I have neither given nor received help on this quiz. Initials _____

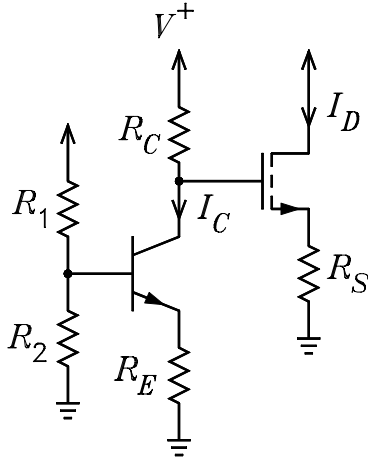1. For the circuit given, $V^+ = 24\text{ V}$, $R_1 = 112\text{ k}\Omega$, $R_2 = 10\text{ k}\Omega$, $V_{BE} = 0.65\text{ V}$, $\beta = 99$, $\alpha = 0.99$, $R_S = 4\text{ k}\Omega$, $K = 0.5\text{ mA/V}$, $V_{TO} = 2\text{ V}$, $I_C = \alpha I_E = \beta I_B$, and $I_D = K(V_{GS} - V_{TO})^2$.
- (a) Solve for R_E for $I_C = 1.2\text{ mA}$.
- (b) Solve for R_C for $I_D = 2\text{ mA}$.



$$R_1 := 112000 \quad R_2 := 10000 \quad V_{BE} := 0.65 \quad \beta := 99 \quad \alpha := 0.99 \quad R_S := 4000$$

$$K := 0.0005 \quad V_{TO} := 2 \quad V_p := 24 \quad I_C := 0.0012 \quad I_D := 0.002$$

$$V_{BB} := V_p \cdot \frac{R_2}{R_1 + R_2} \quad V_{BB} = 1.967 \quad R_{BB} := R_p(R_1, R_2) \quad R_{BB} = 9.18 \cdot 10^3$$

$$R_E := \frac{\alpha}{I_C} \cdot \left(V_{BB} - \frac{I_C}{\beta} \cdot R_{BB} - V_{BE} \right) \quad R_E = 994.898$$

$$V_{GS} := \sqrt{\frac{I_D}{K}} + V_{TO} \quad V_{GS} = 4 \quad V_C := I_D \cdot R_S + V_{GS} \quad V_C = 12$$

$$R_C := \frac{V_p - V_C}{I_C} \quad R_C = 1 \cdot 10^4$$