

ECE 3050 Analog Electronics Quiz 13


April 15, 2009

Professor Leach

Name _____

Instructions. No calculators are allowed on this quiz. Print your name in the space above. **Honor Code:** *I have neither given nor received help on this quiz.* Initials _____

- 1 of 2. The figure shows a Wien Bridge oscillator that puts out a sine wave signal with no input signal.
- (a) In words, how would you go about solving for the frequency at which this circuit would oscillate? Answer: Break the loop between V_o and C_2 , solve for the frequency at which the phase of the loop-gain transfer function is zero degrees, choose R_3 and R_F so that the loop gain is unity.
- (b) One of the resistors in the circuit is to be varied electronically to maintain a constant amplitude sine wave at the op-amp output. If the value of the resistor increases as the amplitude of the output sine wave increases, which resistor would you vary? Explain your choice. If $v_o(t)$ is increasing in amplitude, the gain of the op amp must be decreased to stabilize the amplitude. If the resistor increases in value, it should be where R_3 is in the circuit.

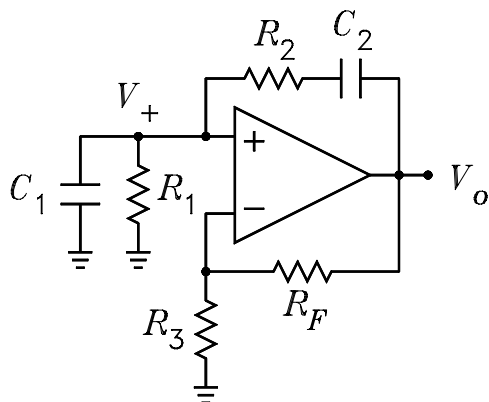


- 2 of 2. The block diagram of an oscillator which uses an inverting amplifier with a gain $-K$ is shown. The feedback network has the transfer function

$$H(s) = \frac{1}{(1 + s/\omega_0)^3}$$

- (a) Solve for the frequency at which the phase of the loop-gain transfer function $-KH(s)$ is 0° (or any multiple of 360°).
 Answer: The phase of $H(j\omega)$ must be -180° . This occurs when

$$\tan^{-1}\left(\frac{\omega}{\omega_0}\right) = 60^\circ \implies \omega = \omega_0 \tan(60^\circ) = \omega_0\sqrt{3}$$

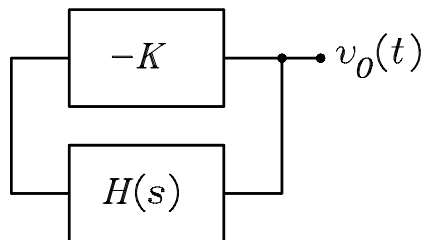- (b) If the circuit is to oscillate at the frequency found in part (a), what must be the value of K ?



At the oscillation frequency, $K |H(j\omega/\omega_0)| = K |1 + j\sqrt{3}|^{-3} = 1$ or $K = |1 + j\sqrt{3}|^3 = 8$.