

Common-Collector Amplifier Example


$$R_p(x,y) := \frac{x \cdot y}{x + y} \quad \text{Function for calculating parallel resistors.}$$

$$R_1 := 100000 \quad R_2 := 120000 \quad R_C := 0 \quad R_E := 5600 \quad R_S := 5000 \quad R_L := 10000$$


$$V_{\text{plus}} := 15 \quad V_{\text{minus}} := -15 \quad V_{BE} := 0.65 \quad V_T := 0.025 \quad \beta := 99 \quad \alpha := 0.99$$

$$r_x := 20 \quad r_0 := 50000$$
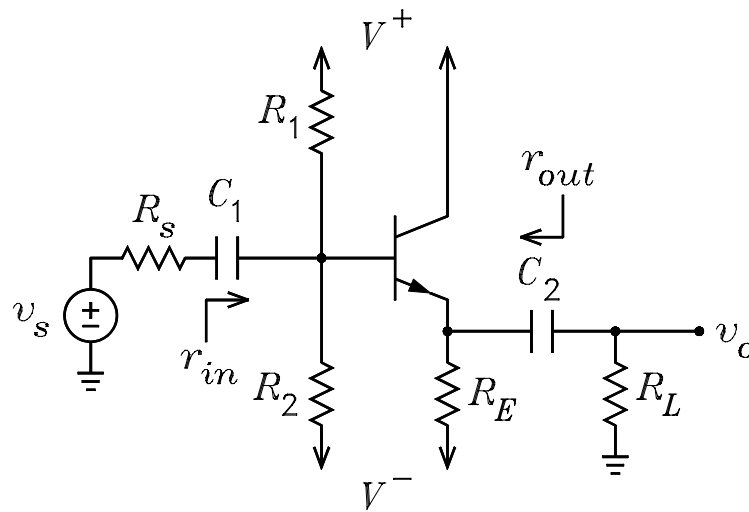
$$v_s := 1 \quad \text{With } v_s = 1, \text{ the voltage gain is equal to } v_o.$$



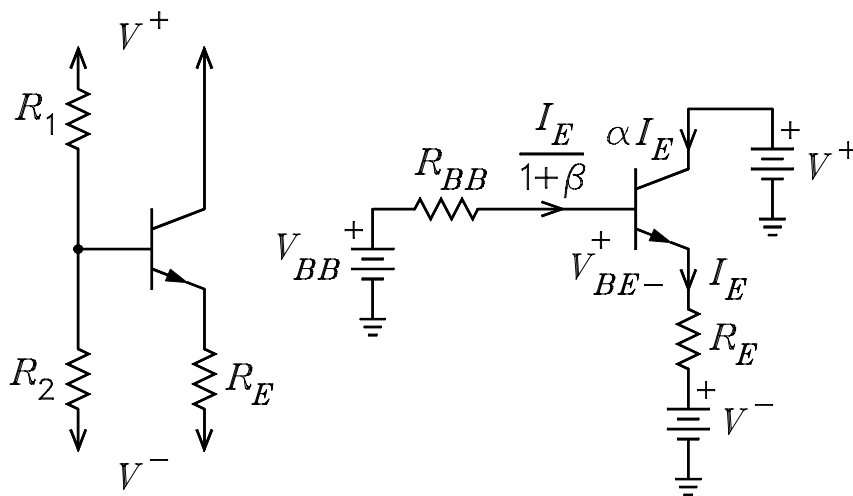DC Bias Circuits - The second circuit follows from a Thevenin equivalent circuit looking out of the base.



$$V_{BB} := \frac{V_{\text{plus}} \cdot R_2 + V_{\text{minus}} \cdot R_1}{R_1 + R_2} \quad V_{BB} = 1.364$$


$$R_{BB} := R_P(R_1, R_2) \quad R_{BB} = 5.455 \cdot 10^4$$

$$I_E := \frac{V_{BB} - V_{\text{minus}} - V_{BE}}{\frac{R_{BB}}{1 + \beta} + R_E} \quad I_E = 2.557 \cdot 10^{-3}$$

$$r_e := \frac{V_T}{I_E} \quad r_e = 9.777$$

AC Solutions

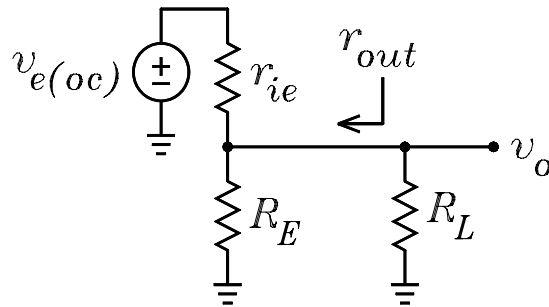This solution uses the equations involving R_{tc} , even though $R_{tc} = 0$. It is based on the Thevenin emitter circuit which has v_{eoc} in series with r_{ie} .



$$v_{tb} := v_s \cdot \frac{R_P(R_1, R_2)}{R_S + R_P(R_1, R_2)} \quad v_{tb} = 0.916$$

$$R_{tb} := R_P(R_S, R_P(R_1, R_2)) \quad R_{tb} = 4.58 \cdot 10^3$$

$$R_{te} := R_P(R_E, R_L) \quad R_{te} = 3.59 \cdot 10^3$$

$$r'_e := \frac{R_{tb} + r_x}{1 + \beta} + r_e \quad r'_e = 55.779$$

$$R_{tc} := R_C \quad R_{tc} = 0$$


$$v_{eoc} := v_{tb} \cdot \frac{r_0 + \frac{R_{tc}}{1 + \beta}}{r'_e + r_0 + \frac{R_{tc}}{1 + \beta}} \quad v_{eoc} = 0.915$$

$$r_{ie} := r'_e \cdot \frac{r_0 + R_{tc}}{r'_e + r_0 + \frac{R_{tc}}{1 + \beta}} \quad r_{ie} = 55.717$$

$$v_o := v_{eoc} \cdot \frac{R_P(R_E, R_L)}{r_{ie} + R_P(R_E, R_L)} \quad v_o = 0.901$$

$$A_v := v_o \quad A_v = 0.901 \quad \text{This is the voltage gain.}$$

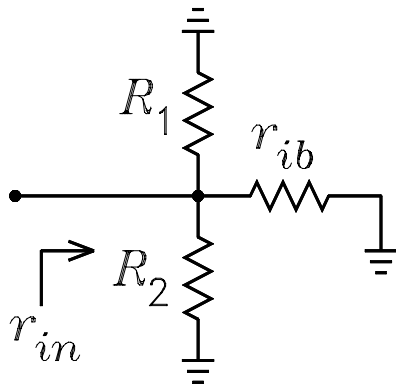
$$r_{out} := R_P(r_{ie}, R_E) \quad r_{out} = 55.168$$



$$r_{ib} := r_x + (1 + \beta) \cdot r_e + R_{te} \cdot \frac{(1 + \beta) \cdot r_0 + R_{tc}}{r_0 + R_{te} + R_{tc}} \quad r_{ib} = 3.359 \cdot 10^5$$

$$r_{in} := R_P(r_{ib}, R_P(R_1, R_2)) \quad r_{in} = 4.693 \cdot 10^4$$

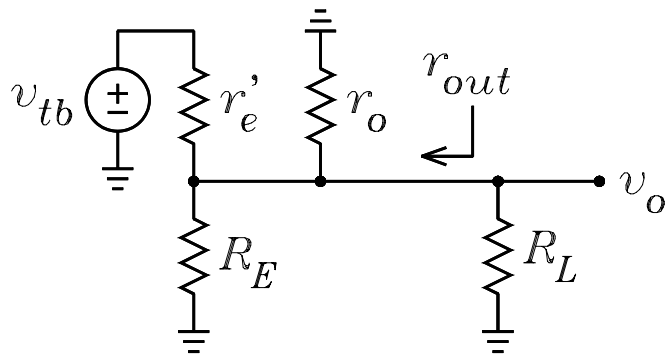The following solution is based on the simplified T model. I prefer it when $R_{tc} = 0$. Note that this is an exact solution, where r_o is considered to be an external resistor. The answers are the same as the ones in the solution above.



$$v_o := v_{tb} \cdot \frac{R_P(R_E, R_P(r_o, R_L))}{r_{ie} + R_P(R_E, R_P(r_o, R_L))} \quad v_o = 0.901$$

$$A_v := v_o \quad A_v = 0.901 \quad \text{This is the voltage gain.}$$

$$r_{out} := R_P(r_{ie}, R_P(r_o, R_E)) \quad r_{out} = 55.107$$

$$r_{ib} := r_x + (1 + \beta) \cdot (r_e + R_P(R_E, R_P(r_o, R_L))) \quad r_{ib} = 3.359 \cdot 10^5$$

$$r_{in} := R_P(r_{ib}, R_P(R_1, R_2)) \quad r_{in} = 4.693 \cdot 10^4$$

Note that the CC amplifier has a voltage gain that is just less than unity, a low output resistance, and a high input resistance.

Approximate Solution 1

Assume $r_x = 0$ and $r_0 = \infty$. See the class notes for the derivation of the gain expression.

$$g_m := \frac{\alpha \cdot I_E}{V_T} \quad g_m = 0.101 \quad r_{ib} := (1 + \beta) \cdot (r_e + R_{te}) \quad r_{ib} = 3.6 \cdot 10^5$$

$$A_v := \frac{R_P(R_1, R_2)}{R_S + R_P(R_1, R_2)} \cdot \frac{r_{ib}}{R_{tb} + r_{ib}} \cdot \frac{\frac{g_m \cdot R_{te}}{\alpha}}{1 + \frac{g_m \cdot R_{te}}{\alpha}} \quad A_v = 0.902$$

This is very close to the exact solution above.

$$r_{in} := R_P(r_{ib}, R_P(R_1, R_2)) \quad r_{in} = 4.737 \cdot 10^4 \quad r_{out} := R_P(r_e, R_{te}) \quad r_{out} = 54.925$$

These are close to the exact solutions above.

Approximate Solution 2

Assume $r_x = 0$ and $r_0 = \infty$. See the class notes for the derivation of the gain expression.

$$A_v := \frac{R_P(R_1, R_2)}{R_S + R_P(R_1, R_2)} \cdot \frac{(1 + \beta) \cdot R_{te}}{R_{tb} + r_{ib}} \quad A_v = 0.902$$

This is the same answer as Approximate Solution 1. The answers for r_{in} and r_{out} are the same.

Note that both approximate solutions can be made exact if r_{ib} is added back to r_{ib} and r_0 is combined in parallel with R_{te} . The latter can be done only when $R_{tc} = 0$.