

### Thévenin Source Circuit with Body Effect

Figure 1(a) shows the MOSFET with a Thévenin source connected to its gate, the body lead connected to signal ground, and the external drain load represented by the resistor  $R_{td}$ . The Thévenin equivalent circuit seen looking into the source can be obtained from the Thévenin equivalent circuit seen looking into the BJT emitter by replacing  $v_{e(oc)}$  with  $v_{s(oc)}$ ,  $r_{ie}$  with  $r_{is}$ ,  $v_{tb}$  with  $v_{tg}/(1 + \chi)$ ,  $R_{tb}$  with  $R_{tg}$ ,  $R_{tc}$  with  $R_{td}$ ,  $r'_e$  with  $r'_s$ , setting  $\alpha = 1$ , and setting  $\beta = \infty$ . The circuit is given in Fig. 1(b), where  $v_{s(oc)}$  and  $r_{is}$  are given by

$$v_{s(oc)} = \frac{v_{tg}}{1 + \chi} \frac{r_0}{r_0 + r'_s} \quad (1)$$

$$r_{is} = r'_s \frac{r_0 + R_{td}}{r_0 + r'_s} \quad (2)$$

The equations for the case where the body is connected to the source are obtained by setting  $\chi = 0$ .

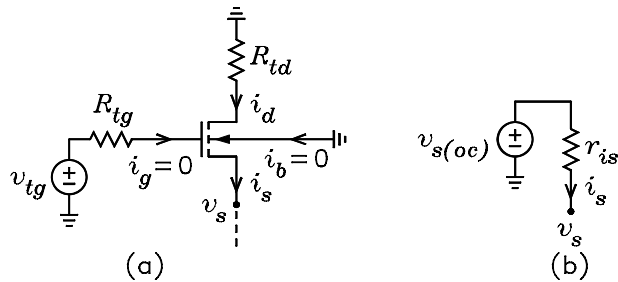


Figure 1: (a) MOSFET with Thévenin source connected to gate. (b) Thévenin source circuit.