

## Thévenin Base Circuit

Although the base is not an output terminal, the Thévenin equivalent circuit seen looking into the base is useful in calculating the base current. It consists of a voltage source  $v_{b(oc)}$  in series with a resistor  $r_{ib}$  from the base node to signal ground. Fig. 1(a) shows the BJT symbol with a Thévenin source connected to its emitter. Fig. 1(b) shows the T model for calculating the open-circuit base voltage. Because  $i_b = 0$ , it follows that  $i'_e = 0$ . Thus there is no drop across  $r_x$  and  $r_e$  so that  $v_{b(oc)}$  is given by

$$v_{b(oc)} = v_e = v_{te} \frac{r_0 + R_{tc}}{R_{te} + r_0 + R_{tc}} \quad (1)$$

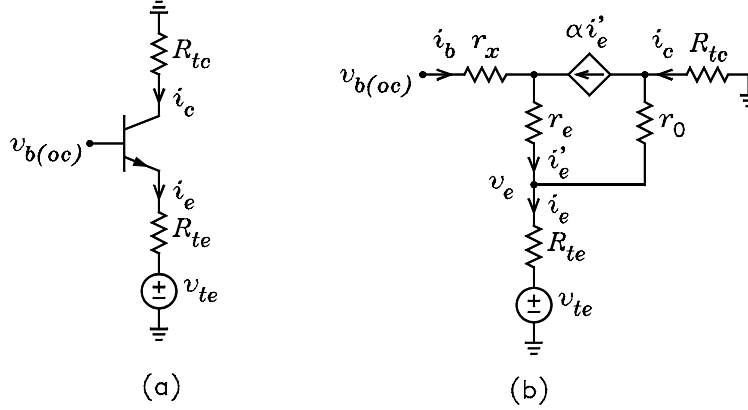


Figure 1: (a) BJT with Thévenin source connected to the emitter. (b) T model for calculating  $v_{b(oc)}$ .

The next step is to solve for the resistance seen looking into the base. It can be calculated by setting  $v_{te} = 0$  and connecting a test current source  $i_t$  to the base. It is given by  $r_{ib} = v_b/i_t$ . Fig. 2(a) shows the T circuit for calculating  $v_b$ , where the current source  $\beta i_t$  has been divided into identical series sources with their common node grounded to simplify use of superposition. By superposition of  $i_t$  and the two  $\beta i_t$  sources, we can write

$$v_b = i_t r_x + (i_t + \beta i_t) [r_e + R_{te} \parallel (r_0 + R_{tc})] - \beta i_t \frac{R_{tc} R_{te}}{R_{tc} + r_0 + R_{te}} \quad (2)$$

This can be solved for  $r_{ib}$  to obtain

$$\begin{aligned} r_{ib} &= \frac{v_b}{i_t} = r_x + (1 + \beta) [r_e + R_{te} \parallel (r_0 + R_{tc})] - \frac{\beta R_{tc} R_{te}}{R_{tc} + r_0 + R_{te}} \\ &= r_x + (1 + \beta) r_e + R_{te} \frac{(1 + \beta) r_0 + R_{tc}}{r_0 + R_{te} + R_{tc}} = r_x + r_\pi + R_{te} \frac{(1 + \beta) r_0 + R_{tc}}{r_0 + R_{te} + R_{tc}} \end{aligned} \quad (3)$$

The Thévenin base circuit is shown in Fig. 2(b).

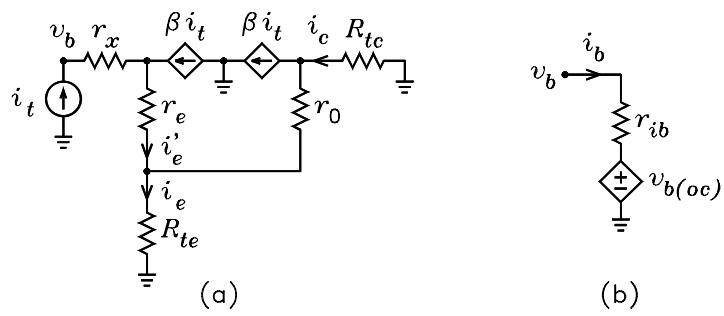


Figure 2: (a) Circuit for calculating  $v_b$ . (b) Thévenin base circuit.