

### ECE 3050 Analog Electronics Quiz 3

June 3, 2009

Professor Leach      Last Name: \_\_\_\_\_ First Name: \_\_\_\_\_


**Instructions. Print** your name in the spaces above. Place a box around any answer. **Honor Code Statement:**

*I have neither given nor received help on this quiz.* Initials \_\_\_\_\_

$$i_D = K (v_{GS} - V_{TO})^2 \quad g_m = 2\sqrt{KI_D} \quad r_s = \frac{1}{g_m} \quad r_0 = \frac{1}{\lambda} + \frac{V_{DS}}{I_D} \quad r_{id} = r_0 (1 + g_m R_{ts}) + R_{ts}$$

For credit, you must give all equations that you use to calculate your answers. Credit will not be given for any answer without full supporting work.

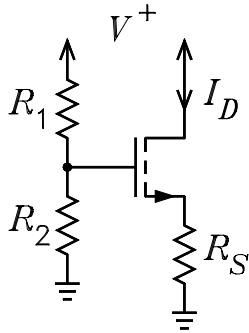1 of 2. For  $V^+ = +18\text{V}$ ,  $R_2 = 120\text{k}\Omega$ ,  $R_S = 800\Omega$ ,  $K = 5 \times 10^{-4}\text{S}$ , and  $V_{TO} = 2\text{V}$ , solve for  $R_1$  for  $I_D = 4.5\text{mA}$ .




$$V_p := 18 \quad K := 0.0005 \quad R_2 := 120000 \quad R_S := 800 \quad V_{TO} := 2 \quad I_D := 0.0045$$

$$V_{GS} := \sqrt{\frac{I_D}{K}} + V_{TO} \quad V_{GS} = 5 \quad V_G := V_{GS} + I_D \cdot R_S \quad V_G = 8.6$$

$$R_1 := R_2 \cdot \left( \frac{V_p}{V_G} - 1 \right) \quad R_1 = 1.312 \cdot 10^5$$

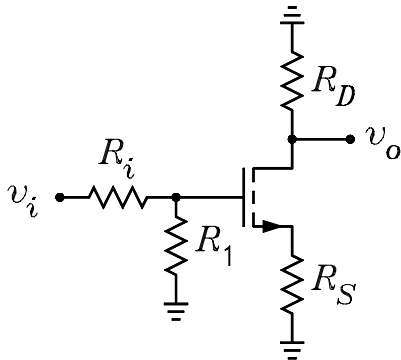2 of 2. For  $K = 5 \times 10^{-4}\text{S}$ ,  $V_{TO} = 2\text{V}$ ,  $I_D = 3\text{mA}$ ,  $r_{id} = 50\text{k}\Omega$ ,  $R_i = 2\text{k}\Omega$ ,  $R_1 = 22\text{k}\Omega$ ,  $R_S = 300\Omega$ , and  $R_D = 30\text{k}\Omega$ , solve for the small-signal voltage gain  $A_v = v_o/v_i$ .



$$K := 0.0005 \quad V_{TO} := 2 \quad I_D := 0.003 \quad r_{id} := 50000 \quad R_i := 2000 \quad R_1 := 22000$$

$$R_S := 300 \quad R_D := 30000 \quad g_m := 2 \cdot \sqrt{K \cdot I_D} \quad g_m = 2.449 \cdot 10^{-3} \quad r_s := g_m^{-1} \quad r_s = 408.248$$

$$A_v := \frac{R_1}{R_i + R_1} \cdot \frac{1}{r_s + R_S} \cdot R_{p2}(r_{id}, R_D) \quad A_v = -24.268$$