

ECE 3050 Analog Electronics Quiz 5

June 17, 2009

Professor Leach Last Name: _____ First Name: _____


Instructions. Print your name in the spaces above. Place a box around any answer. **Honor Code Statement:**

I have neither given nor received help on this quiz. Initials _____

$$g_m = 2\sqrt{KI_D} \quad g_{mb} = \chi g_m \quad r_s = \frac{1}{g_m} \quad r'_s = \frac{r_s}{1 + \chi} \quad r_0 = \frac{1}{\lambda} + \frac{V_{DS}}{I_D} \quad r_{id} = r_0(1 + g_m R_{ts}) + R_{ts}$$

For credit, you must give all equations that you use to calculate your answers. Credit will not be given for any answer without full supporting work.

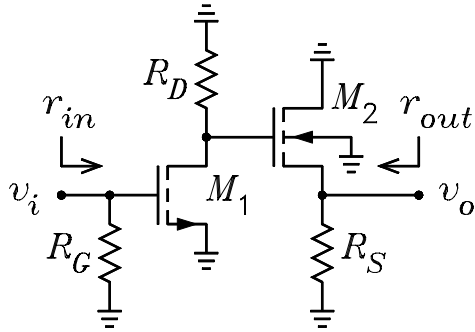1. The ac signal circuit of a CS/CD amplifier is shown. For $I_{D1} = I_{D2} = 2 \text{ mA}$, $R_G = 100 \text{ k}\Omega$, $R_S = 600 \Omega$, $R_D = 22 \text{ k}\Omega$, $K = 5 \times 10^{-4} \text{ A/V}^2$, $\chi = 0.25$, and $\lambda = 0$, solve for $A_v = v_o/v_i$, r_{in} , and r_{out} .



$$K := 0.0005 \quad \chi := 0.25 \quad I_D := 0.002 \quad R_G := 100000 \quad R_S := 600 \quad R_D := 22000$$

$$g_m := 2 \cdot \sqrt{K \cdot I_D} \quad g_m = 2 \cdot 10^{-3} \quad r_s := g_m^{-1} \quad r_s = 500$$

$$r'_s := \frac{r_s}{1 + \chi} \quad r'_s = 400 \quad A_v := g_m \cdot (-R_D) \cdot \frac{1}{1 + \chi} \cdot \frac{R_S}{r'_s + R_S} \quad A_v = -21.12$$

$$r_{in} := R_G \quad r_{in} = 1 \cdot 10^5 \quad r_{out} := R_{p2}(r'_s, R_S) \quad r_{out} = 240$$