

ECE 3050 Analog Electronics Quiz 7


July 7, 2010

Professor Leach

Name _____

Instructions. Print your name in the space above. **Honor Code:** *I have neither given nor received help on this quiz.* Initials _____

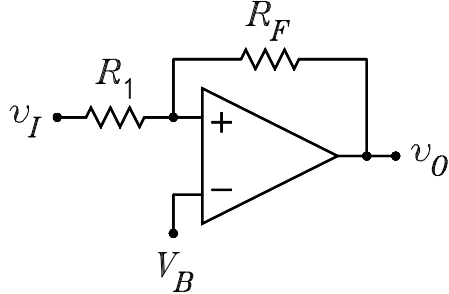1. Given $R_1 = 5\text{ k}\Omega$, $R_F = 30\text{ k}\Omega$, $V_B = 3\text{ V}$, and $V_{SAT} = 12\text{ V}$. Sketch the graph of v_O versus v_I for $-10\text{ V} \leq v_I \leq +10\text{ V}$



A non-inverting Schmitt trigger with trigger points v_{I1} and v_{I2} solved for as follows:

$$v_{I1} \frac{R_F}{R_1 + R_F} + V_{SAT} \frac{R_1}{R_1 + R_F} = V_B \quad \Rightarrow \quad v_{I1} = 1.5\text{ V}$$

$$v_{I2} \frac{R_F}{R_1 + R_F} - V_{SAT} \frac{R_1}{R_1 + R_F} = V_B \quad \Rightarrow \quad v_{I2} = 5.5\text{ V}$$

2. Given $R_1 = 1\text{ k}\Omega$, $R_2 = 2\text{ k}\Omega$, $R_3 = 3\text{ k}\Omega$, $R_4 = 4\text{ k}\Omega$, $R_5 = 5\text{ k}\Omega$, $R_6 = 6\text{ k}\Omega$, $R_7 = 7\text{ k}\Omega$, $R_8 = 8\text{ k}\Omega$, $R_9 = 9\text{ k}\Omega$, and $R_{10} = 1\text{ k}\Omega$.

- (a) For $v_{in} = 1\text{ V}$ and $i_{in} = 0$, solve for v_o .

$$v_o = v_{in} \left(-\frac{R_3}{R_1} \right) \left(-\frac{R_6}{R_4} \right) = 4.5\text{ V}$$

- (b) For $v_{in} = 0$ and $i_{in} = 1\text{ mA}$, solve for v_o .

$$v_o = i_{in} (R_8 \parallel R_9) \left(-\frac{R_{10}}{R_9} \right) \left(1 + \frac{R_6}{R_4 \parallel R_5} \right) = -1.74\text{ V}$$

