

# 4. BIPOLAR JUNCTION TRANSISTOR (BJT) NOISE MEASUREMENTS

---

## 4.1 Object

The objective of this experiment is to measure the mean-square equivalent input noise,  $\overline{v_{ni}^2}$ , and base spreading resistance,  $r_x$ , of some NPN Bipolar Junction Transistors (BJTs).

## 4.2 Theory

### 4.2.1 Equivalent Input Noise

It can be shown that  $v_{ni}^2$ , the mean-square equivalent input noise measured over a narrow frequency band  $\Delta f$  centered at frequency  $f$ , of a resistively loaded BJT amplifier with zero small-signal impedance from both base to ground and emitter to ground is given by

$$v_{ni}^2 = 4kTr_x\Delta f + \left(2q\frac{I_C}{\beta}\Delta f + \frac{K_f I_C \Delta f}{\beta f}\right) r_x^2 + 2qI_C\Delta f \left(\frac{r_x}{\beta} + \frac{V_T}{I_C}\right)^2 \quad (4.1)$$

where,  $r_x$  is the base spreading resistance (ohms),  $\beta = \Delta I_C / \Delta I_B$  is the small-signal current gain (dimensionless),  $I_C$  is the dc collector current (amps),  $I_B$  is the dc base current (amps),  $k = 1.38 \times 10^{-23} \text{ J K}^{-1}$  is Boltzmann's constant,  $T$  is the Kelvin temperature,  $q = 1.60 \times 10^{-19} \text{ C}$  is the electronic charge,  $V_T = kT/q$  is the thermal voltage (volts),  $K_f$  is the flicker noise-coefficient, and  $f$  is the frequency at which the mean-square noise voltage  $v_{ni}^2$  is measured. If the noise measurement is made at frequencies where the flicker noise may be ignored, the expression for the mean-square equivalent input noise simplifies to

$$v_{ni}^2 = 4kTr_x\Delta f + 2q\frac{I_C}{\beta}\Delta fr_x^2 + 2qI_C\Delta f \left(\frac{r_x}{\beta} + \frac{V_T}{I_C}\right)^2 \quad (4.2)$$

If  $\beta$  is sufficiently large, this can be approximated by

$$v_{ni}^2 = 4kTr_x\Delta f + 2qI_C\Delta f \left(\frac{V_T}{I_C}\right)^2 \quad (4.3)$$

This equation can be solved for  $r_x$  to obtain

$$r_x = \frac{v_{ni}^2}{4kT\Delta f} - \frac{2qI_C}{4kT} \left(\frac{V_T}{I_C}\right)^2$$

$$\begin{aligned}
&= \frac{v_{ni}^2}{4kT\Delta f} - \frac{V_T}{2I_C} \\
&= \frac{v_{ni}^2}{4kT\Delta f} - \frac{1}{2g_m}
\end{aligned} \tag{4.4}$$

#### 4.2.2 Base Spreading Resistance

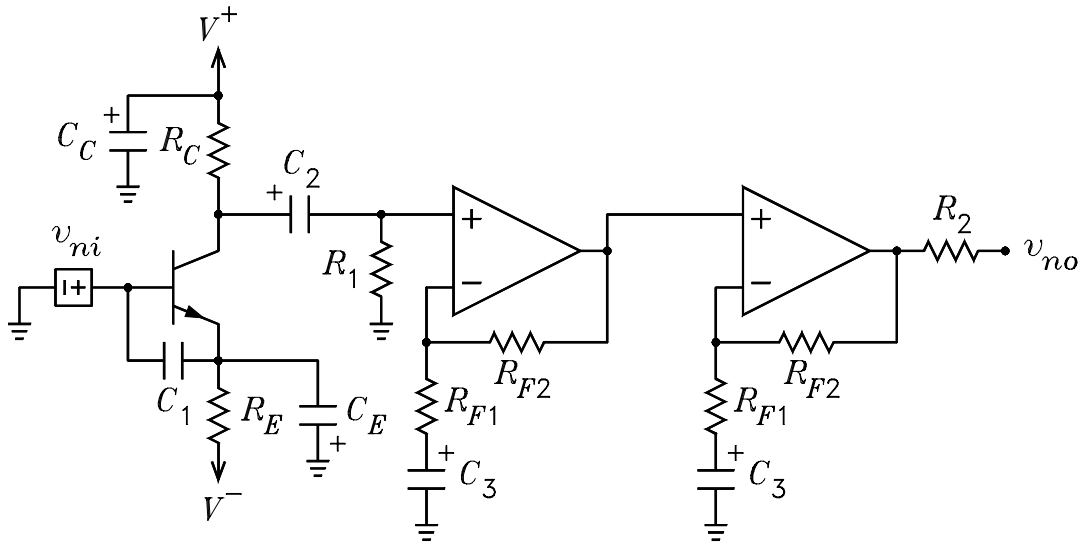


Figure 4-1 Circuit for measuring  $v_{no}$ .

The base spreading resistance  $r_x$  is one of the more prickly parameters to determine. To calculate it from Eq. (4.4),  $\overline{v_{ni}^2}$  must be measured. This is the mean-square noise voltage in series with the base of the BJT. A possible circuit for measuring it is shown in Fig. 4-1. If it is assumed that the op amps are ideal and the thermal noise in the feedback resistors can be ignored, the mean-square noise output voltage of the op amp can be written

$$v_{no}^2 = A_v^2 (g_m R_L)^2 v_{ni}^2 \tag{4.5}$$

$g_m R_L$  is the voltage gain from base to collector of the BJT,  $R_L = r_o \parallel R_C \parallel R_1$  is the resistance seen looking out of the BJT collector,  $r_o$  is the BJT collector-emitter resistance, and  $A_v$  is the gain of the two-stage op-amp amplifier given by

$$A_v = \left(1 + \frac{R_{F2}}{R_{F1}}\right)^2 \tag{4.6}$$

If  $v_{no}$  is measured, Eq. (4.5) can be solved for  $v_{ni}^2$  with

$$v_{ni}^2 = \frac{v_{no}^2}{A_v^2 (g_m R_L)^2} \tag{4.7}$$

## 4.3 Laboratory Procedure

### 4.3.1 Base Spreading Resistance

Assemble the circuit shown in Fig. 4-1 on a solderless breadboard using a 2N4401 NPN BJT. Use a TL071 as the op amp. Use  $V^+ = +15\text{ V}$  and  $V^- = -15\text{ V}$  (these may be reduced to  $9\text{ V}$  if the experimenters choose to assemble the circuits in the shielded boxes). Use  $C_1 = 100\text{ pF}$ ,  $C_2 = 10\text{ }\mu\text{F}$ ,  $C_3 = 330\text{ }\mu\text{F}$ ,  $C_C = C_E = 330\text{ }\mu\text{F}$ ,  $R_{F1} = 3\text{ k}\Omega$ , and  $R_2 = 100\text{ }\Omega$ . Calculate the value of  $R_{F1}$  which would give  $A_v = 100$ . In the circuit, use the next smaller 1% value for  $R_{F2}$ . Power supply decoupling networks on the supply rails consisting of  $100\text{ }\Omega$  resistors and  $100\text{ }\mu\text{F}$  capacitors should be used. The object of  $C_1$  is to suppress undesired rf pickup. It is small enough to be considered an open circuit at the measurement frequencies. The purpose of  $R_2$  is to suppress oscillations in the op amps. After the circuit is assembled, the gain and bandwidth of the op-amp stages should be measured.

Bias the circuit so that the collector current is  $I_C = 0.1\text{ mA}$ . The collector current is given by

$$I_C = \frac{-V^- - V_{BE}}{R_E} \quad (4.8)$$

where  $V_{BE}$  may be assumed to be  $0.65\text{ V}$ . Eq. (4.8) may be used to calculate  $R_E$ . (It should be borne in mind that  $V^-$  is a negative voltage so  $-V^-$  is a positive voltage.)

Select  $R_C = R_E/2$ . This places the collector to emitter bias voltage at approximately one-half the positive power supply voltage. The choice of this bias is somewhat arbitrary.

Place the BJT in the circuit and connect  $R_C$  as shown in the circuit diagram. Measure the dc collector current by using the DMM (Digital Multimeter) to measure the dc voltage across  $R_C$  and then use Ohm's law to determine the current. Measure the dc voltage at each terminal of the transistor.

Use the Dynamic Signal Analyzer to measure the rms noise output noise voltage  $v_{no}$  at a frequency that is high enough so that flicker noise may be neglected and at a low enough frequency so that the frequency response of the op amp and transistor in combination has not begun rolling. That is, make the measurement at a frequency where the noise output voltage is white (or flat) as a function of frequency. Call this value  $v_{no1}$ .

With the BJT not in the circuit, connect  $R_C$  from the left terminal to  $C_2$  to ground. Measure the rms noise output voltage  $v_{no}$ . Call this  $v_{no2}$ .

Repeat the measurement for bias currents of  $I_C = 30\text{ }\mu\text{A}$  and  $I_C = 50\text{ }\mu\text{A}$  for the 2N4401 NPN BJT.

Repeat the measurement for the 2N3904 NPN BJT.

### 4.3.2 Transistor Parameters

Use a transistor curve tracer to measure the small-signal current gain  $\beta$  and the collector-emitter resistance  $r_0$  of the 2N4401 and 2N3904 BJTs for collector currents of  $I_C = 0.1 \text{ mA}$ ,  $I_C = 30 \mu\text{A}$ , and  $I_C = 50 \mu\text{A}$  that were used above. In the small-signal model,  $r_0$  is given by

$$r_0 = \frac{V_A + V_{CE}}{I_C}$$

where  $V_A$  is the Early voltage,  $V_{CE}$  is the collector-emitter bias voltage, and  $I_C$  is the collector bias current.

### 4.3.3 Resistance Measurement

Use the DMM (Digital Multimeter) or the LCR meter to measure the value of each resistor that was used.

### 4.3.4 Measurement Bandwidth

Record the measurement bandwidth that was used by the Dynamic Signal Analyzer. Press Disp Format and then Measurement State.

## 4.4 Laboratory Report

### 4.4.1 Bias

Tabulate the quiescent bias voltages and currents for each transistor for each of the three values of collector current for which data was taken.

### 4.4.2 Base Spreading Resistance

From the data obtained, use Eqs. (4.4) and (4.7) to calculate  $r_x$  for each transistor at the three collector bias currents that were used. For  $v_{no}^2$  in Eq. (4.7), use

$$v_{no}^2 = v_{no1}^2 - v_{no2}^2$$

Calculate the average value of  $r_x$  for each transistor type at the three collector bias currents. Also tabulate the values of  $r_x$  for each of the transistors.

#### 4.4.3 Equivalent Input Noise

Use the values of that  $r_x$  were obtained to calculate  $v_{ni}^2$  using Eq. 4.2. Compare these results to those obtained from Eq. 4.7 and the measured values of  $v_{no}^2$ . Explain any significant differences between these results.