

ECE 6416 Assignment 3

1. For Problem 1 of Assignment 2, show that $F = 19.78$ and $NF = 12.96$ dB with R_1 and C_1 in the circuit. Show that $F = 6$ and $NF = 7.782$ dB if R_1 is replaced by an open circuit and C_1 is replaced by a short circuit.
2. The noise figure of an op amp is $NF = 5$ dB with a source resistance of $R_s = 10$ k Ω .
 - (a) Show that $v_{ni}/\sqrt{\Delta f} = 22.49$ nV/ $\sqrt{\text{Hz}}$.
 - (b) Show that the noise temperature is $T_n = 627$ K.
 - (c) Show that a resistor of value 21.6 k Ω at the op amp input would generate the same noise as the op amp.
3. For Problem 2 of Assignment 2:
 - (a) Use the v_{ni} found in part (c) of the problem to show that $F = 67.24$ and $NF = 18.28$ dB.
 - (b) Show that Eq. (6.71) gives the same results. The intermediate answers are $F_1 = 66$, $F_2 = 3125$, $G_{a1} = 2521$.
4. Given G_n , F_{min} , and $Z_{opt} = R_{opt} + jX_{opt}$ for an amplifier, show that

$$i_n^2 = 4kTG_n\Delta f \quad \gamma_i = \frac{-\text{sgn}(X_{opt})}{\sqrt{1 + (R_{opt}/X_{opt})^2}}$$

$$v_n^2 = \left(\frac{X_{opt}}{\gamma_i}\right)^2 i_n^2 \quad \gamma_r = \frac{2kT_0\Delta f}{\sqrt{v_n^2}\sqrt{i_n^2}} (F_{min} - 1) - \sqrt{1 - \gamma_i^2}$$

where $\text{sgn}(X_{opt}) = X_{opt}/|X_{opt}|$.

5. An amplifier has an input resistance of 150 Ω . Its noise parameters are $v_n/\sqrt{\Delta f} = 2$ nV/ $\sqrt{\text{Hz}}$, $i_n/\sqrt{\Delta f} = 10$ pA/ $\sqrt{\text{Hz}}$, and $\gamma = 0$. It is driven from a source having an output resistance of 75 Ω .
 - (a) Show that $v_{ni}/\sqrt{\Delta f} = 2.401$ nV/ $\sqrt{\text{Hz}}$.
 - (b) Show that $F = 4.802$ and $NF = 6.814$ dB.
 - (c) A resistor R_1 is added in series with the source to make the source impedance seen by the amplifier equal to Z_{opt} . Show that $R_1 = 125$ Ω . If the resistor is considered to be part of the source, not the amplifier, show that $F = 3.5$ and $NF = 5.441$ dB.
 - (d) The result for F above illustrates the noise factor fallacy. For a proper noise analysis, R_1 must be considered to be part of the amplifier, not the source. Show that the correct values are $F = 9.333$ and $NF = 9.7$ dB.
 - (e) Show that R_1 reduces the SNR by 2.886 dB.

6. The source in the amplifier of problem 5 is changed to one having an output resistance $R_s = 1 \text{ k}\Omega$.
- Show that $v_{ni}/\sqrt{\Delta f} = 10.95 \text{ nV}$.
 - Show that $F = 7.5$ and $NF = 8.751 \text{ dB}$.
 - A resistor R_2 is added in parallel with the source to make the source impedance seen by the amplifier equal to Z_{opt} . Show that $R_2 = 250 \Omega$. If the resistor is considered to be part of the source, not the amplifier, show that $F = 3.5$ and $NF = 5.441 \text{ dB}$.
 - The result for F above illustrates the noise factor fallacy. For a proper noise analysis, the parallel resistor must be considered to be part of the amplifier, not the source. Show that the correct values are $F = 17.5$ and $NF = 12.43 \text{ dB}$.
 - Show that R_2 reduces the SNR by 3.68 dB .
7. An amplifier has a voltage gain of 200 and an input resistance of $5 \text{ k}\Omega$. With a resistor of value $5 \text{ k}\Omega$ connected in parallel with its input, the output noise measures $447 \mu\text{V}$ over a noise bandwidth of 100 kHz . The $5 \text{ k}\Omega$ resistor is removed and a white noise source is connected through an attenuator to the input of the amplifier. The attenuator consists of a series $30 \text{ k}\Omega$ resistor and a shunt $6 \text{ k}\Omega$ resistor. The output resistance of the attenuator is $5 \text{ k}\Omega$. The source voltage over a noise bandwidth of 100 kHz has the value $v_n = 53.7 \mu\text{V}$. With the source activated, show that the noise output voltage from the amplifier increases to 1 mV . Use this information to show that $F = 2.5$ and $NF = 3.98 \text{ dB}$.
8. An amplifier is connected to a source with an output resistance R_s through a lossy transmission line having a characteristic impedance $Z_c = R_s$. If the loss in the cable is $k \text{ dB}$, show that the noise figure is increased by $k \text{ dB}$. Hint: Let $K = 10^{-k/20}$. The open-circuit voltage at the amplifier input is $V_{i(oc)} = KV_s + V_{ts} + V_n + I_n R_s = K(V_s + V_{ni})$. It follows that $V_{ni} = (V_{ts} + V_n + I_n R_s) / K$ and $F = v_{ni}^2 / v_{ts}^2$. Compare the value of F with $k = 0$ to the value for $k > 0$.