

## ECE 6416 Design Project Homework 1

An RF amplifier designed to operate at a frequency of 2.5 GHz has the following noise parameters:

Frequency	$NF_{min}$	$ \Gamma_{opt} $	$\angle\Gamma_{opt}$	$R_n$			
2.5 GHz	1.82 dB	0.38	$94.1^\circ$	$15\ \Omega$			
$ s_{11} $	$\angle s_{11}$	$ s_{21} $	$\angle s_{21}$	$ s_{12} $	$\angle s_{12}$	$ s_{22} $	$\angle s_{22}$
0.63	$-117^\circ$	6.4	$-97^\circ$	0.011	$-144^\circ$	0.21	$66^\circ$

The characteristic impedance of the transmission lines used to measure the parameter is  $Z_c = 50\ \Omega$ .

1. (a) Design a two transmission line noise matching network to match a  $50\ \Omega$  source to the input to the amplifier. Assume that each transmission line has a characteristic impedance  $Z_c = 75\ \Omega$ .
  - (b) Calculate the dB decrease of the operating gain  $G_P$  with the noise matching network compared to the operating gain which would be obtained with a conjugate matching network between the source and the amplifier. Note that  $\Gamma_{in}$  in the equation for  $G_P$  is the reflection coefficient looking into the matching network.
  - (c) Use a math program such as Matlab or Mathcad to calculate and plot the noise figure  $NF$  as a function of frequency over the band  $2.5\ \text{GHz} \pm 10\%$ .
2. Repeat problem (1) for a noise matching network consisting of a series capacitor  $C_1$  and a shunt inductor  $L_1$ .
3. Repeat problem (1) for a noise matching network consisting of a series inductor  $L_2$  and a shunt capacitor  $C_2$ .
4. Which network results in the lowest  $NF$  over the band about 2.5 GHz?