

## ECE 6416 Quiz 1


October 6, 2010

Professor Leach

Name \_\_\_\_\_

**Instructions.** Print your name in the space above and at the top of all other pages in your quiz. Clearly mark each answer. Express each numerical answer as a decimal number. Numerical values are  $4kT_0 = 1.6 \times 10^{-20}$  J and  $q = 1.6 \times 10^{-19}$  C. **Honor Code:** *I have neither given nor received help on this quiz.* Initials \_\_\_\_\_

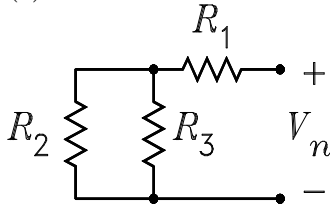1. The figure shows a resistive circuit.
  - (a) Solve for the mean-square value of  $V_n$  using the generalized Nyquist formula.
  - (b) Solve for  $V_n$  by replacing each resistor with its Thévenin model and using superposition. Convert the answer to the mean-square value.
  - (c) Show that the two solutions are equivalent.



(a)


$$v_n^2 = 4kT (R_1 + R_2 \parallel R_3) \Delta f$$

(b)

$$\begin{aligned} V_n &= V_{t1} + V_{t2} \frac{R_3}{R_2 + R_3} + V_{t3} \frac{R_2}{R_2 + R_3} \\ v_n^2 &= 4kTR_1 \Delta f + 4kTR_2 \Delta f \left( \frac{R_3}{R_2 + R_3} \right)^2 + 4kTR_3 \Delta f \left( \frac{R_2}{R_2 + R_3} \right)^2 \\ &= 4kT \left( R_1 + \frac{R_2 R_3^2 + R_2^2 R_3}{(R_2 + R_3)^2} \right) \Delta f \\ &= 4kT (R_1 + R_2 \parallel R_3) \Delta f \end{aligned}$$

(c) They are already equal to each other.

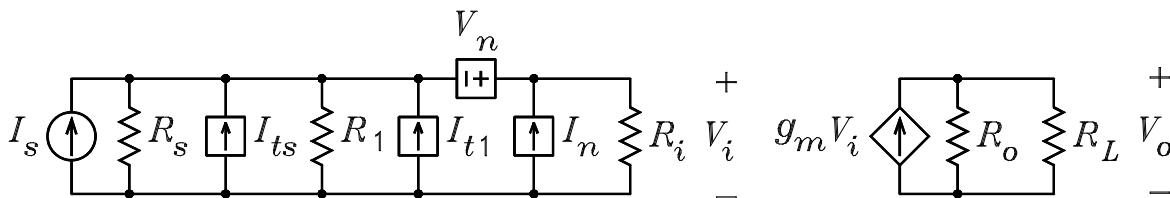2. Shown is the noise model of an amplifier.
  - (a) Solve for the noise current  $I_{ni}$  in parallel with  $I_s$  that generates the same noise as all noise sources in the circuit.
  - (b) Set  $I_{ni} = I_{ts} + V_n'/R_s + I_n'$  and solve for  $V_n'$  and  $I_n'$ .
  - (c) Solve for the mean-square values  $v_n'^2 = \overline{V_n' V_n'^*}$  and  $i_n'^2 = \overline{I_n' I_n'^*}$ . In the expressions, let  $\overline{V_n' I_n'^*} = v_n' i_n' \gamma$ . Express all answers in terms of  $v_n$  (or  $v_n^2$ ),  $i_n$  (or  $i_n^2$ ), and  $\gamma$ .
  - (d) Solve for  $\overline{V_n' I_n'^*}$  in the expression for the correlation coefficient  $\gamma' = \overline{V_n' I_n'^*} / v_n' i_n'$  between  $V_n'$  and  $I_n'$ . You do not have to write out the equation for  $\gamma'$ .



(a)

$$I_{i(sc)} = I_s + I_{ts} + I_{t1} + I_n + \frac{V_n}{R_s \parallel R_1} = I_s + I_{ni}$$
$$I_{ni} = I_{ts} + I_{t1} + I_n + \frac{V_n}{R_s \parallel R_1} = I_{ts} + I_{t1} + I_n + \frac{V_n}{R_1} + \frac{V_n}{R_s}$$

(b)

$$V'_n = V_n \quad I'_n = I_{t1} + I_n + \frac{V_n}{R_1}$$

(c)


$$v_n'^2 = v_n^2 \quad i_n'^2 = \frac{4kT\Delta f}{R_1} + i_n^2 + 2\gamma \frac{v_n i_n}{R_1} + \frac{v_n^2}{R_1^2}$$

(d)

$$\overline{V_n I_n^*} = V_n \overline{\left( I_{t1} + I_n + \frac{V_n}{R_1} \right)^*} = \frac{V_n V_n^*}{R_1} + \overline{V_n I_n^*} = \frac{v_n^2}{R_1} + \gamma v_n i_n$$

3. For  $R_1 = 4 \text{ k}\Omega$ ,  $R_2 = 2 \text{ k}\Omega$ , and  $C = 0.01 \text{ }\mu\text{F}$  and  $f = 10 \text{ kHz}$ ,

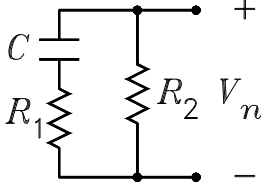- (a) Solve for the spot noise voltage in nV across the circuit due to  $R_1$ .  
(b) Solve for the spot noise voltage in nV across the circuit due to  $R_2$ .  
(c) Solve for the total spot noise voltage in nV across the circuit.



(a)

$$V_{n1} = V_{t1} \frac{R_2}{R_1 + R_2 + \frac{1}{j\omega C}} \quad v_{n1}^2 = 4kTR_1 \left| \frac{R_2}{R_1 + R_2 + \frac{1}{j\omega C}} \right|^2 = 2.58 \text{ nV}$$

(b)

$$V_{n2} = V_{t2} \frac{R_1 + \frac{1}{j\omega C}}{R_1 + R_2 + \frac{1}{j\omega C}} \quad v_{n2}^2 = 4kTR_2 \left| \frac{R_1 + \frac{1}{j\omega C}}{R_1 + R_2 + \frac{1}{j\omega C}} \right|^2 = 3.92 \text{ nV}$$

(c)

$$v_n^2 = \sqrt{v_{n1}^2 + v_{n2}^2} = 4.69 \text{ nV}$$