

Introduction to Electroacoustics and Audio Amplifier Design

W. Marshall Leach, Jr.
Georgia Institute of Technology
School of Electrical and Computer Engineering
Atlanta, Georgia 30332-0250 USA

Contents

1	Basic Principles of Sound	1
1.1	Sound	1
1.2	Sources of Sound	2
1.3	Velocity of Sound	2
1.4	Frequency of Sound	2
1.5	Pitch	3
1.6	Human Speech	5
1.7	Frequency Bands	5
1.8	Audio Sub Bands	6
1.9	Sound Pressure Level	8
1.10	Equal Loudness Contours	9
1.11	Loudness Levels	12
1.12	Audio Test Signals	14
1.13	Problems	18
2	Fundamentals of Acoustics	21
2.1	Basic Equations of Acoustics	21
2.2	The Acoustic Wave Equation	23
2.3	The Plane Wave	24
2.4	Specific Impedance	25
2.5	Acoustic Energy	25
2.6	Acoustic Intensity	26
2.7	Wavelength	27
2.8	Particle Displacement	28
2.9	The Simple Spherical Wave	28
2.10	Volume Velocity	30
2.11	Power Radiated in a Spherical Wave	32
2.12	Acoustic Images	33
2.13	The Directivity Pattern	35
2.14	The Plane Circular Piston	36
2.15	The Pattern Beamwidth	39
2.16	Fresnel Diffraction Effects	40
2.17	Acoustic Reflections	42
2.18	Problems	46

3	Analogous Circuits of Acoustical Systems	49
3.1	Acoustic Sources	49
3.2	Acoustic Impedance	50
3.3	The Plane Wave Tube	51
3.3.1	Infinitely Long Tube	53
3.3.2	Closed Tube	53
3.3.3	Open-Ended Tube	54
3.4	Acoustic Resistance	56
3.5	Acoustic Compliance	59
3.6	Acoustic Mass	60
3.7	Acoustic Impedance on a Piston in a Baffle	63
3.8	Radiation Impedance on a Piston in a Tube	67
3.9	Radiation Impedance on a Piston in Free Air	68
3.10	Problems	70
4	Analogous Circuits of Mechanical Systems	73
4.1	Mechanical Sources	73
4.2	Mass, Compliance, and Resistance	74
4.3	Mechanical Systems	76
4.4	Electromagnetic-Mechanical Transducer	78
4.5	Crystal Electrostatic-Mechanical Transducer	82
4.6	Condenser Electrostatic-Mechanical Transducer	83
4.7	Mechano-Acoustic Transducer	88
4.8	Problems	90
5	Microphones	93
5.1	Classifications	93
5.2	Modeling Diaphragm Reflections	94
5.3	Diaphragm Back Acoustical Load	97
5.4	Diaphragm Mechanical Parameters	98
5.5	Condenser Microphone	98
5.6	Condenser Microphone SPICE Simulation	102
5.7	Condenser Microphone Buffer Amplifiers	105
5.8	Dynamic Microphone	106
5.9	Ribbon Microphone	110
5.10	Proximity Effect	113
5.11	Combination Microphone	115
5.12	Problems	118
6	Moving-Coil Loudspeakers	119
6.1	Construction	119
6.2	Analogous Circuits	123
6.3	Combination Analogous Circuit	125
6.4	Infinite Baffle Analogous Circuit	126
6.5	Low-Frequency Solution for U_D	127
6.6	Low-Frequency Bode Plots for U_D	129

6.7	Small-Signal Parameters	130
6.8	High-Frequency Solution for U_D	131
6.9	On-Axis Pressure	133
6.10	Pressure Transfer Function	133
6.11	Bode Plots of On-Axis Pressure	134
6.12	Filter Theory Description of $G(s)$	136
6.13	Cutoff Frequencies	137
6.14	Effect of Non-Zero Generator Resistance	138
6.15	Frequency of Peak Response	139
6.16	Voice-Coil Impedance	140
6.17	On-Axis Pressure Sensitivity	142
6.18	Acoustic Power Response	144
6.19	Reference Efficiency	146
6.20	Diaphragm Displacement Function	146
6.21	Voice-Coil Electrical Power Rating	148
6.22	Displacement Limited Power Rating	148
6.23	SPICE Models	149
6.24	Problems	154
7	Closed-Box Loudspeaker Systems	159
7.1	Modeling the Box	159
7.2	The Analogous Circuits	162
7.3	The Volume Velocity Transfer Function	164
7.4	The On-Axis Pressure Transfer Function	165
7.5	Effect of the Box on the System Response	166
7.6	Sensitivity of the Lower Cutoff Frequency	168
7.7	System Design with a Given Driver	169
7.8	System Design From Specifications	171
7.9	A SPICE Simulation Example	173
7.10	Problems	176
8	Vented-Box Loudspeaker Systems	179
8.1	Modeling the Enclosure	179
8.2	Effect of the Vent	181
8.3	The On-Axis Pressure Transfer Function.	181
8.4	Voice-Coil Impedance Function	183
8.5	The Magnitude-Squared Function	184
8.6	The B4 Alignment	186
8.7	The QB3 Alignments	187
8.8	The Chebyshev Alignments	187
8.9	Example Pressure Responses	188
8.10	Design with a Given Driver	189
8.11	Design from Specifications	194
8.12	Vented-Box SPICE Example	195
8.13	Problems	199

9 Crossover Networks	203
9.1 Role of Crossover Networks	203
9.2 First-Order Networks	204
9.3 Second-Order Networks	206
9.4 Third-Order Networks	208
9.5 L-Pad Design	209
9.6 Constant-Voltage and All-Pass Functions	211
9.7 Effect of the Voice-Coil Impedance	212
9.8 Effect of the Driver Phase Response	213
9.9 Active Crossover Networks	218
9.9.1 Second-Order Filters	218
9.9.2 Third-Order Butterworth Filters	219
9.9.3 Fourth-Order Filters	220
9.10 SPICE Modeling Example	221
9.11 Problems	225
10 Acoustic Horns	229
10.1 The Webster Horn Equation	229
10.2 Salmon's Family of Horns	229
10.3 Finite Length Horn Size	232
10.4 A Horn Analogous Circuit	233
10.5 SPICE Examples	234
10.6 Horn Driving Units	239
10.7 Mid-Frequency Range	240
10.8 Condition for Maximum P_{AR}	242
10.9 The Horn Efficiency	242
10.10 The Low-Frequency Range	243
10.11 The High-Frequency Range	243
10.12 Low-Frequency System Design	244
10.12.1 Design with a Given Driver	244
10.12.2 System Design from Specifications	246
10.13 Problems	249
11 Audio Power Amplifiers	251
11.1 Power Specifications	251
11.2 Feedback Amplifier Gain	252
11.3 Effect of Feedback on Distortion and Noise	253
11.4 Effect of Feedback on Output Resistance	254
11.5 The Stability Criterion	255
11.6 The Single-Pole Amplifier	258
11.7 The Two-Pole Amplifier	260
11.8 The Alternate Stability Criterion	262
11.9 Techniques for Compensating Feedback Amplifiers	264
11.9.1 Gain Constant Reduction	267
11.9.2 First Pole Lag Compensation	268
11.9.3 Second Pole Lead Compensation	270

11.9.4 Feedforward Compensation	271
11.10 Signal Tracing	271
11.11 Power Supply Design	275
11.12 Amplifier Circuit Topologies	277
11.12.1 Power Output Stage	277
11.12.2 Voltage Gain Stage	281
11.12.3 Input Stage	284
11.12.4 Completed Amplifier Circuit	286
11.13 Gain-Bandwidth Product	288
11.14 Slew Rate	290
11.15 Decoupling and Grounding	291
11.16 Protection Circuits	293
11.17 Power Dissipation	299
11.18 Amplifier Measurements	299
11.18.1 Power Rating	299
11.18.2 Voltage Gain	300
11.18.3 Frequency Response	300
11.18.4 Output Resistance and Damping Factor	301
11.18.5 Slew Rate	301
11.18.6 Signal-to-Noise Ratio	302
11.18.7 Total Harmonic Distortion	302
11.18.8 Intermodulation Distortion	304
11.19 Problems	306
A References	313
B Driver Parameter Measurements	315
B.1 Basic Theory	315
B.2 The Measurement Test Set	316
B.3 Measuring R_E , f_S , Q_{MS} , Q_{ES} , and Q_{TS}	318
B.4 Measuring V_{AS}	319
B.5 Conversion to Infinite-Baffle Parameters	320
B.6 Measurement of L_E and R'_E	320
B.7 Summary Sheet	322
C 4th-Order Bandpass Systems	323
C.1 System Description	323
C.2 Output Volume Velocity	324
C.3 On-Axis Pressure	326
C.4 Fourth-Order Band-Pass Functions	326
C.5 System Parameters	327
C.6 Design Procedure	328
D Electroacoustic Glossary of Symbols	331
E The Isobaric Connection	335

F	6th-Order Bandpass Systems	339
F.1	System Transfer Function	339
F.2	System Alignment Functions	341
F.3	System Design from Specifications	342
F.4	Example System Design	343
G	Assisted Vented-Box Alignments	347
G.1	5th-Order Alignments	348
G.1.1	Butterworth	348
G.1.2	Chebyshev	348
G.2	6th-Order Alignments	349
G.2.1	Butterworth	349
G.2.2	Chebyshev	350
G.3	The Vented-Box System Parameters	350
G.4	Example Design from Specifications	351
H	A Closed-Box Equalizer	353
H.1	Equalizer Transfer Function	353
H.2	Equalizer Circuit	354
H.3	Example Realization	355
I	Passive Radiator Systems	357
I.1	System Transfer Function	357
I.2	Example System Design	359

Preface

This book is an outgrowth of a senior level elective course in audio engineering that I have taught to electrical engineering students at the Georgia Institute of Technology. The first part of the book covers basic acoustics. The emphasis is on that part of acoustics that pertains to the field of audio engineering. Most of the remainder of the book concerns the application of the tools of electroacoustics to the analysis and synthesis of microphones, loudspeakers, crossover networks, and acoustic horns. The book concludes with a chapter that covers the basic theory of audio amplifier design.

Electroacoustics is that part of acoustics that pertains to the modeling of acoustical systems with electrical circuits. Because most acoustical devices have a mechanical part, the modeling of mechanical systems with electrical circuits is a basic part of electroacoustics. Separate chapters in the book are devoted to analogous circuits of mechanical systems and to analogous circuits of acoustical systems. The traditional approach in these circuits has been to use transformers to model the coupling between the electrical, the mechanical, and the acoustical parts. A major departure in this book is the use of controlled sources to model the coupling. An advantage of this approach is that it avoids the need for mobility analogs in the acoustical circuits. In addition, the author has found that students have much less difficulty with the approach. Perhaps this is because the controlled-source circuits are more intuitive than the transformer circuits. In addition, the circuits can be easily analyzed with circuit simulation software such as SPICE.

Electroacoustic models are developed for the more common microphone types and for the moving-coil loudspeaker driver. Separate chapters cover closed-box and vented-box loudspeaker systems. Although the emphasis is on basic system theory, practical methods of design are also presented. Because crossover networks are such an important part of loudspeaker systems, a chapter is devoted to crossover networks. Acoustic horns are a vital component in public address systems. A chapter is devoted to horn models. In all cases, SPICE simulation examples are presented where appropriate.

One might ask why a chapter on audio amplifiers is included in a book that is primarily concerned with electroacoustics. Without a power amplifier, a loudspeaker could not make sound. Therefore, one might say that the role of an amplifier in a system is just as important as the role of a loudspeaker. The chapter on amplifiers is not intended to be an in-depth chapter on electronic theory. Instead, it addresses the more important aspects of amplifier design with an emphasis on the basic operation of the circuits. Practical examples are presented that illustrate how some of the pitfalls of amplifier design can be avoided.

The second edition corrects errors found by students and myself in the first edition. Also, six appendices have been added.

W. Marshall Leach, Jr.
April 1999